

28. Review

Dec. 10, 2018

- Algorithms
- Using building blocks
- Binary system
- Conversion between binary and decimal
- Sign extension and overflow
- Other bases

REVIEW SESSION

DEC. 16 (SUNDAY) 2:00 PM - -
(HERE) EER 1.516

TA OFFICE HOURS (EXTRA)

MON. DEC. 17

EER 4.704 2-5 PM

6 PM - - -

Converting Binary (2's C) to Decimal

1. If leading bit is one, take two's complement to get a positive number.
2. Add powers of 2 that have "1" in the corresponding bit positions.
3. If original number was negative, add a minus sign.

$$\begin{aligned} X &= 01101000_{\text{two}} \\ &= 2^6 + 2^5 + 2^3 = 64 + 32 + 8 \\ &= 104_{\text{ten}} \end{aligned}$$

n	2^n
0	1
1	2
2	4
3	8
4	16
5	32
6	64
7	128
8	256
9	512
10	1024

Assuming 8-bit 2's complement numbers.

Converting Decimal to Binary (2's C)

First Method: *Division*

1. Find magnitude of decimal number. (Always positive.)
2. Divide by two – remainder is least significant bit.
3. Keep dividing by two until answer is zero, writing remainders from right to left.
4. Append a zero as the MS bit;
if original number was negative, take two's complement.

$$X = 104_{\text{ten}}$$

$$104/2 = 52 \text{ r}0 \quad \textit{bit 0}$$

$$52/2 = 26 \text{ r}0 \quad \textit{bit 1}$$

$$26/2 = 13 \text{ r}0 \quad \textit{bit 2}$$

$$13/2 = 6 \text{ r}1 \quad \textit{bit 3}$$

$$6/2 = 3 \text{ r}0 \quad \textit{bit 4}$$

$$3/2 = 1 \text{ r}1 \quad \textit{bit 5}$$

$$1/2 = 0 \text{ r}1 \quad \textit{bit 6}$$

$$X = 01101000_{\text{two}}$$

Sign Extension

To add two numbers, we must represent them with the same number of bits.

If we just pad with zeroes on the left:

4-bit

0100 (4)

1100 (-4)

8-bit

00000100 (still 4)

00001100 (12, not -4)

Instead, replicate the MS bit -- the sign bit:

4-bit

0100 (4)

1100 (-4)

8-bit

00000100 (still 4)

11111100 (still -4)

Overflow

If operands are too big, then sum cannot be represented as an n -bit 2's comp number.

$$\begin{array}{r} 01000 \quad (8) \\ + 01001 \quad (9) \\ \hline 10001 \quad (-15) \end{array} \qquad \begin{array}{r} 11000 \quad (-8) \\ + 10111 \quad (-9) \\ \hline 01111 \quad (+15) \end{array}$$

We have overflow if:

- signs of both operands are the same, and
- sign of sum is different.

Another test -- easy for hardware:

- carry into MS bit does not equal carry out

↳ MOST SIGNIFICANT

Converting from Binary to Hexadecimal

Every four bits is a hex digit.

- start grouping from right-hand side

011101010001111010011010111

↓ ↓ ↓ ↓ ↓ ↓ ↓

3 A 8 F 4 D 7

*This is not a new machine representation,
just a convenient way to write the number.*

Examples of Logical Operations

AND **USEFUL AS "MASKS"**

- useful for clearing bits
 - AND with zero = 0
 - AND with one = no change

AND

11000101
00001111
00000101

OR

- useful for setting bits
 - OR with zero = no change
 - OR with one = 1

OR

11000101
00001111
11001111

NOT

- unary operation -- one argument
- flips every bit


NOT

11000101
00111010

Fractions: Fixed-Point

How can we represent fractions?

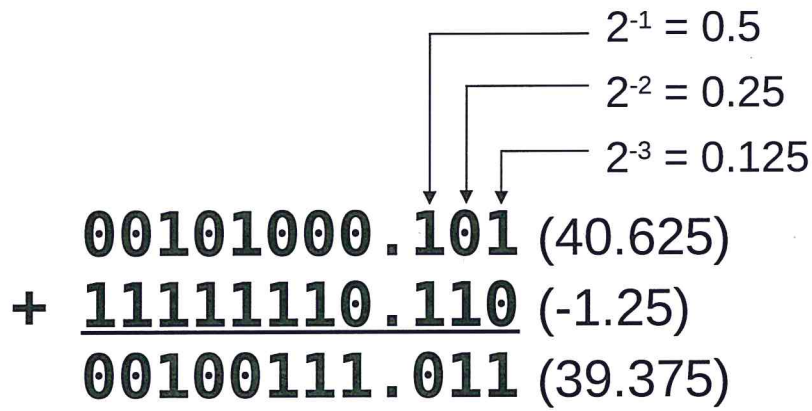- Use a “binary point” to separate positive from negative powers of two -- just like “decimal point.”
- 2’s comp addition and subtraction still work.
 - if binary points are aligned



The diagram shows a binary addition problem with three numbers aligned at their binary points. The first number is 00101000.101, the second is 11111110.110 (underlined), and the result is 00100111.011. Three arrows point from the binary point to the right to the first three bits of the fractional part of the first number, labeled with their respective weights: 2⁻¹ = 0.5, 2⁻² = 0.25, and 2⁻³ = 0.125.

$$\begin{array}{r} 00101000.101 \quad (40.625) \\ + \underline{11111110.110} \quad (-1.25) \\ \hline 00100111.011 \quad (39.375) \end{array}$$

No new operations -- same as integer arithmetic.

Very Large and Very Small: Floating-Point

Large values: 6.023×10^{23} -- requires 79 bits

Small values: 6.626×10^{-34} -- requires >110 bits

Use equivalent of “scientific notation”: $F \times 2^E$

Need to represent F (*fraction*), E (*exponent*), and sign.

IEEE 754 Floating-Point Standard (32-bits):




$$N = (-1)^S \times 1.\text{fraction} \times 2^{\text{exponent} - 127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = (-1)^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

IEEE 754 Floating Point Standard


Single Precision

 

$$\Rightarrow N = (-1)^S \times 1.\text{fraction} \times 2^{\text{exponent} - 127}, \quad 1 \leq \text{exponent} \leq 254$$
$$N = (-1)^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

Floating Point Example

 Single-precision IEEE floating point number:



- Sign is 1 – number is negative.
- Exponent field is 01111110 = 126 (decimal).
- Fraction is 0.100000000000... = 0.5 (decimal).

$$\text{Value} = -1.5 \times 2^{(126-127)} = -1.5 \times 2^{-1} = -0.75.$$

Text: ASCII Characters


ASCII: Maps 128 characters to 7-bit code.

- both printable and non-printable (ESC, DEL, ...) characters

00 nul	10 dle	20 sp	30 0	40 @	50 P	60 `	70 p
01 soh	11 dc1	21 !	31 1	41 A	51 Q	61 a	71 q
02 stx	12 dc2	22 "	32 2	42 B	52 R	62 b	72 r
03 etx	13 dc3	23 #	33 3	43 C	53 S	63 c	73 s
04 eot	14 dc4	24 \$	34 4	44 D	54 T	64 d	74 t
05 enq	15 nak	25 %	35 5	45 E	55 U	65 e	75 u
06 ack	16 syn	26 &	36 6	46 F	56 V	66 f	76 v
07 bel	17 etb	27 '	37 7	47 G	57 W	67 g	77 w
08 bs	18 can	28 (38 8	48 H	58 X	68 h	78 x
09 ht	19 em	29)	39 9	49 I	59 Y	69 i	79 y
0a nl	1a sub	2a *	3a :	4a J	5a Z	6a j	7a z
0b vt	1b esc	2b +	3b ;	4b K	5b [6b k	7b {
0c np	1c fs	2c ,	3c <	4c L	5c \	6c l	7c
0d cr	1d gs	2d -	3d =	4d M	5d]	6d m	7d }
0e so	1e rs	2e .	3e >	4e N	5e ^	6e n	7e ~
0f si	1f us	2f /	3f ?	4f O	5f _	6f o	7f del

CMOS

↳ TRANSISTORS TO (LOGIC) GATES

 


n-channel

~~CONDUCTS~~ IF $G=1V$ (EXAMPLE) LOGIC 1

G: GATE

S: SOURCE

D: DRAIN

 


p-channel CONDUCTS IF $G=0V$

~~(LOGIC 0)~~
(LOGIC 0)

LIKE A SWITCH



AND Gate

 

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Add inverter to NAND.


NAND Gate (AND-NOT)

  

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


Note: Parallel structure on top, serial on bottom.

NOR GATE

 


(OR-NOT)


Basic Logic Gates

 


NOT

 


OR

 

NOR

 

AND

 


NAND

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 

A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as A+B!

*To convert AND to OR
(or vice versa),
invert inputs and output.*


$$\overline{(X + Y)} = \overline{X} \cdot \overline{Y}$$

More than 2 Inputs?

AND/OR can take any number of inputs.

- AND = 1 if all inputs are 1.
- OR = 1 if any input is 1.
- Similar for NAND/NOR.

 
Can implement with multiple two-input gates,
or with single CMOS circuit.



Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

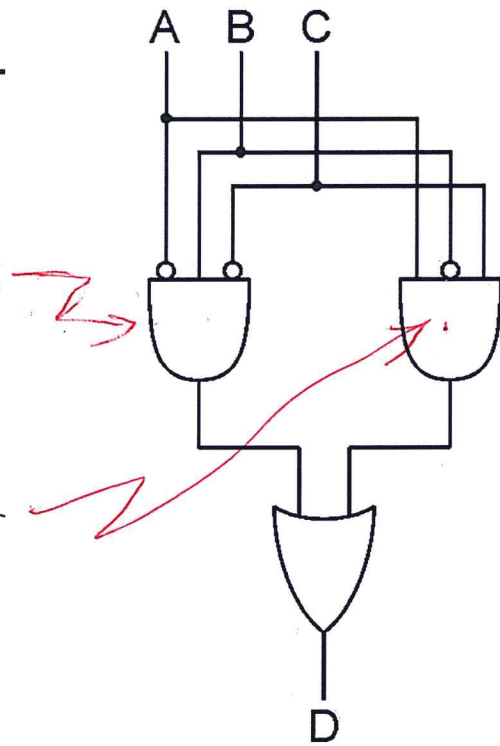


1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

Decoder

n inputs, 2^n outputs

 - exactly one output is 1 for each possible input pattern



ENCODER = 2^n INPUTS, n OUTPUTS
(ONE-HOT)



w	x	y	z	A	B
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

INVERSE OF
DECODER

Multiplexer (MUX)

n -bit selector and 2^n inputs, one output

 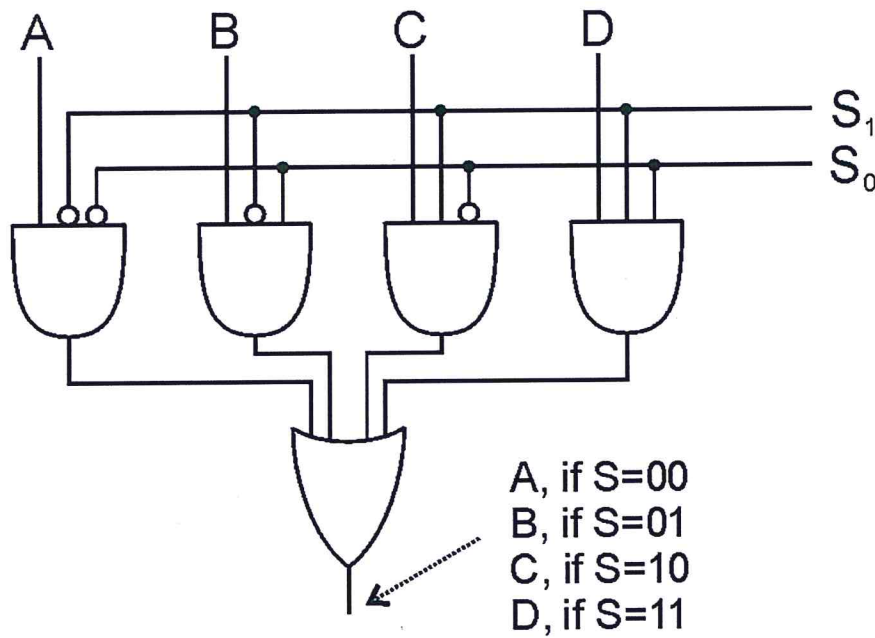- output equals one of the inputs, depending on selector




4-to-1 MUX

PRIORITY ENCODER


HIGH		LOW		O_3	O_2	O_1	O_0
W	X	Y	Z				
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Full Adder


A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Four-bit Adder

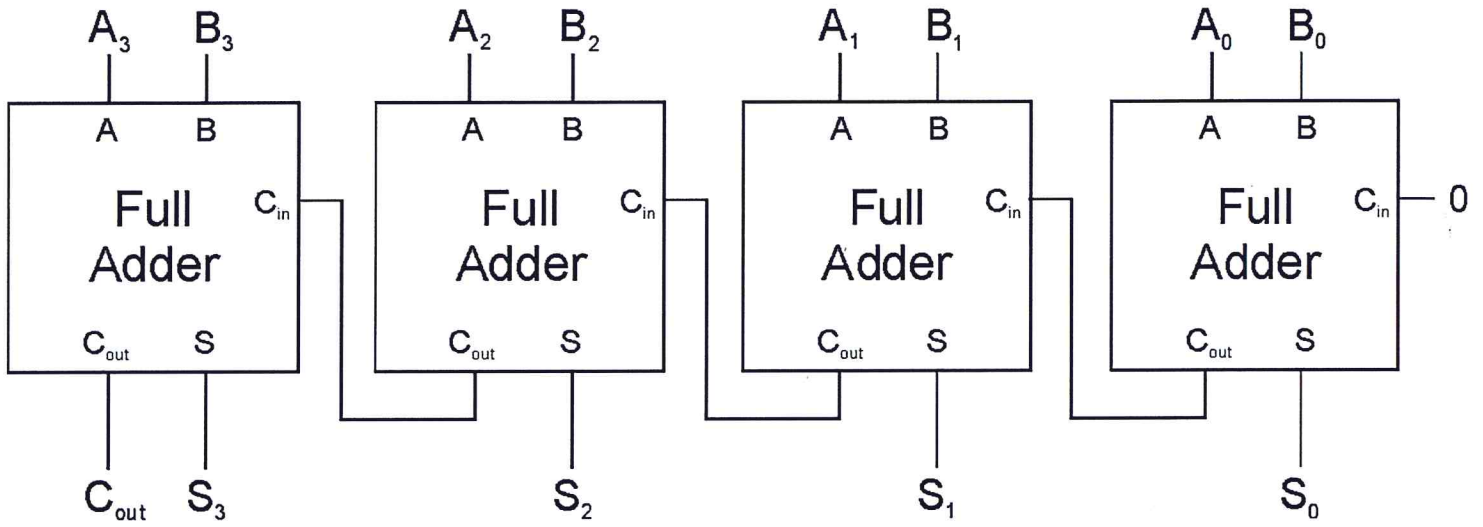





Programmable Logic Array

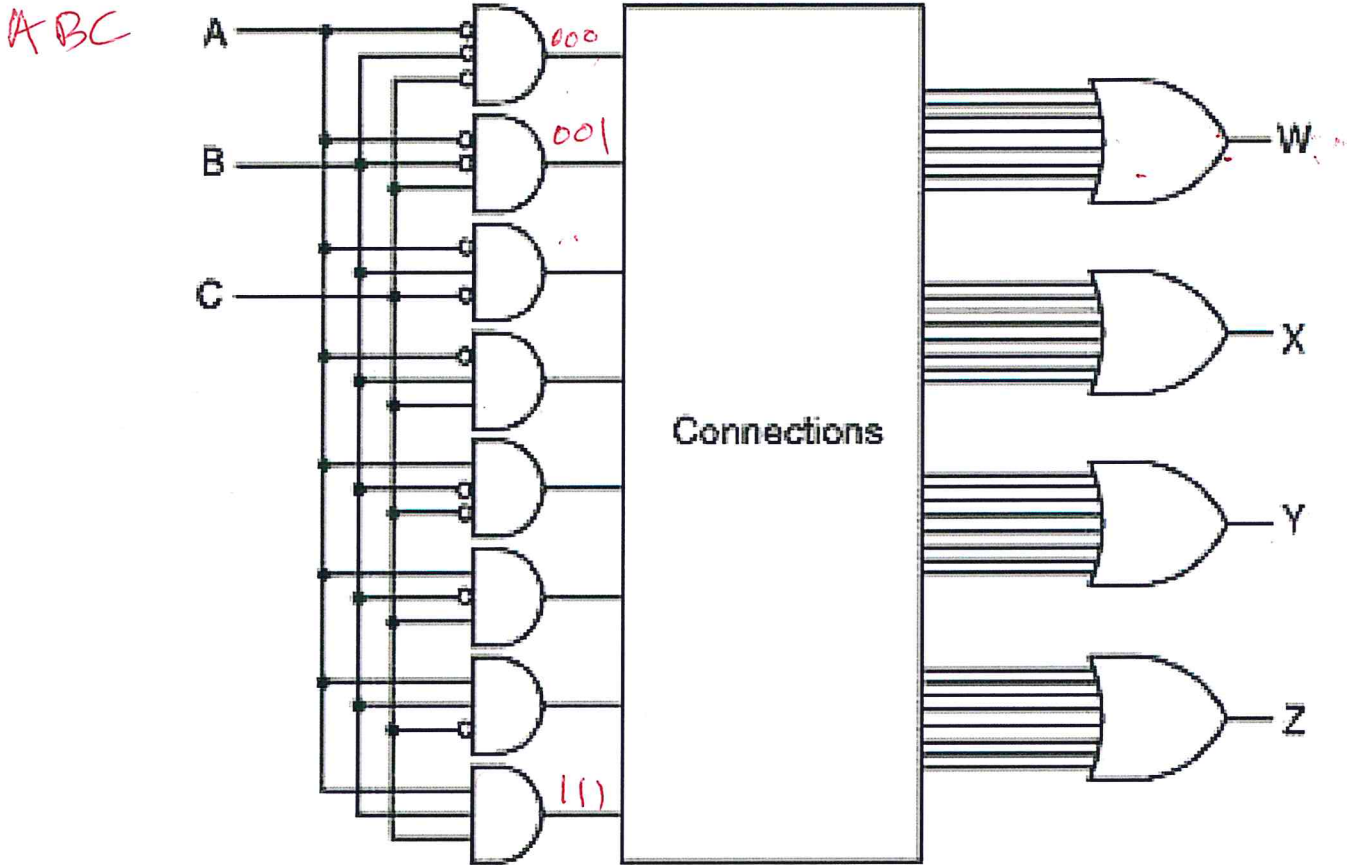

R-S Latch: Simple Storage Element

 


S	R	OUT
1	1	PREV. VAL.
0	1	1
1	0	0
0	0	<u>NA</u>

    


Gated D-Latch

Two inputs: D (data) and WE (write enable)

 
- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$



Register

 


2² x 3 Memory

 

State Machine


Another type of sequential circuit

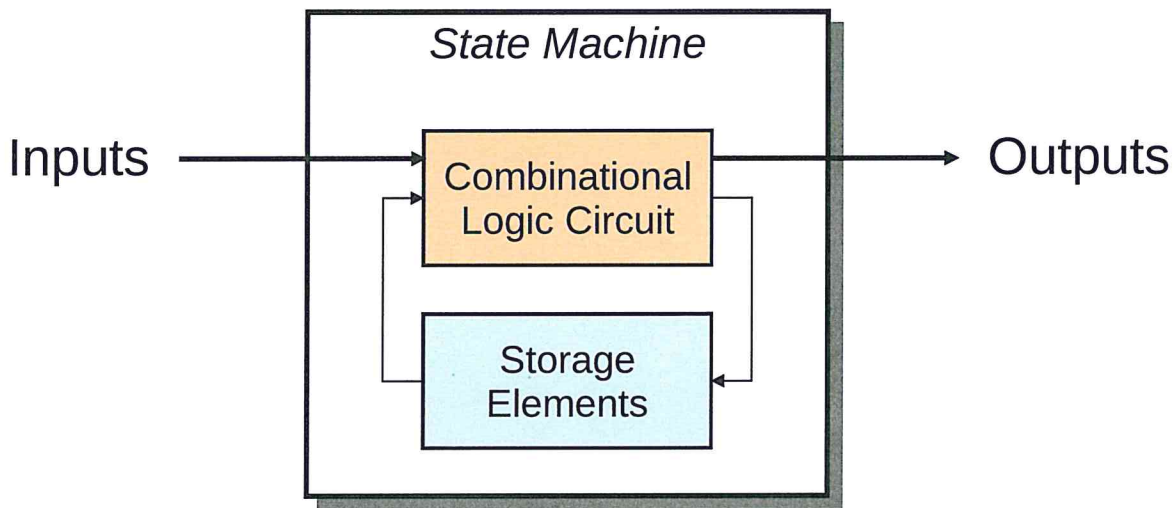- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**




State Diagram

 Shows **states** and **actions** that cause a **transition** between states.



Storage: Master-Slave Flipflop

 A pair of gated D-latches,
to isolate *next* state from *current* state.



During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

LC-3 Data Path

Combinational Logic

Storage

State Machine

