 


5. Logic Circuits, Storage Elements Sept. 17, 2018 (Chapter 3, 3.3-3.4)

- **Logic gates (cont'd)**
 - Transistor structures
 - Gate-level circuits
 - De Morgan's law
- **Combinational Logic Circuits**
 - Decoder
 - Multiplexer
 - Full Adder
 - Programmable Logic Array
- **Storage Elements**
 - R-S Latch
 - Gated D Latch
 - Register
 - Memory

NAND Gate (AND-NOT)

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0




PATH FROM
 C TO GND
 IFF A=1 AND
B=1



Note: Parallel structure on top, serial on bottom.

AND Gate

AB

 

NAND

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


Add inverter to NAND.

NOT


Basic Logic Gates




NOT

 


OR

 

NOR

 

AND

 

NAND


Truth Tables of Basic Gates

A	B	\bar{A}	\bar{B}	$A \cdot B$	$\overline{A \cdot B}$	$A + B$	$\overline{A + B}$
0	0	1	1	0	1	0	1
0	1	1	0	0	1	1	0
1	0	0	1	0	1	1	0
1	1	0	0	1	0	1	0

INSTANCE OF DE MORGAN'S LAW



Structure of CMOS Logic

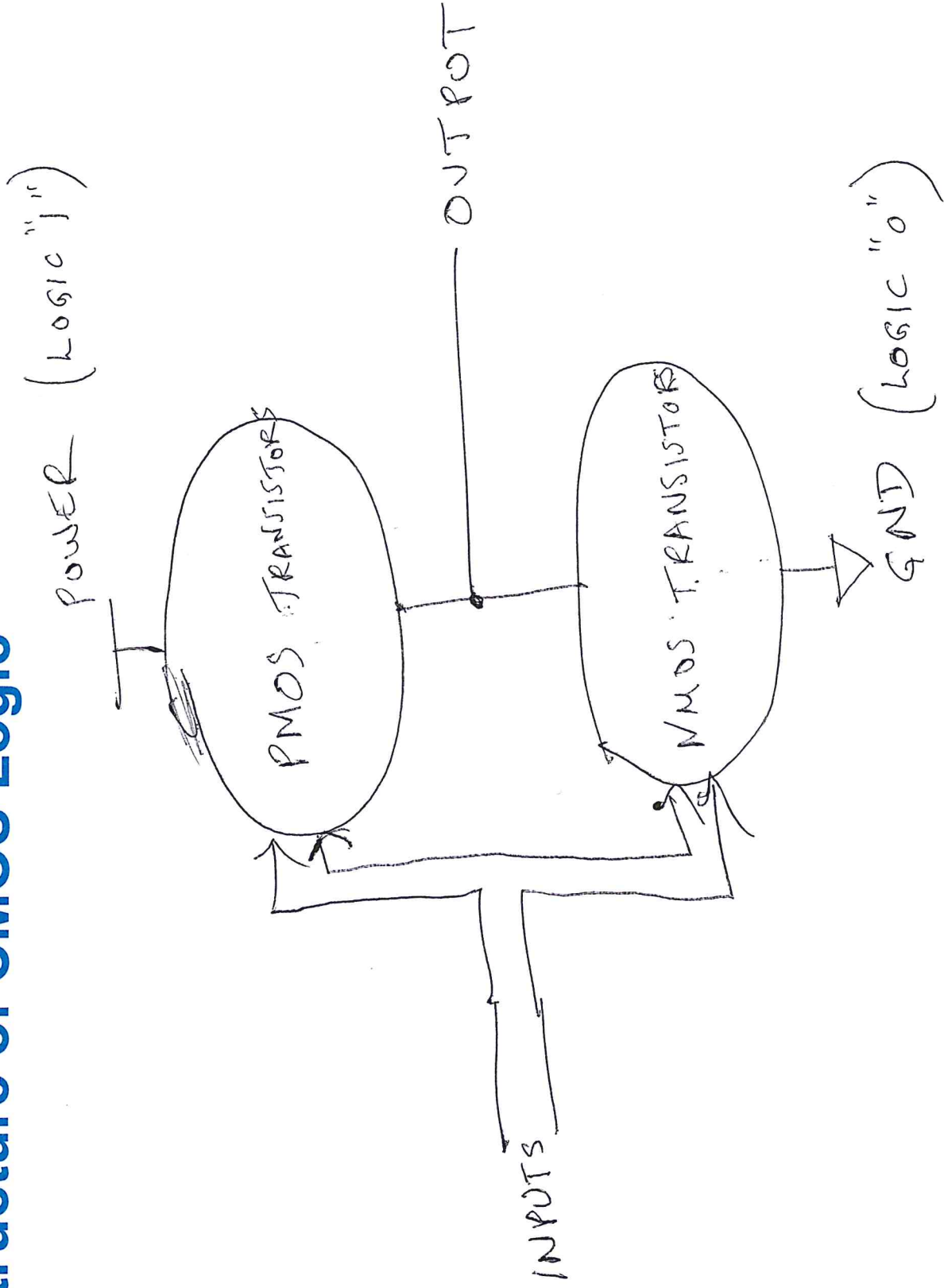

DeMorgan's Law

WHY?



CONVERT CIRCUIT BLOCKS -

AND \rightarrow OR

AND \rightarrow NAND

Converting between gate types (AND to OR, etc.) (with help from NOT)

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\overline{\bar{A} \cdot \bar{B}}$	$A + B$
0	0	1	1	1	0	0
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	0	1	1

  



$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

NOT A




MORE THAN 2 INPUTS

  

$$A \cdot B \cdot C = (A \cdot B) \cdot C$$

$$A + B + C + D = (A + B) + (C + D)$$

 

↑
NOR

↓
NAND



Logical Completeness


Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

1. AND combinations that yield a "1" in the truth table.

$$D = \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

2. OR the results of the AND gates.

 

LOGIC FUNCTIONS

1. COMBINATIONAL

OUTPUT IS A FUNCTION OF INPUTS

2. SEQUENTIAL


OUTPUT DEPENDS ON INPUT
SEQUENCE

[STORE "STATES" FROM PAST INPUTS]

Decoder

n inputs, 2^n outputs

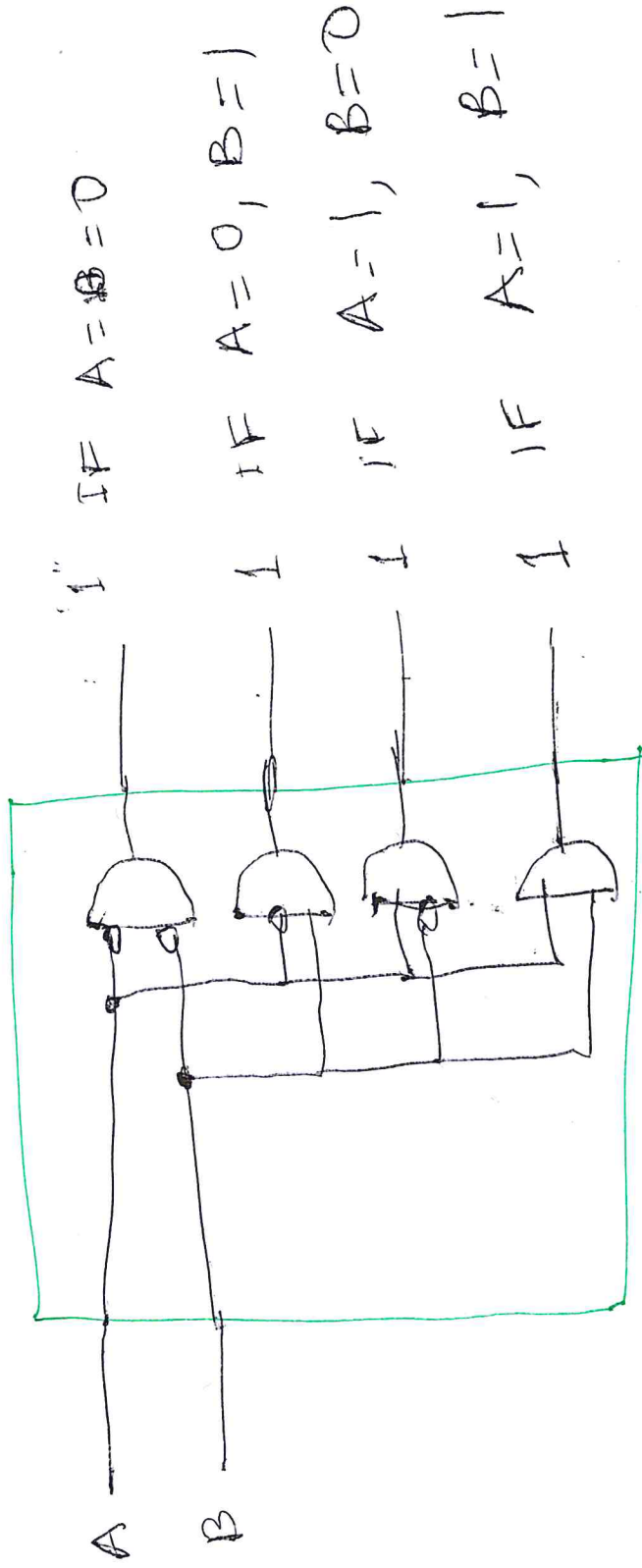- exactly one output is 1 for each possible input pattern



MULTIPLEXER (MUX)

N-BIT SELECTOR


2^n - INPUTS

1 - OUTPUT

FOR 2 BITS,

INPUT A, B

SELECT S

 


$$= \bar{S} \cdot A + S \cdot B$$

Multiplexer (MUX)


n -bit selector and 2^n inputs, one output

- output equals one of the inputs, depending on selector

4-INPUT MUX

 

XOR WITH THIS MUX

 


4-to-1 MUX

$F = D - A$


Full Adder

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Full Adder

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

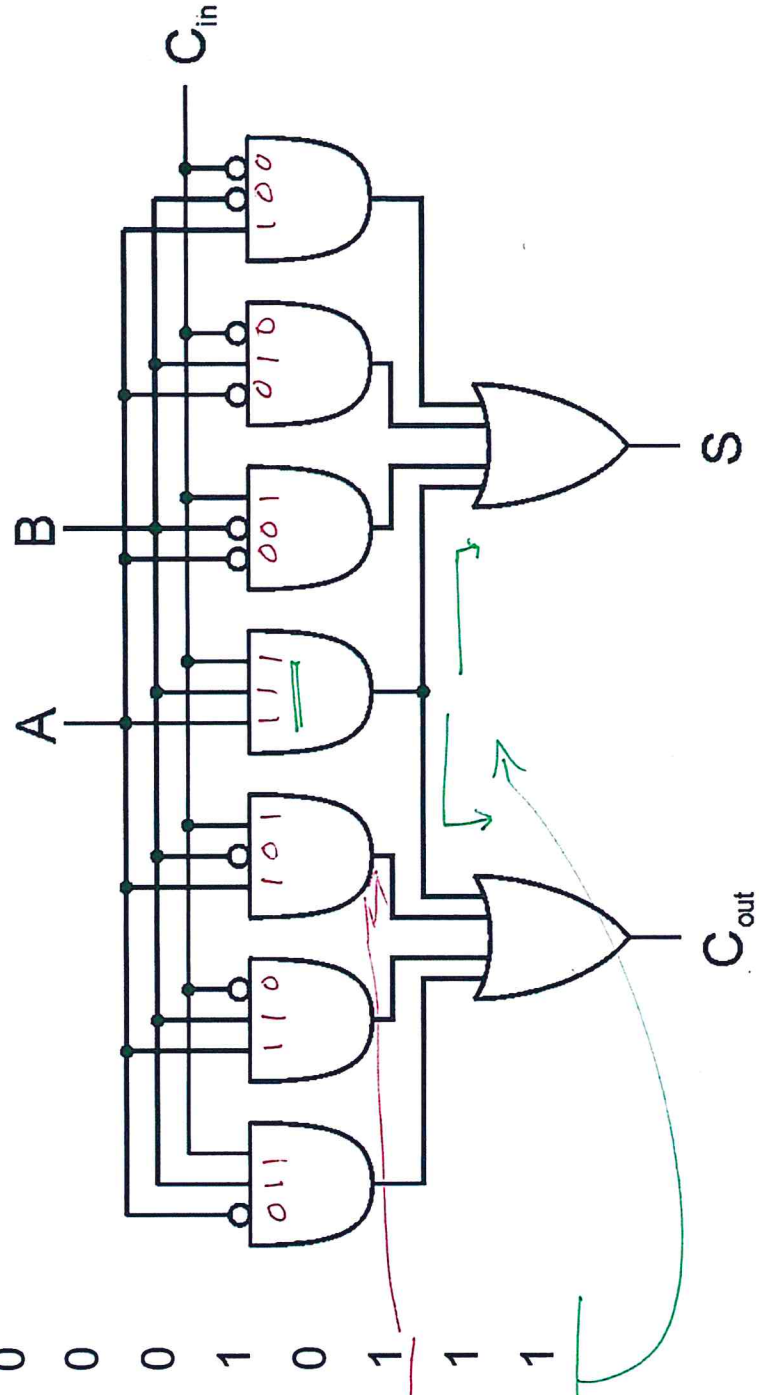


Logic Circuit for Adder

FYJ

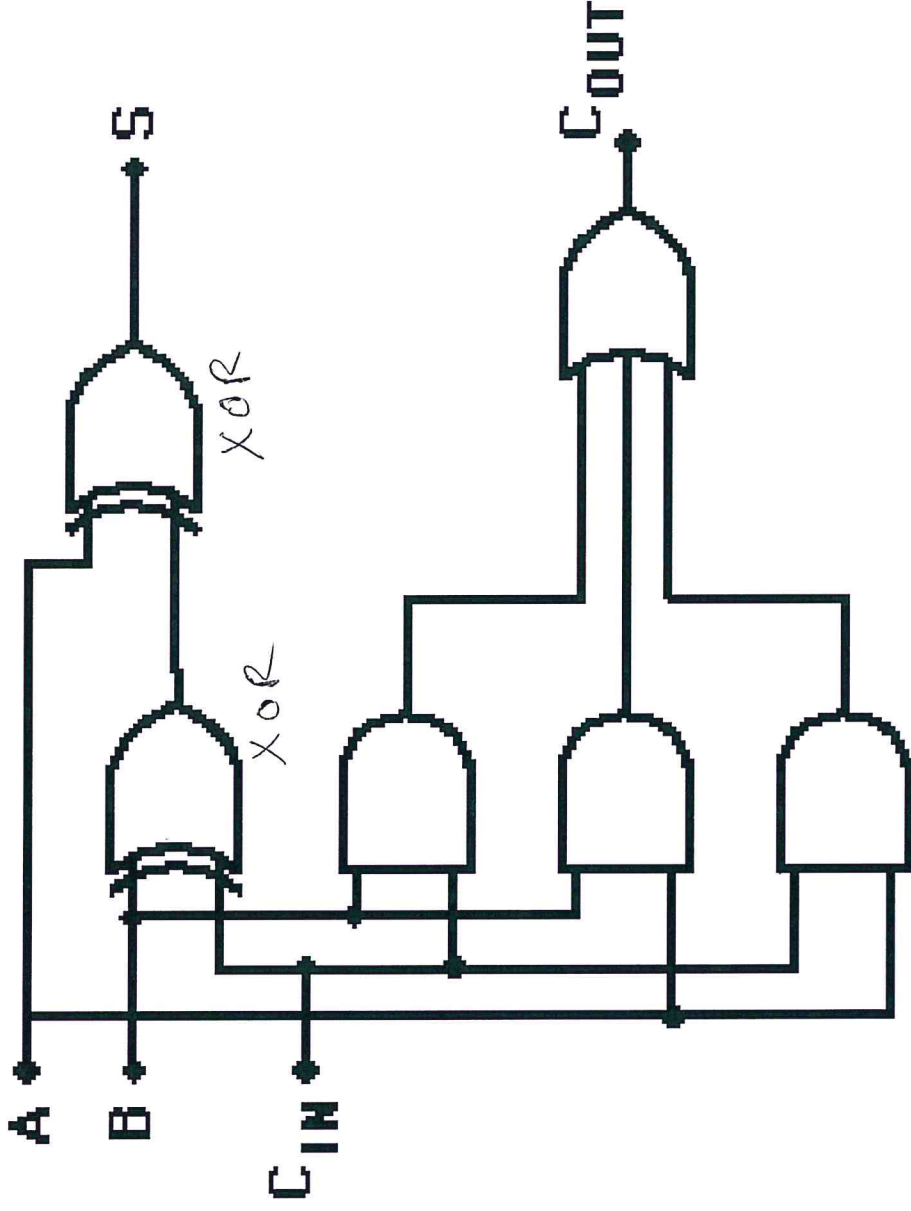


FYI

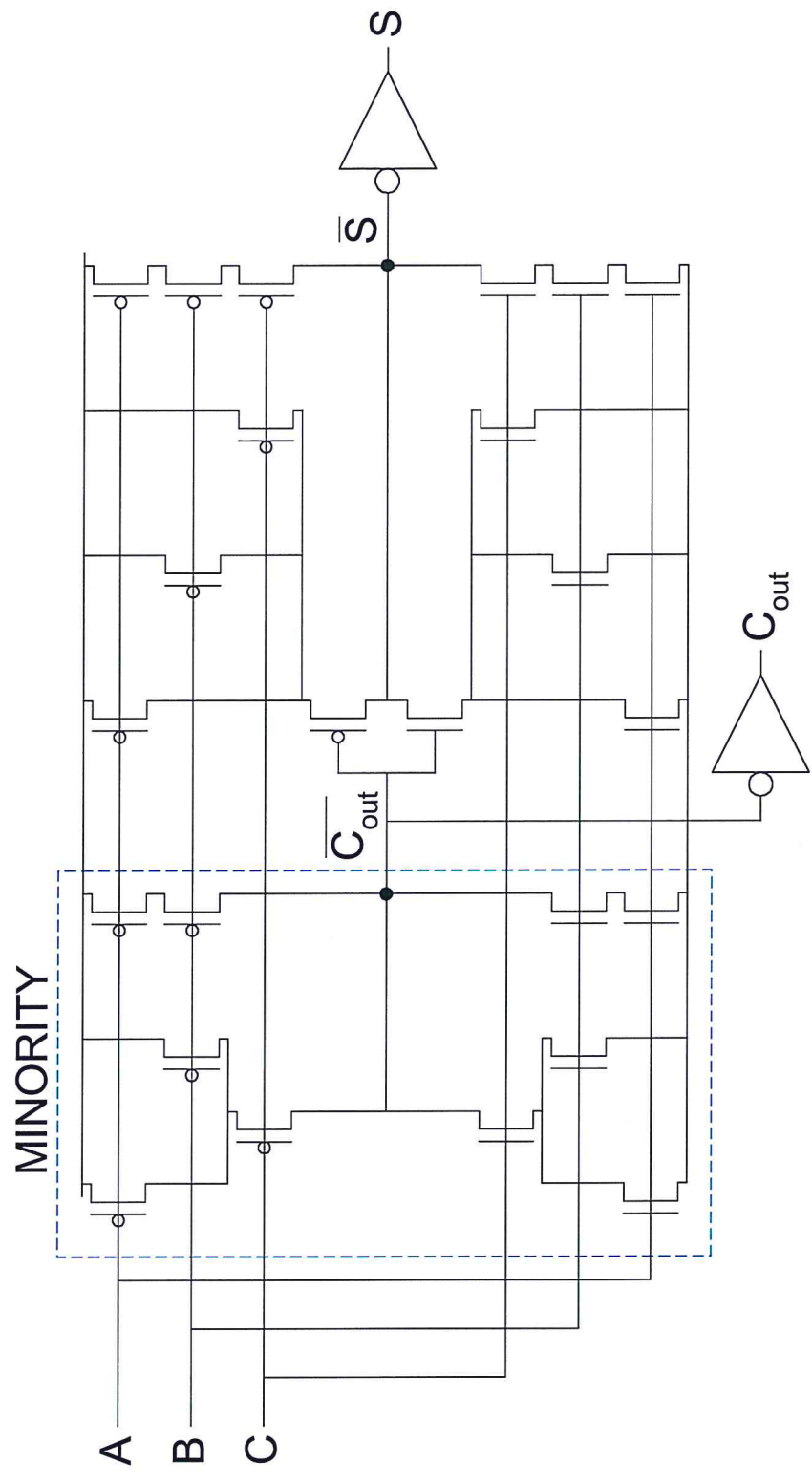More Detailed View of Adder Circuit: Transistors




Layout of Adder Cell


FYI

 

Four-bit Adder


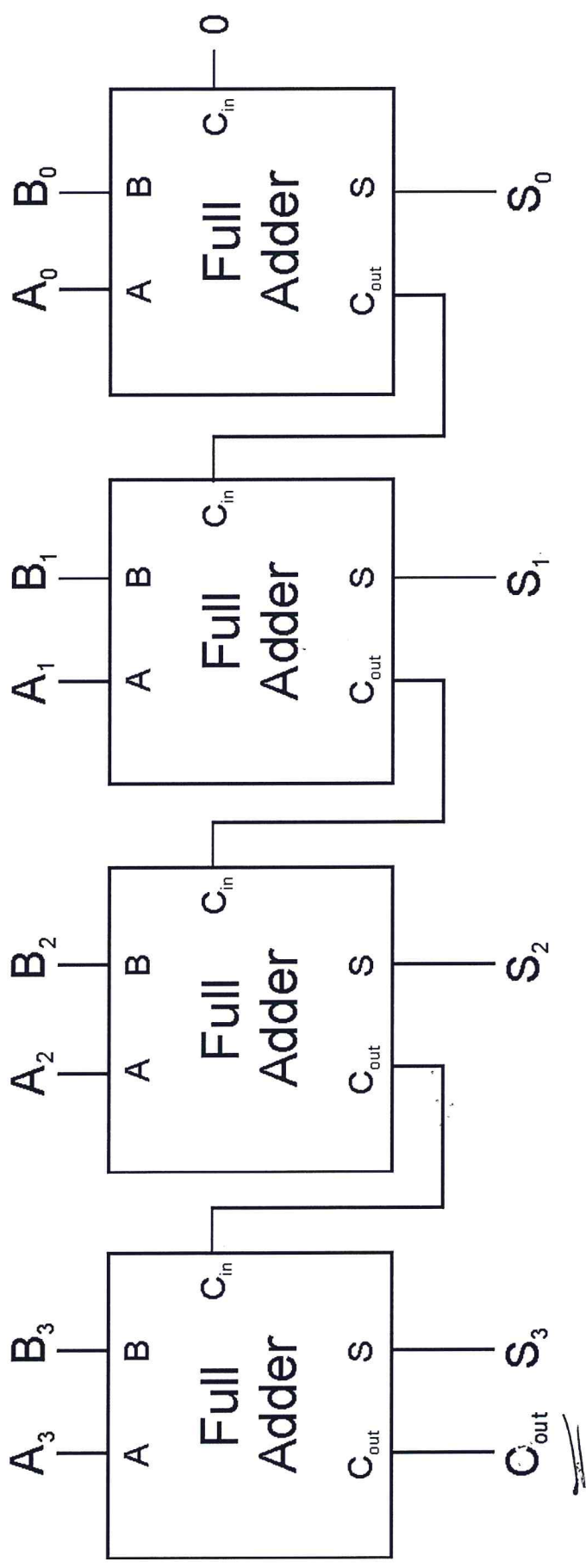


Programmable Logic Array

 

SEQUENTIAL CIRCUIT

[FOR MEMORY, STORAGE]

 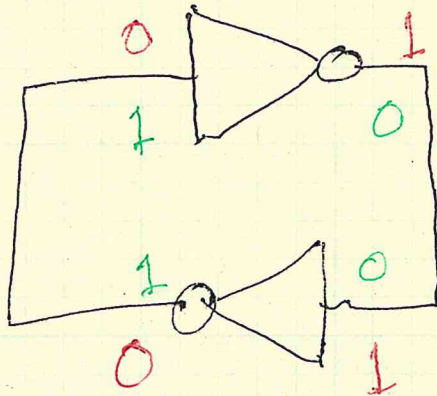

OSCILLATOR



R-S Latch: Simple Storage Element

