

# 7. The Stored-Program (von Neumann) Computer

Sept. 24, 2018  
(Chapter 4)


- **Review**
  - **Finite-State Machines**
  - **Example: design of control for a warning sign**
- **LC-3 data path**
- **The stored program computer**
  - **Interface to memory**
  - **Input/Output**
  - **Control**
  - **Example instructions**

# Review:

## Complete Example
 
### A blinking traffic sign

- A • No lights on
- B • 1 & 2 on
- C • 1, 2, 3, & 4 on
- D • 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



**A**



**B**




**C**



**D**


# Finite-State Machine (FSM) for Controller

Input: **Switch** (ON=1, or OFF=0)

 


Transition from one state to next when **Clock** becomes 1

ON EACH CLOCK CYCLE

 
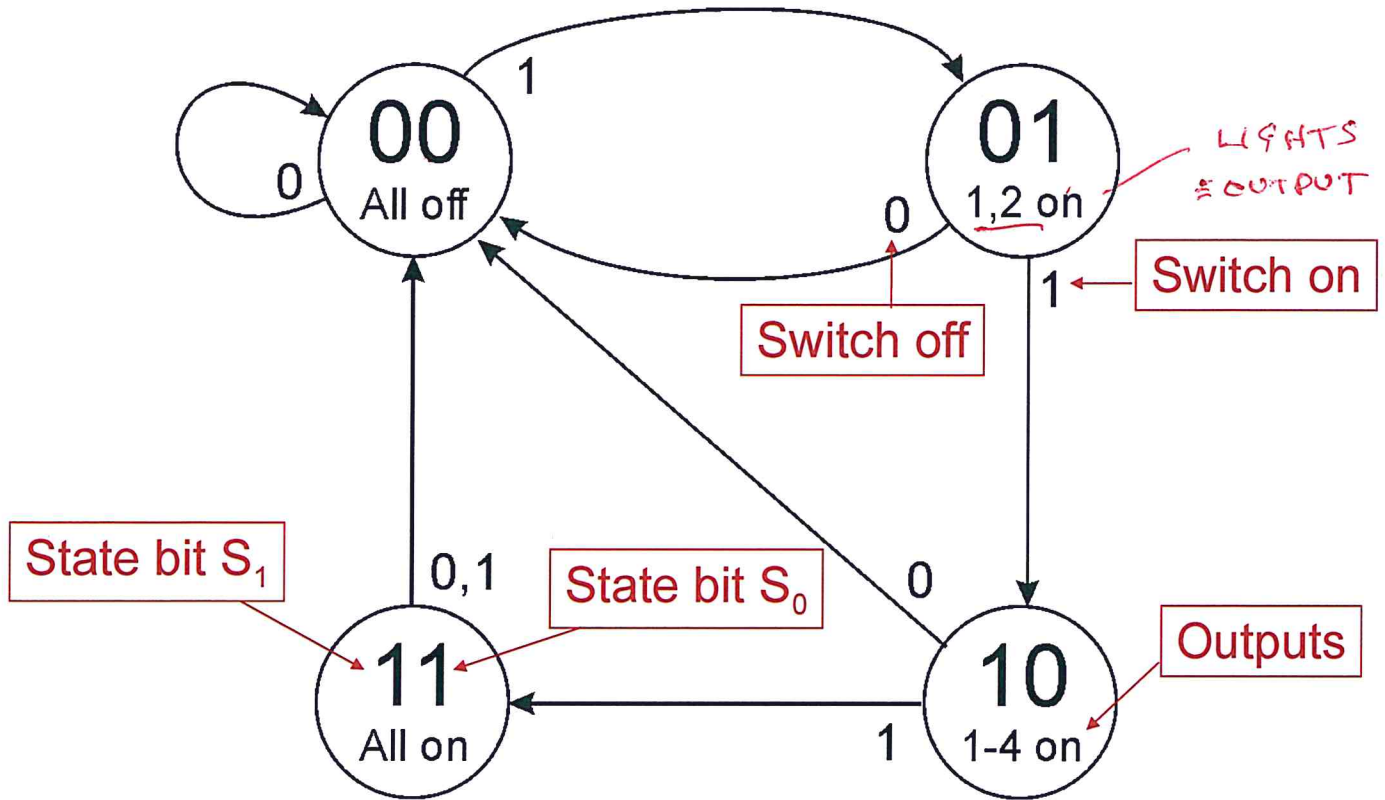
# Traffic Sign State Diagram – with assignment of storage element values to states



Transition on each clock cycle.

ANOTHER ASSIGNMENT


A: 0001


B: 0010

C: 0100

D: 1000
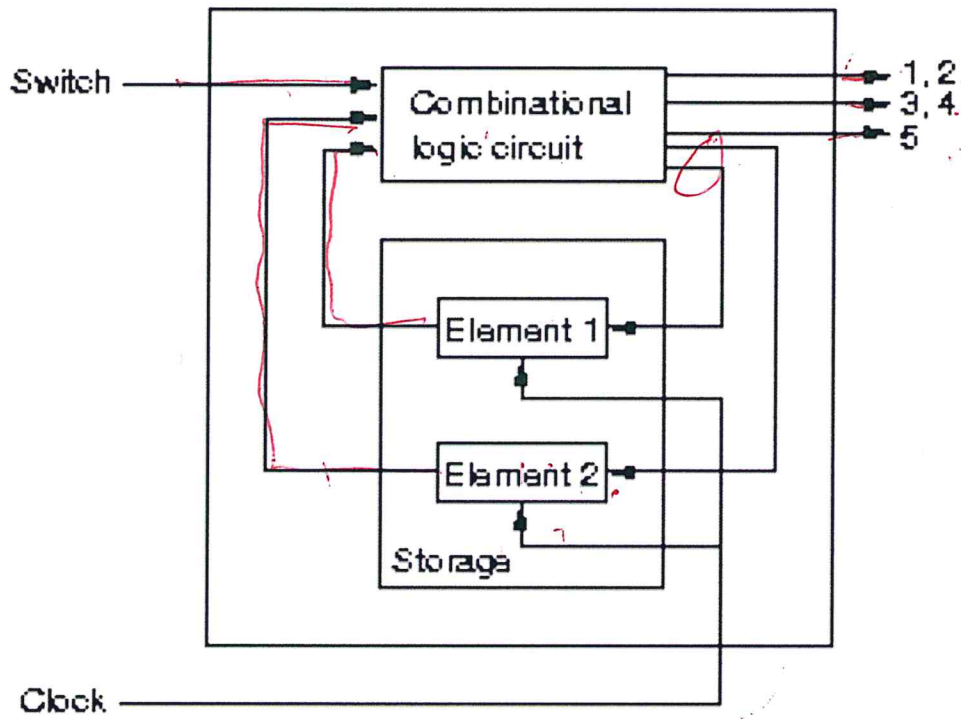
# Block Diagram of Finite-State Controller



 

## State Table for FSM

INPUTS

$S_1S_0$	SW OFF	SW ON	1,2	3,4	5
00	00	01	0	0	0
01	00	10	1	0	0
10	00	11	1	1	0
11	00	00	1	1	1

PRESENT STATE

NEXT STATE

OUTPUTS


# Truth Table for Lights

Lights 1 and 2  
Lights 3 and 4  
Light 5

$S_1$	$S_0$	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

↑

# Logic Circuit for Lights

 



## Truth Table for Next State Function


Next State:  $S_1^+ S_0^+$   
(depend on state and input)

In	$S_1$	$S_0$	$S_1^+$	$S_0^+$
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0



Whenever  $In=0$ , next state is 00.

X: "DON'T CARE"

# Logic Circuit for Next-State Function

 


# Sequencing the FSM

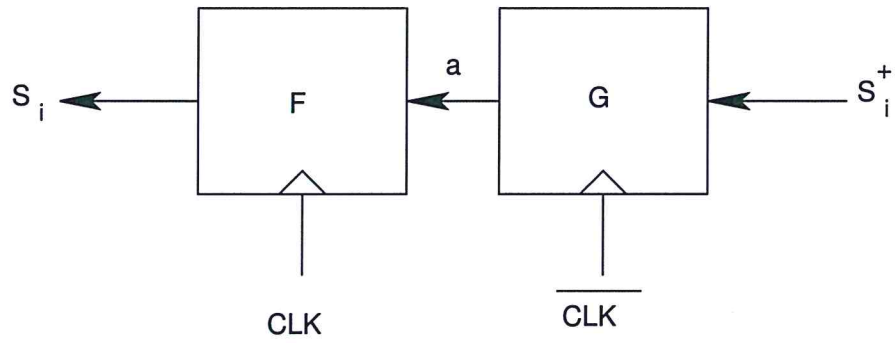 


# Clocking

# MASTER-SLAVE FF (FLIP-FLOP)

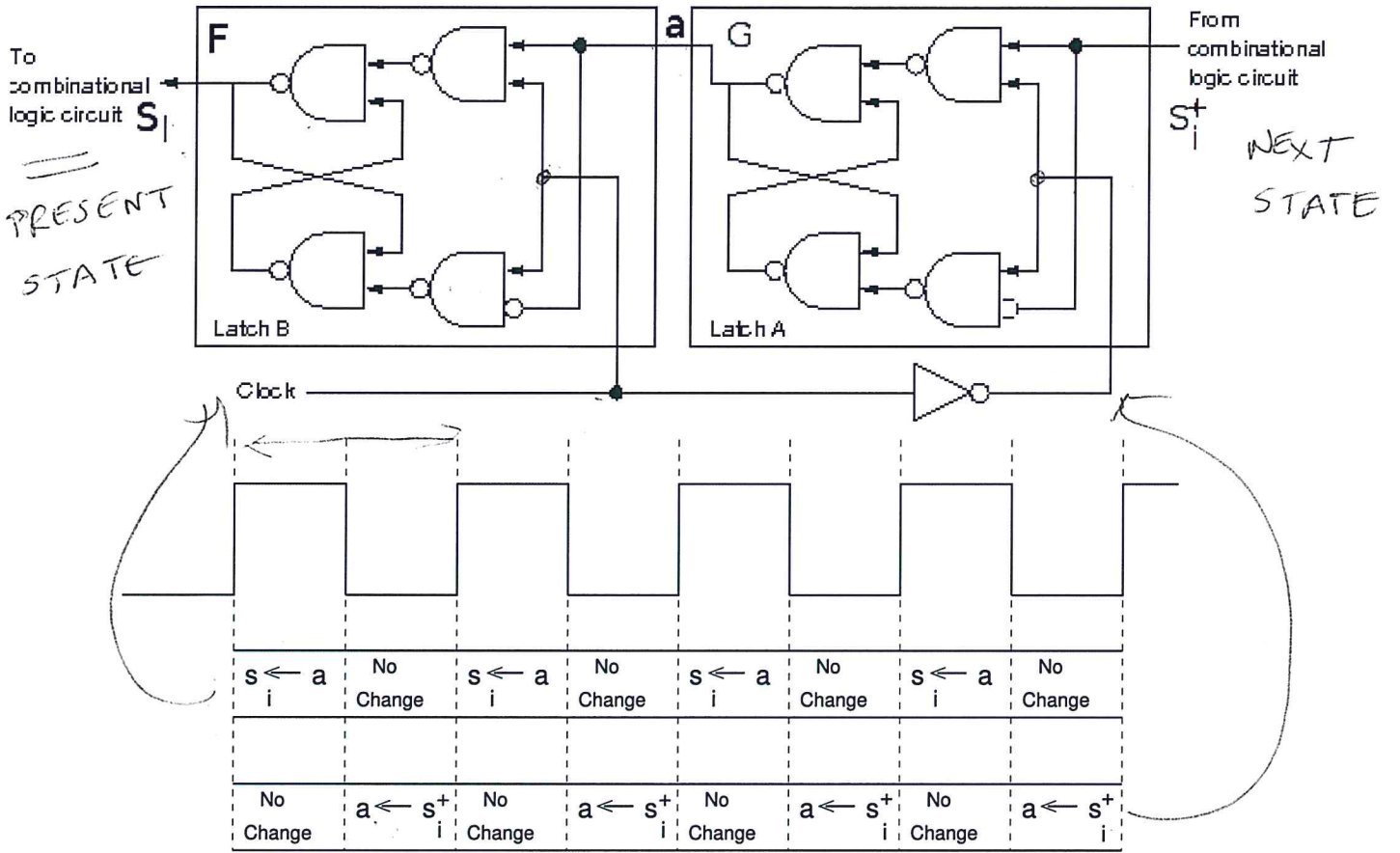

# "Simulating" the Traffic Sign Logic

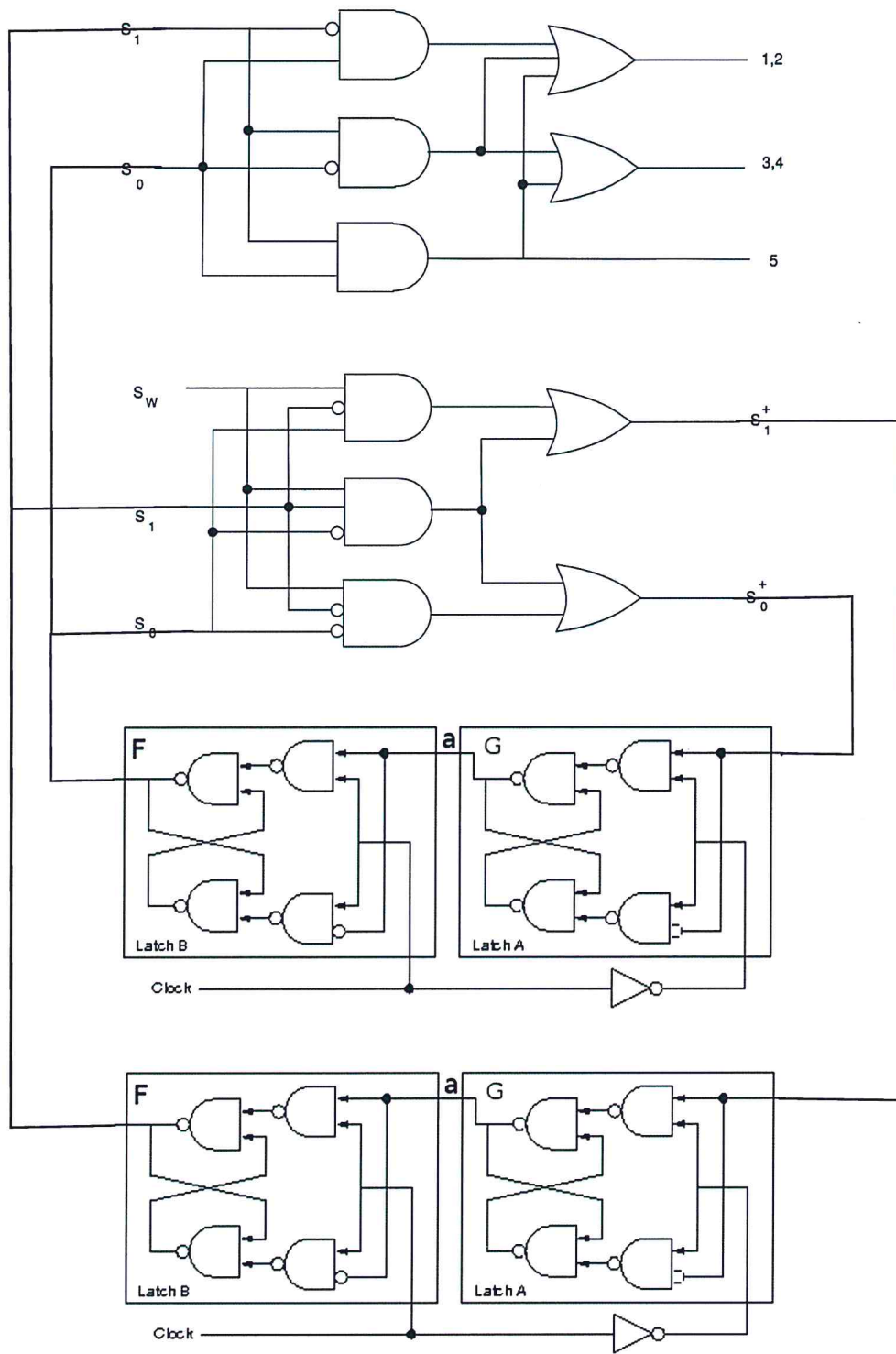

# The Stored Program Computer

## 1943: ENIAC

- Presper Eckert and John Mauchly -- first general electronic computer.  
(or was it John V. Atanasoff in 1939? – special-purpose electronic computer)
- Hard-wired program -- settings of dials and switches.

## 1944: Beginnings of EDVAC

- among other improvements, includes program stored in memory

## 1945: John von Neumann

- wrote a report on the stored program concept,  
known as the *First Draft of a Report on EDVAC*

The basic structure proposed in the draft became known as the “von Neumann machine” (or model).

- a memory, containing instructions and data
- a processing unit, for performing arithmetic and logical operations
- a control unit, for interpreting instructions


For more history, see <http://www.computerhistory.org/>

# LC-3 Data Path


Combinational Logic

Storage

State Machine

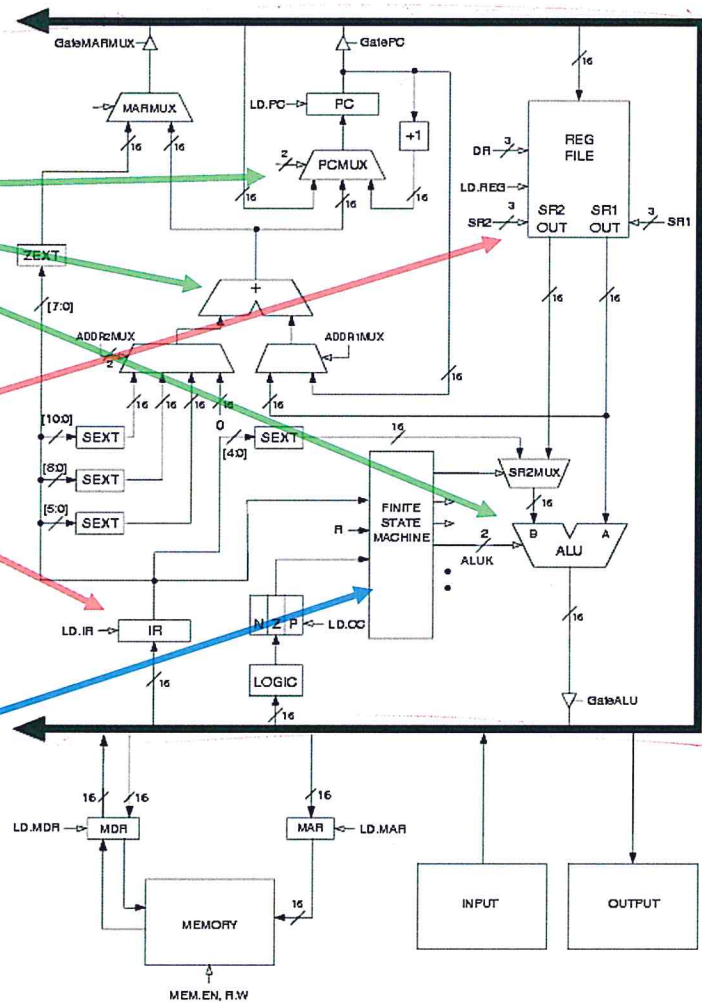

# Von Neumann Model

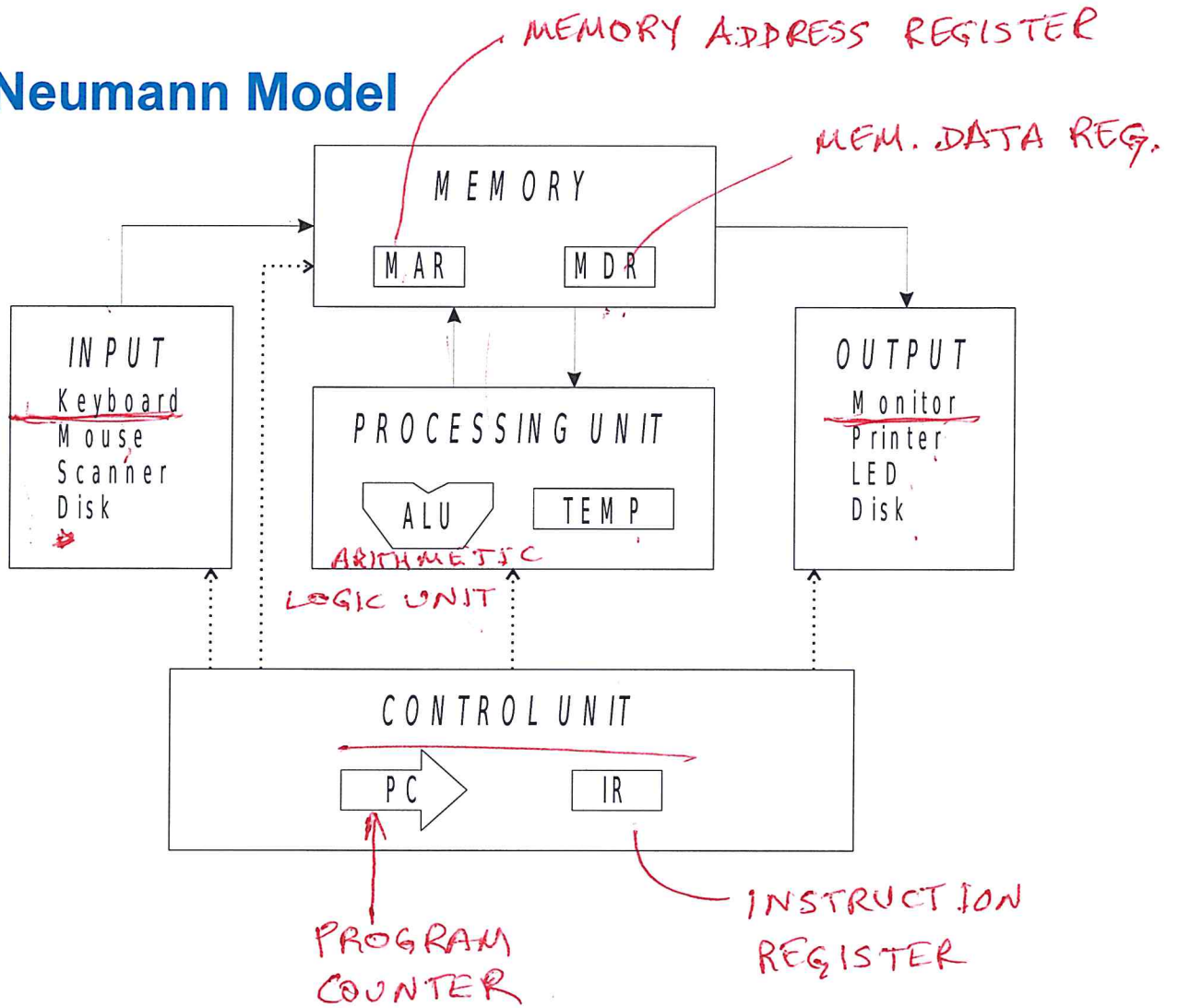




# Memory

## ARRAY

$2^4$  WORDS X 8 BITS


ADDRESS: 4 BITS

CONTENTS (DATA) = 8 BITS

 
 
## OPERATIONS

LOAD : PUT ADDRESS IN MAR  
(READ) SEND A "READ" COMMAND  
GET DATA FROM MDR



STORE  
(WRITE)

WRITE DATA INTO MDR  
PUT ADDRESS INTO MAR  
SEND A "WRITE" SIGNAL TO  
MEMORY

# PROCESSING UNIT

## FUNCTION UNITS

↳ ALU

LC3: ADD

AND, NOT

## REGISTERS

LC3: TEMP STORAGE (16 BIT)

8 REGISTERS, 16 BITS

$R_7, \dots, R_0$

I/O

LC3: KEYBOARD INPUT

KBDR  
(DATA)

KBSR  
(STATUS)

## MONITOR OUTPUT

DDR

DSR

("DISPLAY")

# CONTROL

IR - INST. REG.

PC - PROG. COUNTER


NEXT INSTRUCTION:

→ ADDRESS IS IN PC

→ EXECUTES INSTR. AT THAT  
ADDRESS

⇒ MANY CYCLES

# Instruction Processing

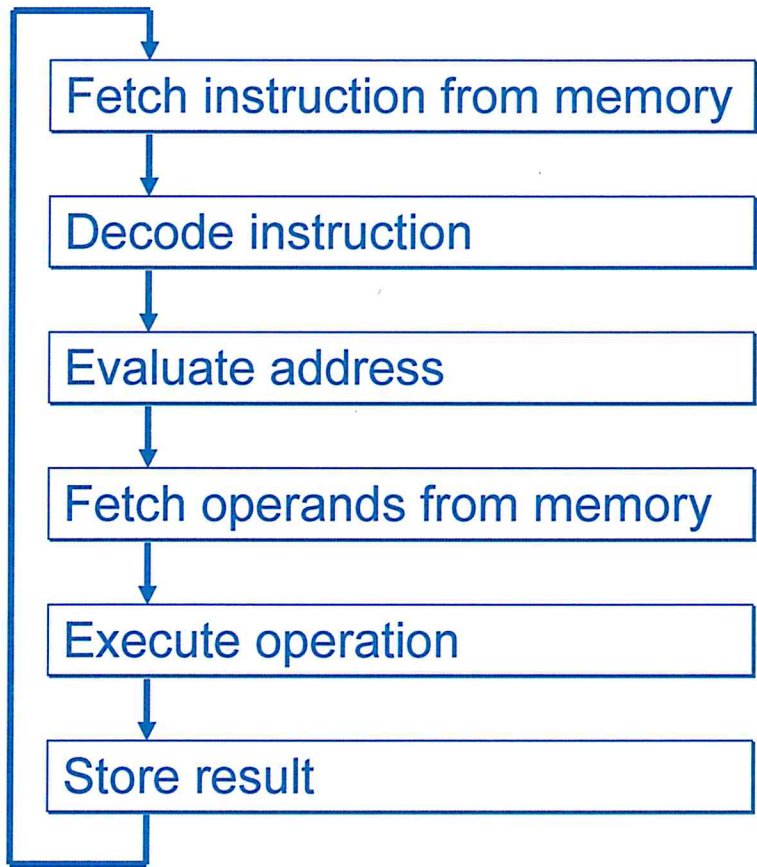

ADDR: IN PC

# Instruction Processing: FETCH

DATA IN

LOAD ADDRESS POINTED TO BY PC.

INTO IR.

- 
- $MAR \leftarrow (PC)$
  - SEND "READ" TO MEMORY
  - COPY CONTENTS INTO IR  
 $IR \leftarrow (MDR)$
  - $PC \leftarrow PC + 1$

