

10. Interconnects in CMOS Technology

Jacob Abraham

Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020


September 29, 2020

Introduction to Wires on a Chip


Most of chip is wires (interconnect)

- Most of the chip is covered by wires, many layers of wires
- Transistors: little things under wires
- Wires as important as transistors
 - Affect
 - Speed
 - Power
 - Noise
- Alternating layers usually run orthogonally

Intel Damascene copper

 


IBM air gap between Cu

 




 

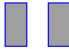
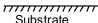
Wire Geometry

- Pitch = $w + s$
- Aspect Ratio, $AR = t/w$
 - Old processes had $AR \ll 1$
 - Modern processes have $AR \approx 2$ to pack in many skinny wires



Layer Stack

- Number of metal layers has been increasing
 - AMI 0.6 μm process has 3 metal layers
 - Modern processes use 6-10+ metal layers
- Example: Intel 180 nm process
 - M1: thin, narrow ($< 3\lambda$)
 - High density cells
 - M2-M4: thicker
 - For longer wires
 - M5-M6: thickest
 - For V_{DD} , GND, CLK


Layer	T (nm)	W (nm)	S (nm)	AR	
6	1720	860	860	2.0	
	1000				
5	1600	800	800	2.0	
	1000				
4	1080	540	540	2.0	
	700				
3	700	320	320	2.2	
	700				
2	700	320	320	2.2	
	700				
1	480	250	250	1.9	
	800				
					 Substrate

Wire Resistance

$\rho = \text{resistivity } (\Omega * m)$

$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

 - $R_{\square} = \text{sheet resistance } (\Omega/\square)$
 - \square is a dimensionless unit
- Count number of squares
 - $R = R_{\square} * (\# \text{ of squares})$



Choice of Metals

- Until the 180 nm generation, most wires were aluminum
- Modern processes often use copper
 - Cu atoms diffuse into silicon and damage FETs
 - Must be surrounded by a diffusion barrier

Metal	Bulk Resistivity ($\mu\Omega * cm$)
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3

Sheet Resistance

Typical sheet resistances in 180 nm process

Layer	Sheet Resistance (Ω/\square)
Diffusion (silicided)	3–10
Diffusion (no silicide)	50–200
Polysilicon (silicided)	3–10
Polysilicon (no silicide)	50–400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02


Contact Resistance

- Contacts and vias also have 2-20 Ω resistance
- Use many contacts for lower R
 - Many small contacts for current crowding around periphery
- Multiple contacts also help improve the yield (failure or high resistance of a contact will have only a small effect on the overall resistivity)




Wire Capacitance

 - Wire has capacitance per unit length
 - To neighbors
 - To layers above and below
- $C_{total} = C_{top} + C_{bot} + 2C_{adj}$




Capacitance Trends

- Parallel plate equation: $C = \epsilon A/d$
 - Wires are not parallel plates, but obey trends
 - Increasing area (W , t) increases capacitance
 - Increasing distance (s , h) decreases capacitance
- Dielectric Constant
 - $\epsilon = k\epsilon_0$
- $\epsilon_0 = 8.85 \times 10^{-14} \text{ F/cm}$
- $k = 3.9$ for SiO_2
- Processes are starting to use low-k dielectrics
 - $k \approx 3$ (or less) as dielectrics use air pockets

 

 
- $W \gg H \Rightarrow$ Parallel Plate Model
 - $C = k \cdot \epsilon_0 \cdot \frac{W \cdot L}{H}$
- $W \leq H \Rightarrow$ Fringing Model
 - $C \propto \log(W)$
- For Deep Sub-Micron (DSM) (or nanoscale) processes, fringing model applies



- $T \gg W \Rightarrow$ Parallel Plate Model
 - $C = k \cdot \epsilon_0 \cdot \frac{T \cdot L}{W}$
- $T \leq W \Rightarrow$ Fringing Model
 - $C \propto \log(T)$
- For DSM processes, parallel plate model applies

M2 Capacitance Data

 - Typical wires have $\approx 0.2 \text{ fF}/\mu\text{m}$
 - Compare to $2 \text{ fF}/\mu\text{m}$ for gate capacitance




Diffusion and Polysilicon

- Diffusion capacitance is very high (about $2\text{ fF}/\mu\text{m}$)
 - Comparable to gate capacitance
 - Diffusion also has high resistance
 - Avoid using diffusion *runners* for wires!
- Polysilicon has lower C but high R
 - Use for transistor gates
 - Occasionally for very short wires between gates

Lumped Element Models

 - Wires are a distributed system
 - Approximate with lumped element models




- 3-segment π -model accurate to 3% in simulation
- L-model needs 100 segments for same accuracy!
- Use single segment π -model for Elmore delay

When to use Lumped versus Distributed Models

- First find the total R and total C for the wire.
 - If $RC \gg t_r$ (or t_f) of driver then use distributed (Π or T) model
 - If $RC \leq t_r$ (or t_f) of driver then use lumped (L) model
- It is safe to use distributed model always, but this results in more circuit elements and larger simulation times.
- To find number of distributed elements to use
 - Increase the number of elements, and stop when the error between k and $k + 1$ elements is acceptably small.
- Distributed RC delay is about half that of lumped RC
- This can be validated by using the Elmore model for the distributed wire (see previous slide)
- Rule of Thumb: for a distributed wire, propagation delay can be estimated as $\sim RC/2$.

 
Example

- Metal2 wire in 180 nm process
 - 5 mm long
 - $0.32\text{ }\mu\text{m}$ wide
- Construct a 3-segment π -model
 - $R_{\square} = 0.05\text{ }\Omega/\square \implies R = 781\text{ }\Omega$
 - $C_{\text{permicron}} = 0.2\text{ fF}/\mu\text{m} \implies C = 1\text{ pF}$



Wire RC Delay

 - Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example
 - $R = 2.5 \text{ k}\Omega * \mu\text{m}$ for gates
 - Unit inverter: $0.36 \mu\text{m}$ nMOS, $0.72 \mu\text{m}$ pMOS




- $t_{pd} = 1.1 \text{ ns}$

- A capacitor does not like to change its voltage instantaneously
- A wire has high capacitance to its neighbor
 - When the neighbor switches from $1 \rightarrow 0$ or $0 \rightarrow 1$, the wire tends to switch too
 - Called capacitive **coupling** or **crosstalk**
- Crosstalk effects
 - **Noise** on nonswitching wires
 - Increased **delay** on switching wires

Crosstalk Delay

 - Assume layers above and below on average are quiet
 - Second terminal of capacitor can be ignored
 - Model as $C_{gnd} = C_{top} + C_{bot}$
- Effective C_{adj} depends on behavior of neighbors
 - Miller Effect**




B	ΔV	$C_{eff(A)}$	MCF
Constant	V_{DD}	$C_{gnd} + C_{adj}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{DD}$	$C_{gnd} + 2C_{adj}$	2

Crosstalk Noise


- Crosstalk causes noise on nonswitching wires
- If victim is floating:
 - model as capacitive voltage divider
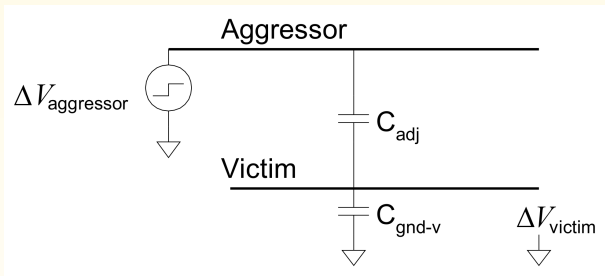
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$



Driven Victims

 - Usually victim is driven by a gate that fights noise
 - Noise depends on relative resistances
 - Victim driver is in linear region, aggressor in saturation
 - If sizes are same, $R_{aggressor} = 2 - 4 \times R_{victim}$




$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \frac{1}{1+k} \Delta V_{aggressor}$$

$$k = \frac{\tau_{aggressor}}{\tau_{victim}} = \frac{R_{aggressor}(C_{gnd-a} + C_{adj})}{R_{victim}(C_{gnd-v} + C_{adj})}$$

Coupling Waveforms

 Simulated Coupling for $C_{adj} = C_{victim}$





Noise Implications

- So what if we have noise?
- If the noise is less than the noise margin, nothing happens
- Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - But glitches cause extra delay
 - Also cause extra power from false transitions
- Dynamic logic never recovers from glitches
- Memories and other sensitive circuits also can produce the wrong answer


Goal: achieve delay, area, power goals with acceptable noise

  - Degrees of freedom
 - Width
 - Spacing
 - Layer
 - Shielding




Repeaters

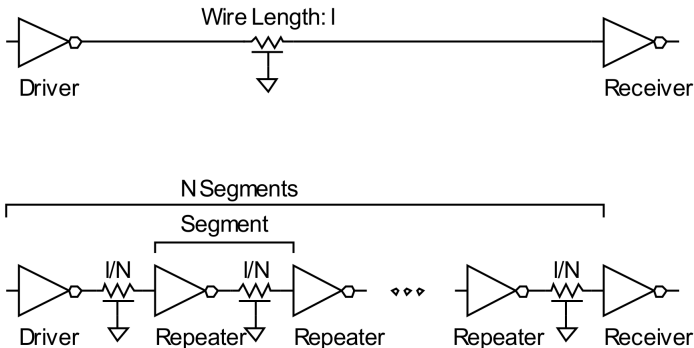- R and C are proportional to l
- RC delay is proportional to l^2
 - Unacceptably great for long wires
- Break long wires into N shorter segments
 - Drive each one with an inverter or buffer



Repeater Design

 - How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit
 - Wire length l
 - Wire Capacitance $C_w * l$, Resistance $R_w * l$
 - Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C' * W$, Resistance R/W



Repeater Results

- Write equation for Elmore Delay
 - Differentiate with respect to W and N
 - Set equal to 0, solve


$$\frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}}$$

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC' R_w C_w}$$

~ 60–80 ps/mm in 0.18 μ process

$$W = \sqrt{\frac{RC_w}{R_w C'}}$$

Clock Distribution

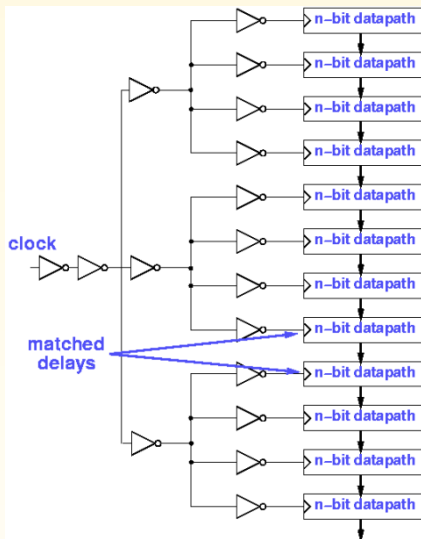


High peak currents to
drive typical clock loads
(≈ 1000 pF)

$$I_{peak} = C \frac{dV}{dt}$$

$$P_d = CV_{DD}^2 f$$

H-Trees

 


Matching Delays in Clock Distribution

- Balance delays of paths
- Match buffer and wire delays to minimize skew
- Issues
 - Load of latch (driven by clock) is data-dependent (capacitance depends on source voltage)
 - Process variations
 - IR drops and temperature variations
- Tools to support clock tree design


Clocking in the Itanium Processor

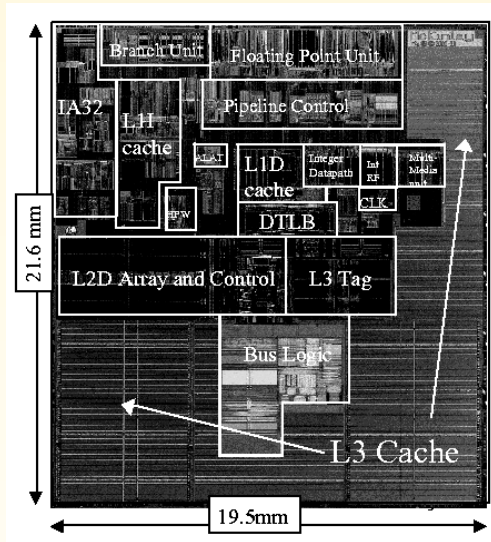- 0.18 μ technology
- 1GHz core clock
- 200 MHz system clk
- Core clocking
 - 260 mm^2
 - 1 primary driver
 - 5 repeaters
 - 157,000 clocked latches




Source for the slides on Itanium: Intel/HP

Clock Generation

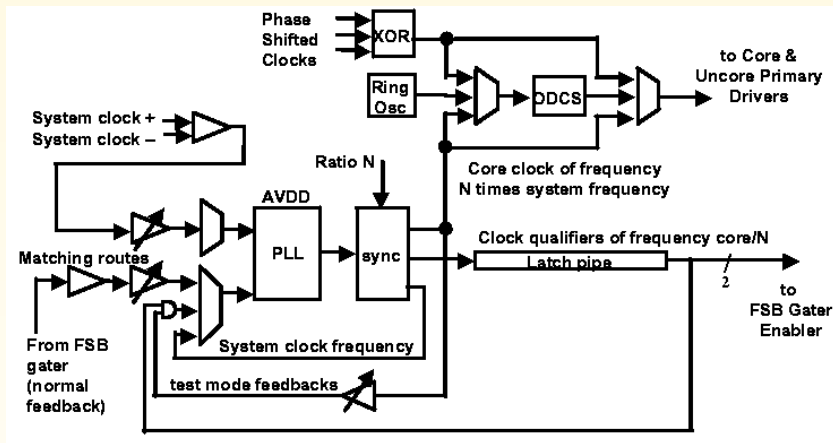


Core Clock Distribution

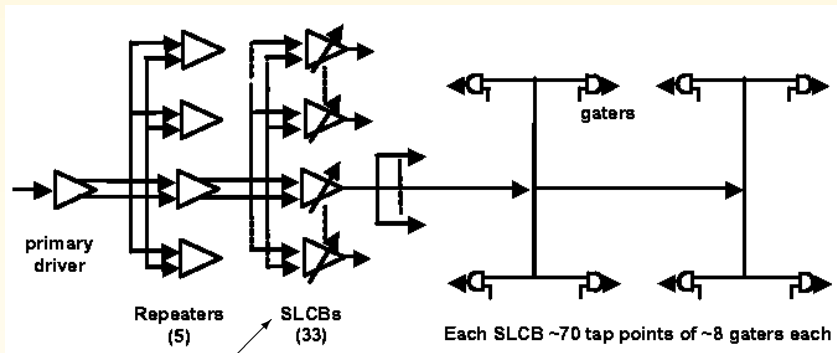


Second Level Clock Buffer (SLCB)

SLCB Schematic

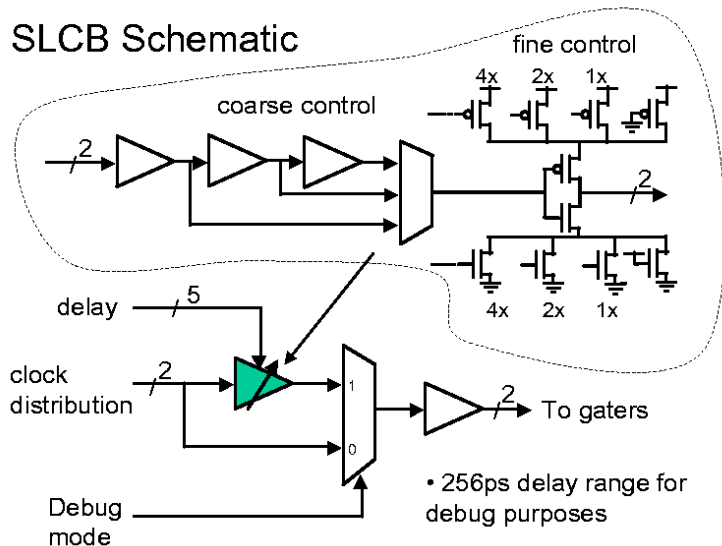

First Level Route Geometry

 

Measured Skew

