

### 3. Implementing Logic in CMOS

Jacob Abraham

Department of Electrical and Computer Engineering  
The University of Texas at Austin

VLSI Design  
Fall 2020

September 3, 2020

ECE Department, University of Texas at Austin


Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 1 / 37

### Static CMOS Circuits
 
#### N- and P-channel Networks

- N- and P-channel networks implement logic functions
  - Each network connected between **Output** and  $V_{DD}$  or  $V_{SS}$
  - Function defines path between the terminals



ECE Department, University of Texas at Austin


Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 1 / 37
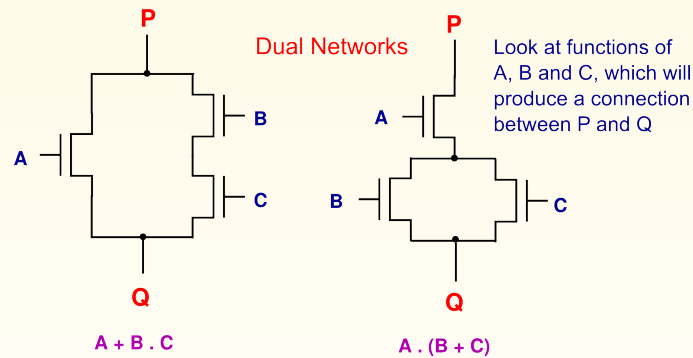
## Duality in CMOS Networks

Straightforward way of constructing static CMOS circuits is to implement dual N- and P- networks


- N- and P- networks must implement **complementary** functions
- Duality **sufficient** for correct operation (but not necessary)



## Constructing Complex Gates


 
Example:  $F = \overline{(A \cdot B) + (C \cdot D)}$

- 1 Take uninverted function  $F = (A \cdot B) + (C \cdot D)$  and derive N-network
- 2 Identify *AND*, *OR* components: F is *OR* of AB, CD
- 3 Make connections of transistors


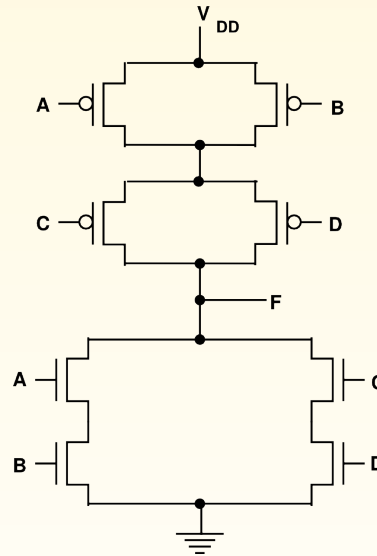 
## Construction of Complex Gates, Cont'd

- 4 Construct P-network by taking complement of N-expression ( $AB + CD$ ), which gives the expression,  $(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})$
- 5 Combine P and N circuits




ECE Department, University of Texas at Austin


Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 4 / 37

## Layout of Complex Gate

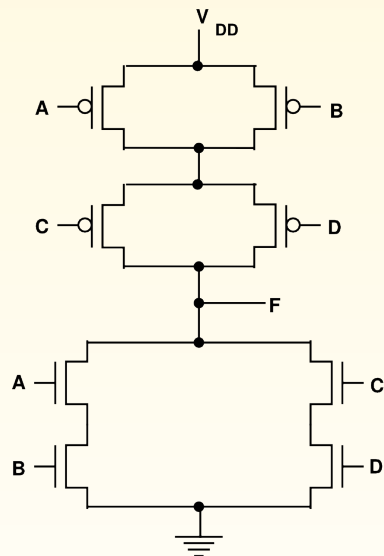

AND-OR-INVERT (AOI) gate

 

Note: Arbitrary shapes are not allowed in some nanoscale design rules

ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 5 / 37

## Example of Compound Gate

$$F = \overline{(A + B + C) \cdot D}$$


Note:

N- and P- graphs are duals of each other

In this case, the function is the complement of the switching function between F and GND

Question: Does it make any difference to the function if the transistor with input D is connected between the parallel A, B, C, transistors and GND?

What about the electrical behavior?

 


ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020

6 / 37

## Example of More Complex Gate

 

$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$


ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020

7 / 37

### Example of More Complex Gate

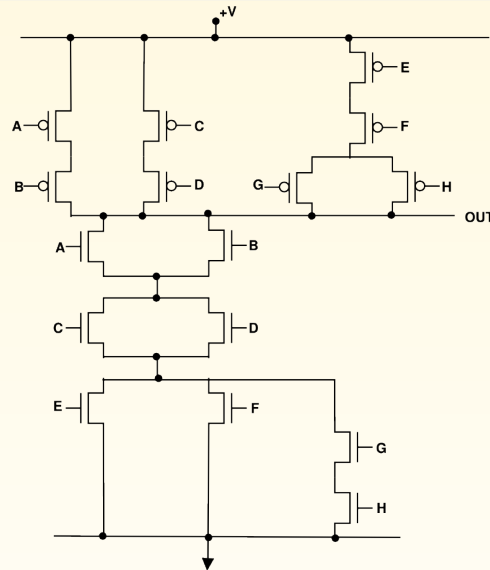

$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$


ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020

7 / 37

### Exclusive-NOR Gate in CMOS

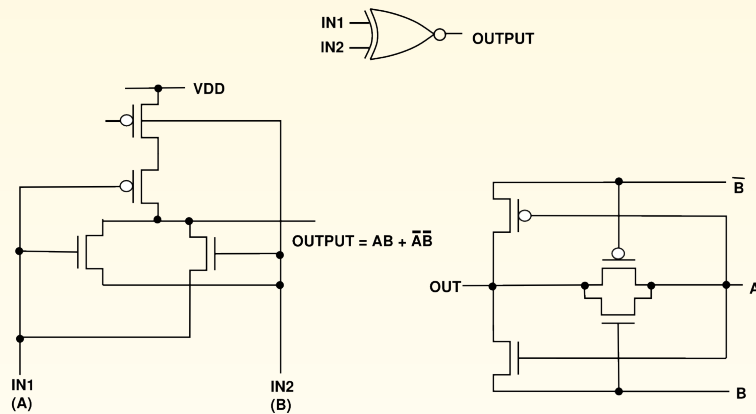

Note: designs such as these should be checked very carefully for correct behavior using circuit simulation

ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020


8 / 37

## Pseudo nMOS Logic

Based on the old NMOS technology where a “depletion” transistor was used as a pullup resistor


What happens when there is no path from Z to ground (i.e.,  $Z = 1$ )?

 What happens when there is a path from Z to ground (i.e.,  $Z = 0$ )?


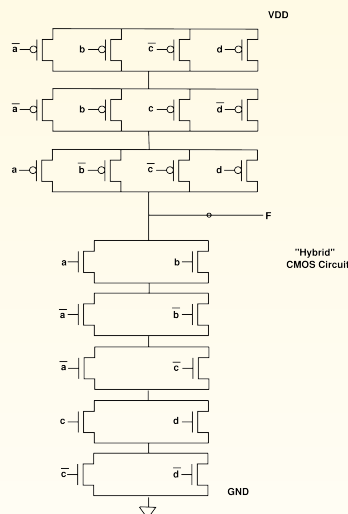
## Duality is Not Necessary for a CMOS Structure

Functions realized by N and P networks must be **complementary**, and one of them must conduct for every input combination




$$F = a \cdot b + \bar{a} \cdot \bar{b} + a \cdot c + c \cdot d + \bar{c} \cdot \bar{d}$$

The N and P networks are **NOT duals**, but the **switching functions they implement are complementary**
 
### Example of Another Complex CMOS Gate

This circuit does not have a pMOS network – just one transistor for each function; it will work only if F and G are complements of each other. Why?




Can evaluate the voltages at F and G ( $\{0, V_{DD}\}$ ) for each value of  $x, y$ , and  $z$

$$F = x \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot z + x \cdot y \cdot \bar{z} + x \cdot y \cdot z$$

$$G = \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z}$$
 
### Example of Another Complex CMOS Gate

This circuit does not have a pMOS network – just one transistor for each function; it will work only if F and G are complements of each other. Why?




Can evaluate the voltages at F and G ( $\{0, V_{DD}\}$ ) for each value of  $x, y$ , and  $z$

$$F = x \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot z + x \cdot y \cdot \bar{z} + x \cdot y \cdot z$$

$$G = \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z}$$
 
### Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of  $x, y$ , and  $z$  which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$


$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$

$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)
 
### Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of  $x, y$ , and  $z$  which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$

$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$


$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)


 
### Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of  $x, y$ , and  $z$  which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$

$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$

$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)

### Signal Strength


Voltages represent digital logic values

- **Strength** of signal:
  - How close it approximates ideal voltage
- $V_{DD}$  and  $GND$  rails are strongest 1 and 0
- nMOS transistors pass a strong 0
  - But degraded or weak 1
- pMOS transistors pass a strong 1
  - But degraded or weak 0


**Therefore, nMOS transistors are best for the “pull-down” network**
 
## Pass Transistors and Transmission Gates


Transistors can be used as switches; however, they could produce degraded outputs



 **Transmission gates** pass both 0 and 1 well




## Pass Transistor Logic

 

 
### "Pull-Up" Circuit

- Used to restore degraded logic 1 from output of nMOS pass transistor


 
## Pass Transistor Logic – Better Layout


Group similar transistors, so they can be in the same well



## Tristates


**Tristate Buffer** produces **Z** (high impedance) when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

 


Non-Restoring Tristate

 - Transmission gate acts as a tristate buffer
- Only two transistors, but **nonrestoring**
- Noise on A is passed to Y




 
## Tristate Inverter

Tristate inverter produces restored output, but complements signal



## Multiplexers

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

  


How many transistors are needed?  
(The better design uses 3 NAND  
gates and 1 inverter)

## Transmission Gate MUX

 
### Nonrestoring MUX

- Uses two transmission gates  $\Rightarrow$  only 4 transistors


 
### Inverting MUX – adds an inverter


- Uses compound gate AOI22
- Alternatively, a pair of tristate inverters (same thing)



## 4:1 Multiplexer
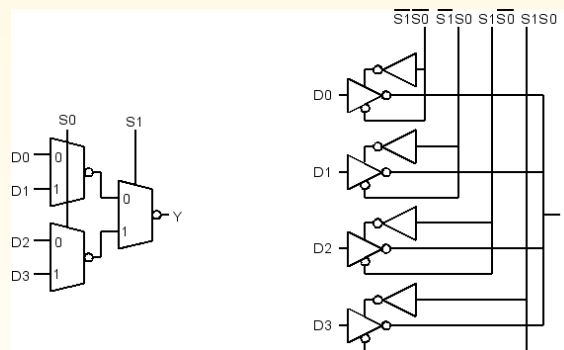
### A 4:1 MUX chooses one of 4 inputs using two selects


- Two levels of 2:1 MUXes
- Alternatively, four tristates



## D Latch


 
### Basic Memory Element

- When  $CLK = 1$ , latch is transparent
  - D flows through to Q like a buffer
- When  $CLK = 0$ , the latch is opaque
  - Q holds its old value independent of D
- a.k.a., **transparent latch** or **level-sensitive latch**



  
## D Latch, Cont'd

D Latch Design:  
MUX chooses  
between D and  
old Q




D Latch  
Operation

 


## D Flip-Flop (D-Flop)
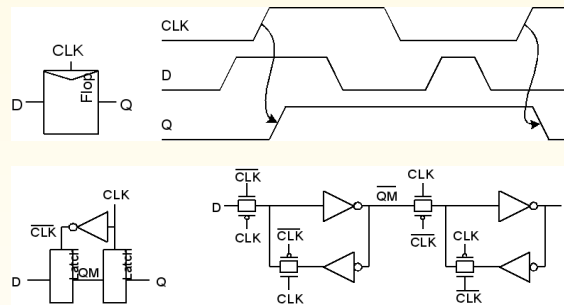
### Another common storage element

- When CLK rises, D is copied to Q
- At all other times, Q holds its value
- **positive edge-triggered flip-flop** or **master-slave flip-flop**
- Built from “master” and “slave” D latches




## D Flip-Flop Operation

 
 
## Race Condition – Hold Time Failure

Back-to-back flops can malfunction from clock skew


- Second flip-flop fires late
- Sees first flip-flop change and captures its result
- Called **hold-time failure** or **race condition**


 
## Non-Overlapping Clocks

A simple way to prevent races

- This works as long as non-overlap exceeds clock skew
- Used in safe (conservative) designs
- Industry does not generally use this approach – managing skew more carefully instead





## Gate Layout

### Building a library of standard cells


- Layout can be time consuming
- One solution is to have layouts of commonly used functions (Inverter, NAND, OR, MUX, etc.), designed to fit together very well

### Standard cell design methodology


- $V_{DD}$  and  $GND$  should abut (standard height)
- Adjacent gates should satisfy design rules
- nMOS at bottom and pMOS at top
- All gates include well and substrate contacts
- One of the large industry suppliers is ARM, others include TSMC and other foundries

## Examples of Standard Cell Layout

Inverter

 


NAND3

 


Horizontal N-diffusion and P-diffusion strips  
Vertical Polysilicon gates  
Metal1  $V_{DD}$  rail at top, Metal1  $GND$  rail at bottom  
 $32\lambda$  by  $40\lambda$
 
## Wiring Tracks and Well Spacing

**Wiring Track** is the space required for a wire  
Example,  $4\lambda$  width,  $4\lambda$  spacing from neighbor =  $8\lambda$  pitch  
Transistors also consume one wiring track




 Example, **well spacing**: wells must surround transistors by  $6\lambda$   
Implies  $12\lambda$  between opposite transistor flavors  
Leaves room for one wire track



 
## Example of Area Estimation

Estimate area by counting wiring tracks  
Multiply by 8 to express in  $\lambda$




 Estimating area of O3AI  
Sketch a stick diagram and estimate area



 
## Example Circuit 1

Fill in the Karnaugh map to represent the Boolean function implemented by the pass-transistor circuit.



## Example Circuit 1

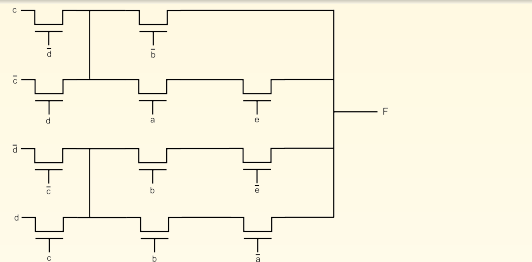


$F(a,b,c,d,e)$ :

	e				e			
	c				c			
	a				a			
d	0	0	1	1	1	1	0	0
	1	1	0	0	0	0	1	1
	0	0	1	1	1	0	1	0
b	1	1	0	0	0	1	0	1
 
## Example Circuit 2


Find the function, F, implemented by the following circuit



$$\overline{A} + BC + \overline{B} \overline{C}$$
 
## Example Circuit 2


Find the function, F, implemented by the following circuit



$$\overline{A} + BC + \overline{B} \overline{C}$$
 
### Example Circuit 3

Find the functions X and Y implemented by the following circuit




ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 35 / 37
 
### Example Circuit 3

Find the functions X and Y implemented by the following circuit



ECE Department, University of Texas at Austin

Lecture 3. Implementing Logic in CMOS

Jacob Abraham, September 3, 2020 36 / 37

## Functions to Circuits

Label the circuit so that it implements the function:

$$F = a \cdot (b \cdot c + \bar{b} \cdot \bar{c})$$

