
 


## 6. Memory, Finite-State Machines (Chapter 3, 3.5, 3.6)

Sept. 19, 2018







- **Review**
  - Storage Elements (latches)
- **D-Latch, Registers**
- **Memories**
  - Address space
  - Memory structure
- **Finite-State Machines**
  - State diagram
  - Implementation
- **Example: warning sign**

# R-S Latch: Simple Storage Element

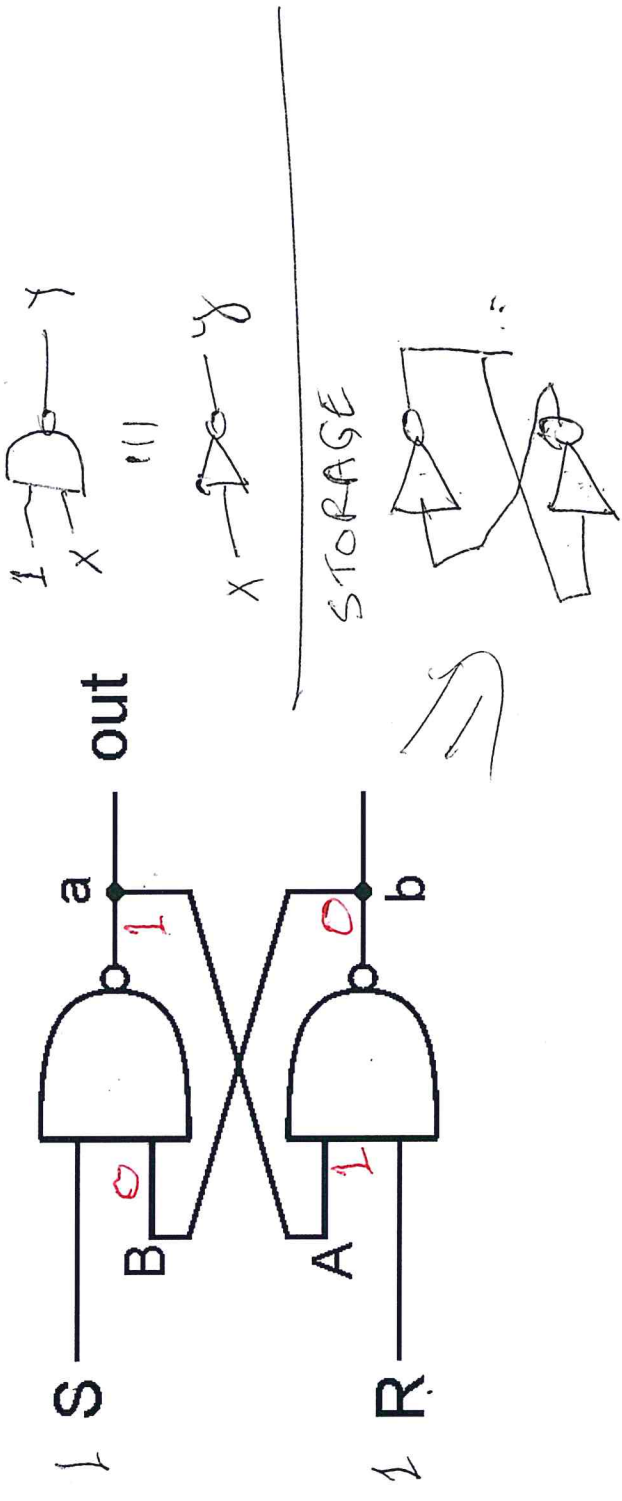

# R-S Latch Behavior

Start with output = 0

   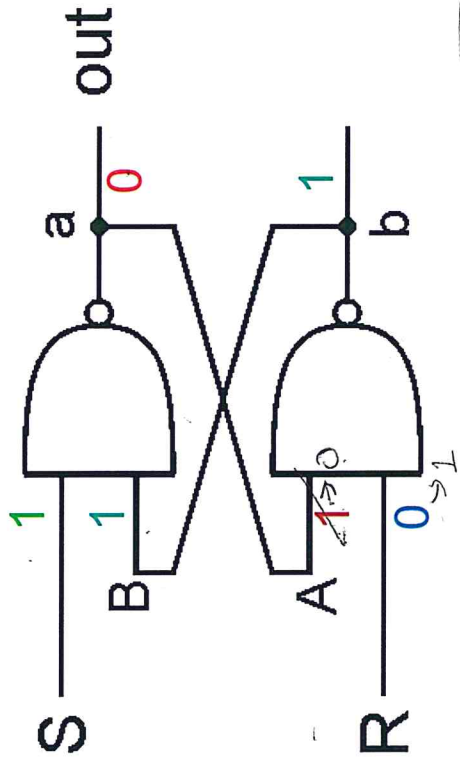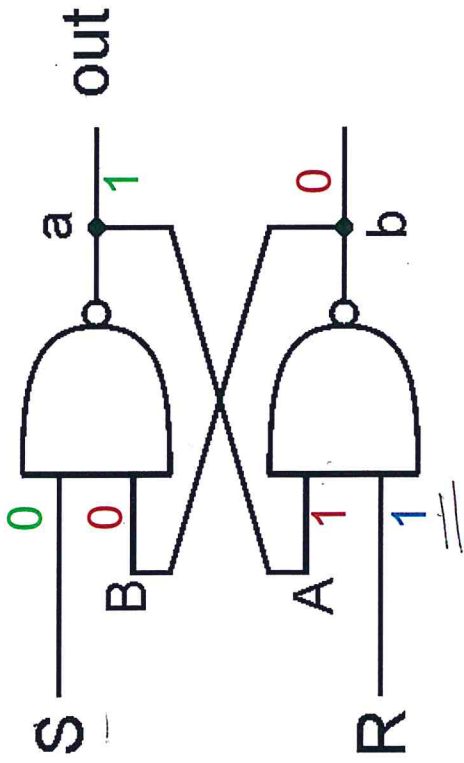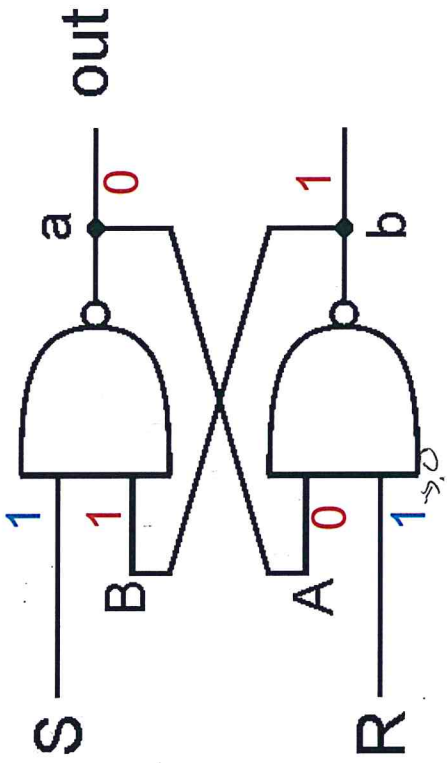

# S-R LATCH

$R = S = 1$  : HOLD (PREVIOUS VALUE)

$R = 0, S = 1$  :  $OUT = 0$


$R = 1, S = 0$  :  $OUT = 1$

$R = 0, S = 0$  : NOT ALLOWED
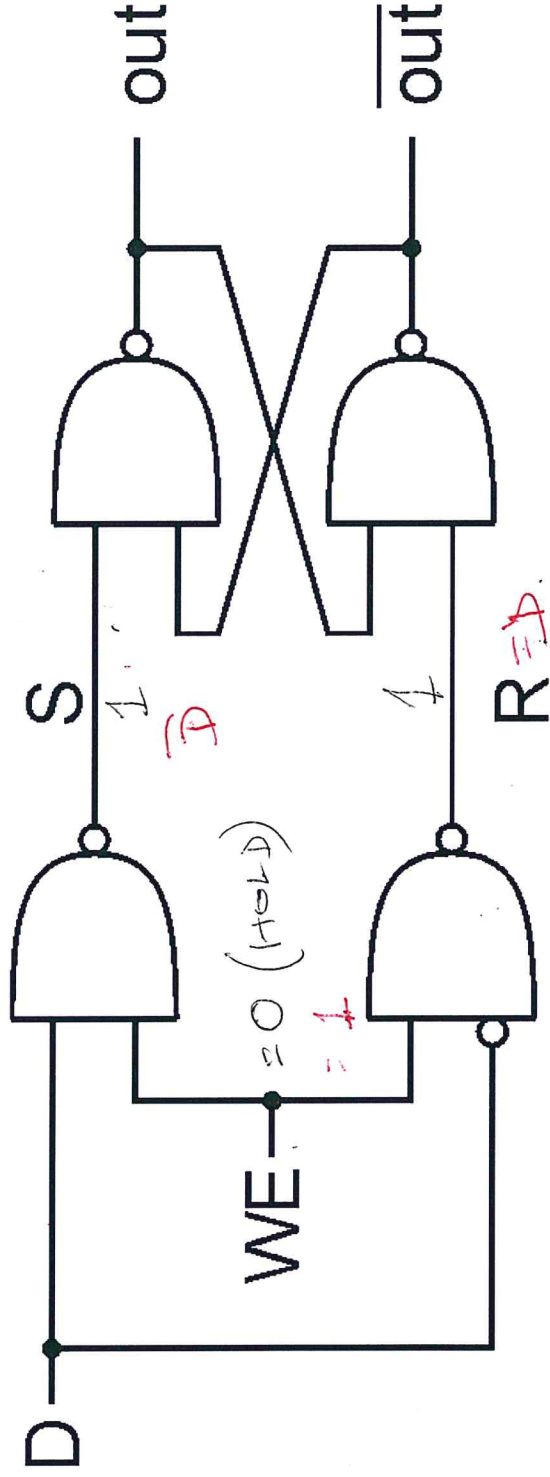
# Gated D-Latch

Two inputs: D (data) and WE (write enable)


- when **WE = 1**, latch is set to **value of D**
  - **S = NOT(D)**, **R = D**
- when **WE = 0**, latch holds **previous value**
  - **S = R = 1**


 
# Register

A register stores a multi-bit value.

- We use a collection of D-latches, all controlled by a common WE.
- When WE=1, n-bit value D is written to register.



# Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- just a convention -- could be left to right, but must be consistent

Use brackets to denote range:

D[l:r] denotes bit l to bit r, from *left to right*

$A = \overset{15}{0} \overset{14}{1} \overset{13}{0} \overset{12}{1} \overset{11}{0} \overset{10}{0} \overset{9}{1} \overset{8}{1} \overset{7}{1} \overset{6}{0} \overset{5}{1} \overset{4}{0} \overset{3}{1} \overset{2}{0} \overset{1}{1} \overset{0}{0}$



$A[14:9] = 101001$




$A[2:0] = 101$

May also see  $A\langle 14:9 \rangle$ , especially in hardware block diagrams.

# Memory

**Address Space:**  
number of locations  
(usually a power of 2)

$k = 2^n$   
locations

 

**Addressability:**  
number of bits per location  
(e.g., byte-addressable)

$m$  bits




# 2<sup>2</sup> x 3 Memory

Address

2 BITS


Data In

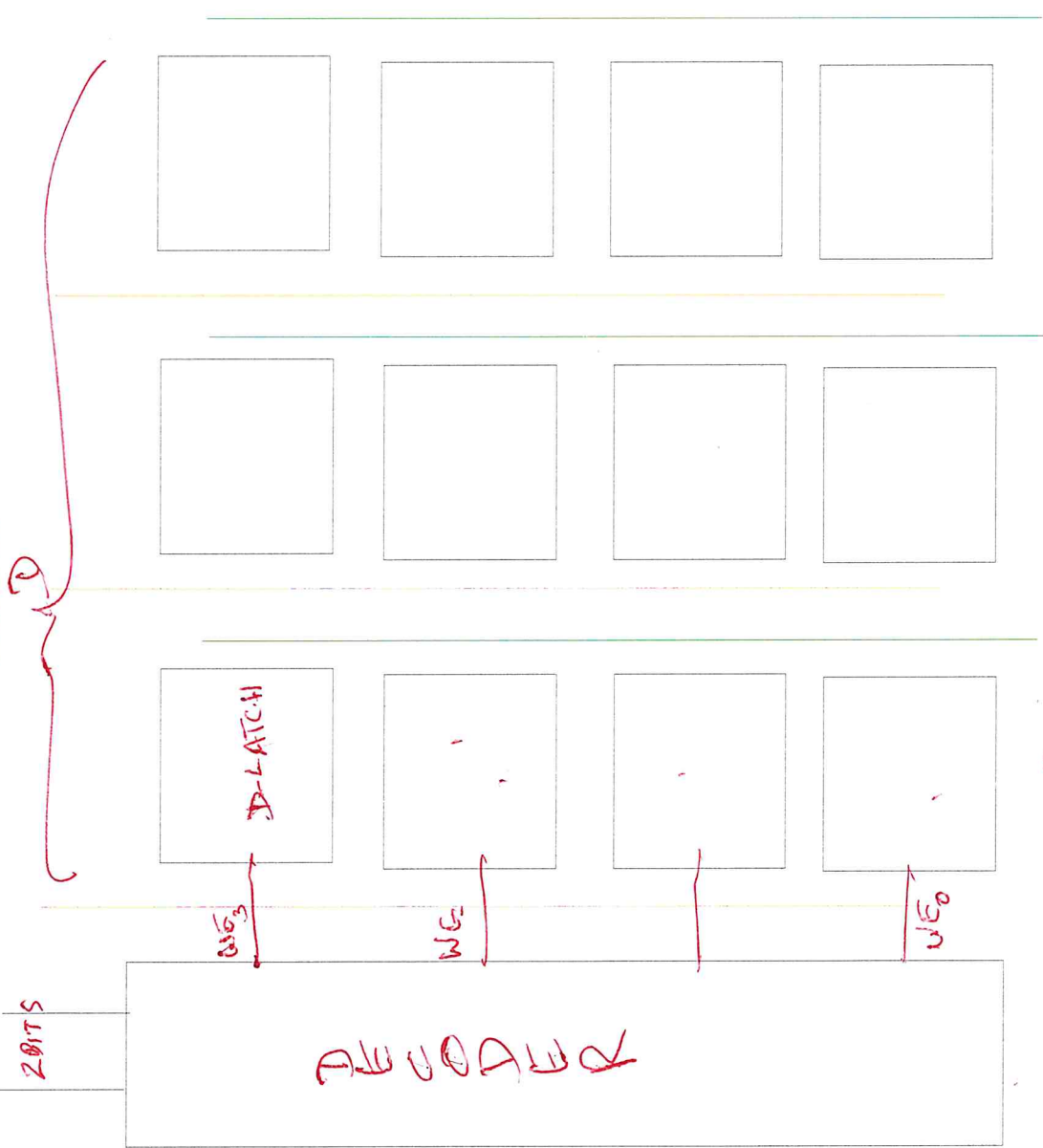

Data Out


Q

# 2<sup>2</sup> x 3 Memory

 


# SEQUENTIAL LOGIC

EXAMPLE: LOCK

 

COMBINATIONAL

 

SEQUENTIAL

EX: R-13, L-22, R-3

STATE:

"SNAPSHOT" OF THE RELEVANT ELEMENTS  
OF A SYSTEM

## State of Sequential Lock

Our lock example has four different states, labelled A-D:

- A:** The lock is **not open**, and no relevant operations have been performed.
  - B:** The lock is **not open**, and the user has completed the **R-13** operation.
  - C:** The lock is **not open**, and the user has completed **R-13**, followed by **L-22**.
  - D:** User has completed **R-13**, followed by **L-22**, followed by **R-3**: the lock is **open**.
-

# FINITE-STATE MACHINES

1. FINITE NUMBER OF STATES

2. ~~EXTERNAL INPUTS~~


OUTPUTS

3.

4. SPECIFIED STATE TRANSITIONS


5. SPECIFIED OUTPUT VALUES

"STATE DIAGRAM"

 


OR, "STATE TABLE"

# STATE DIAGRAM FOR LOCK

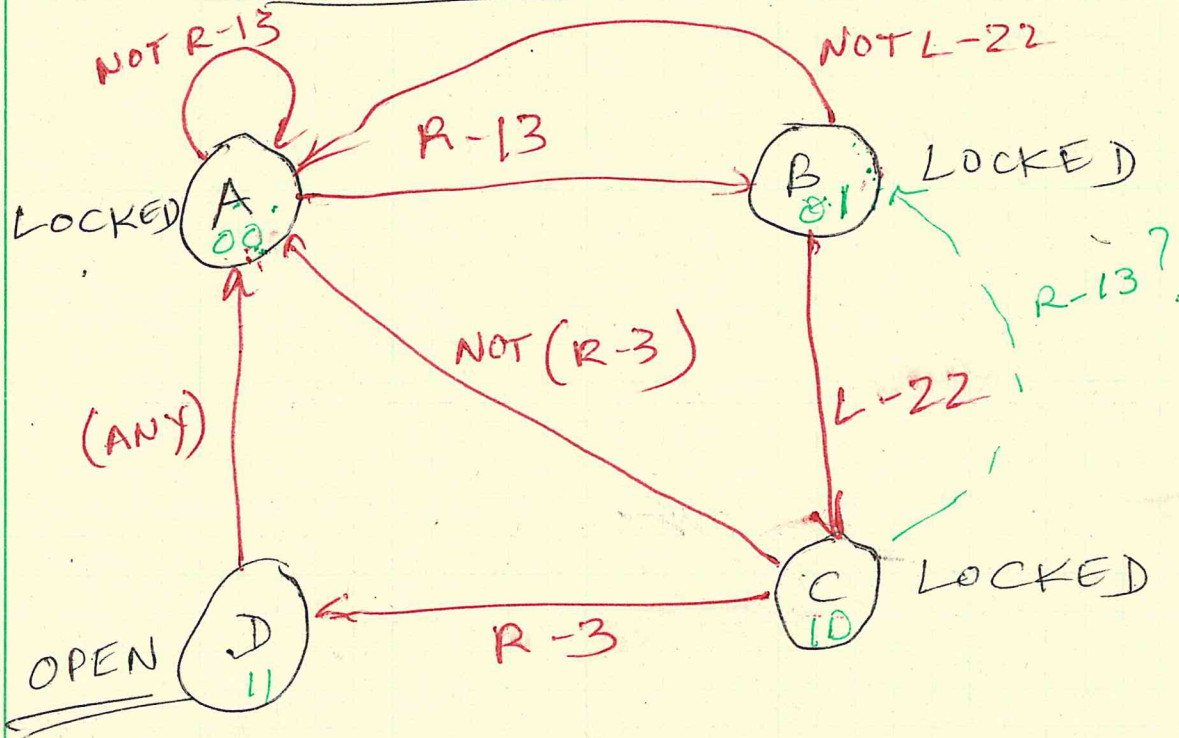

TYPICALLY,

 CLOCK TRIGGERS TRANSITIONS FROM ONE STATE TO THE NEXT




# Implementing a Finite State Machine

## Combinational logic


- Determine outputs and next state.

## Storage elements

- Maintain state representation.

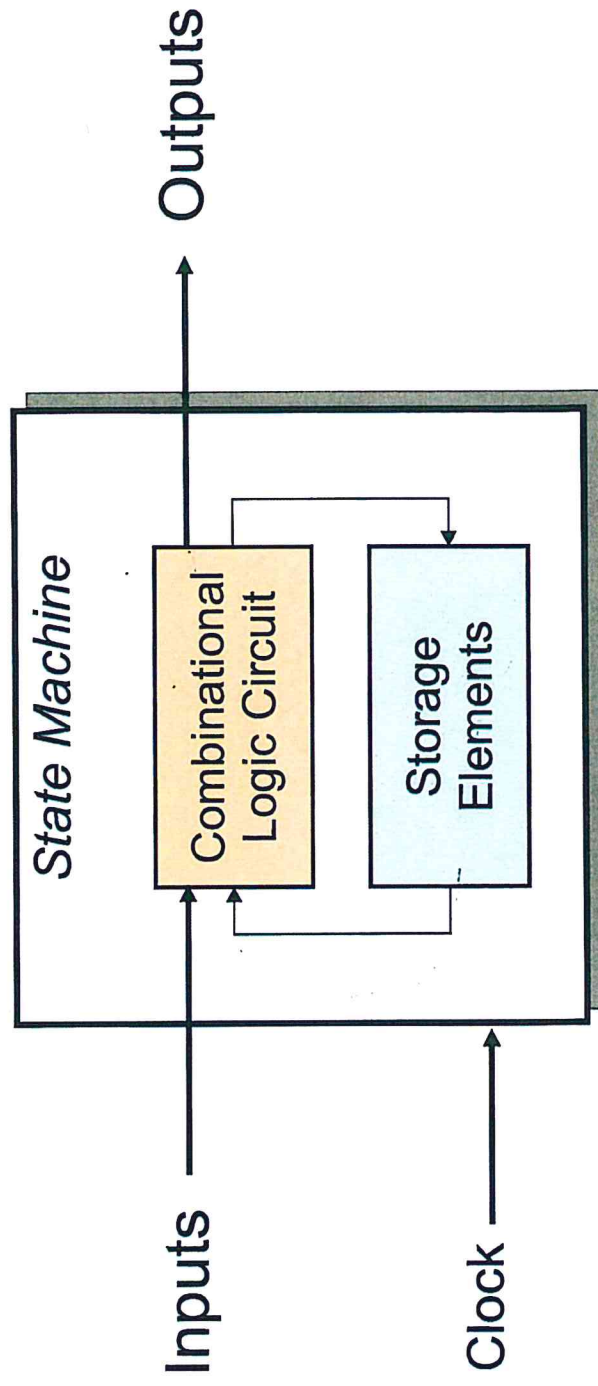

# Storage: Master-Slave Flipflop

 

During 1<sup>st</sup> phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2<sup>nd</sup> phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.