

Jacob Abraham

Department of Electrical and Computer Engineering The University of Texas at Austin

> VLSI Design Fall 2020

October 8, 2020

ture 12. Dynamic CMOS Logic

Jacob Abraham, October 8, 2020 1 / 25

Jacob Abraham, October 8, 2020 1 / 25

Review: Fixing Hold-Time Violations


ECE Department, University of Texas at Austi


ECE Department, University of Texas at Austin


- Measure all hold times with respect to the main clock
- Adjust the hold time if the flop is receiving a delayed clock
- Compute the shortest path delay from the rising edge of the clock

Lecture 12. Dynamic CMOS Logic

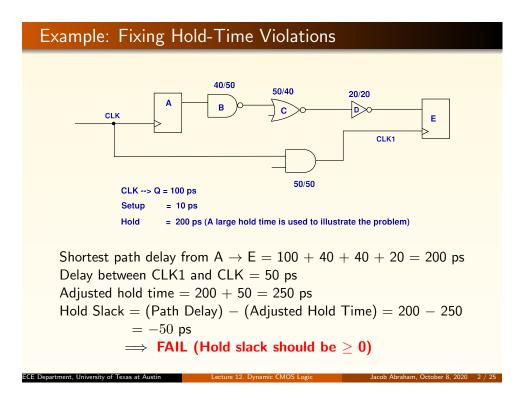
• Check to see if there are any hold time failures




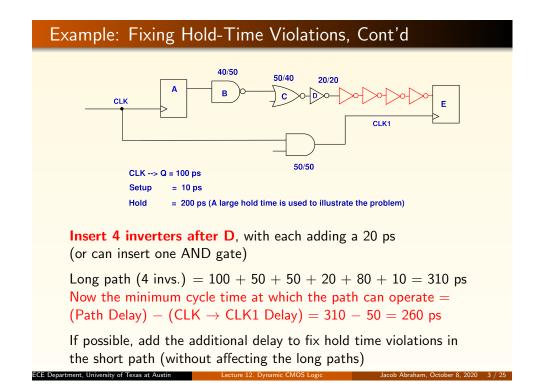

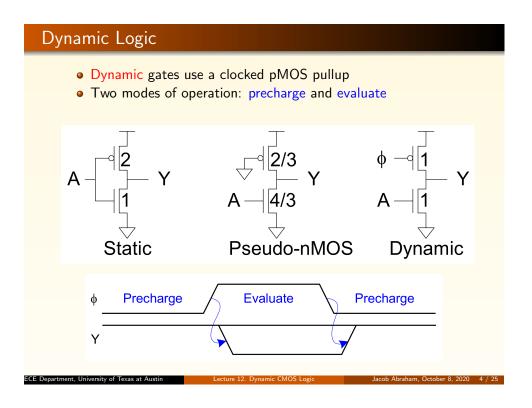

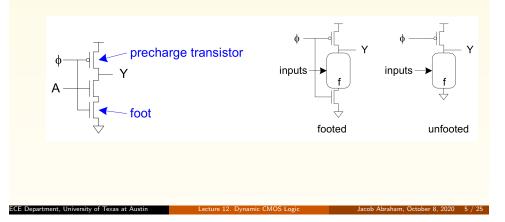The "Foot" Transistor What if pulldown network is ON during precharge? Use series evaluation transistor to prevent fight between pMOS and nMOS transistors




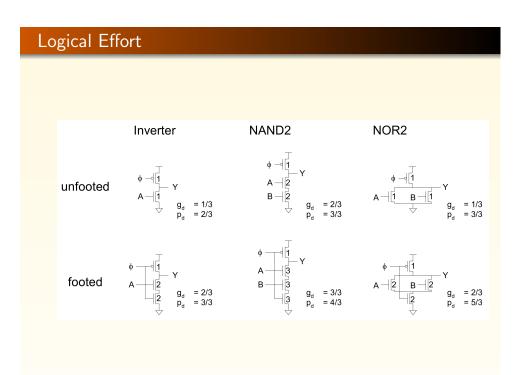

e 12. Dynamic CMOS Logi


Jacob Abraham, October 8, 2020 6 / 25

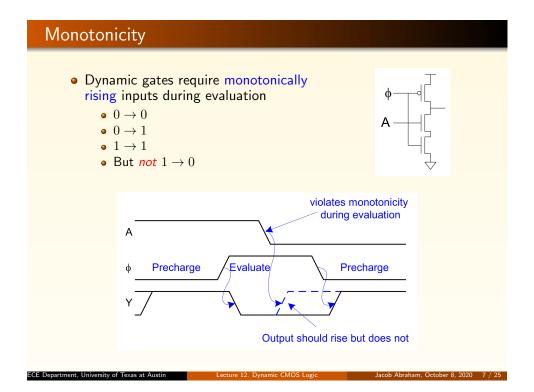ECE Department, University of Texas at Austin





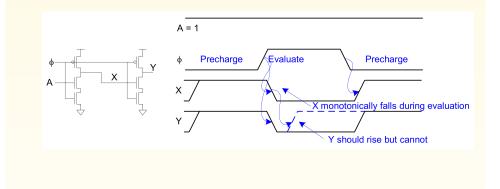
- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




c CMOS L

Domino Gates

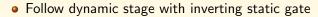ECE Department, University of Texas at Au



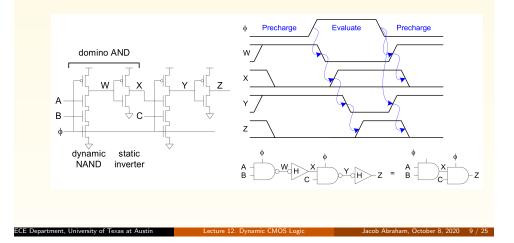
- Dynamic/static pair is called domino gate
- Produces monotonic outputs



Jacob Abraham, October 8, 2020 8 / 25

Domino Optimizations

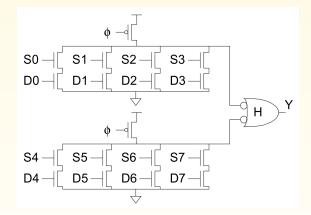- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially, precharge in parallel
- Evaluation is more critical than precharge
- HI-skewed static stages can perform logic




c CMOS I

Jacob Abraham, October 8, 2020 10 / 25

Dual-Rail Domino


ECE Department, University of Texas at Au

 - Domino only performs noninverting functions:
 AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
 - Takes true and complementary inputs
 - Produces true and complementary outputs



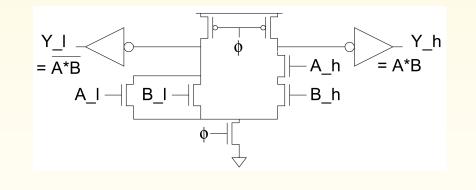
Example: AND/NAND

- Given A_h, A_l, B_h, B_l
- Compute $Y_h = A * B$, $Y_l = \sim (A * B)$
- Pulldown networks are conduction complements



Example: XOR/XNOR

ECE Department, University of Texas at A

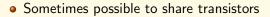



• Sharing works well in implementations of symmetric functions

c CMOS L

Jacob Abraham, October 8, 2020 12 / 25

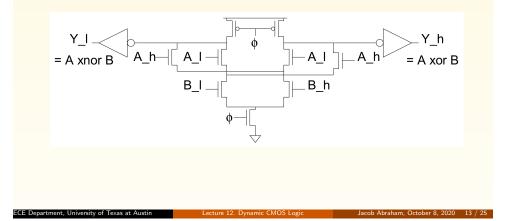• See papers on "relay logic" published over 50 years ago




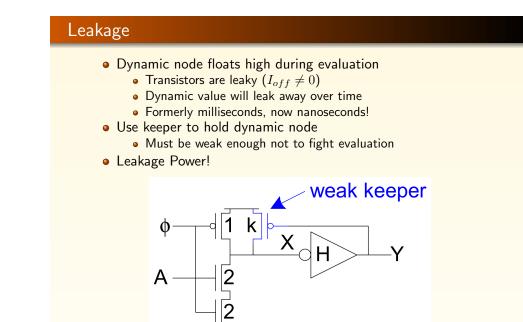


Charge Sharing

ECE Department, University of Texas at Austin

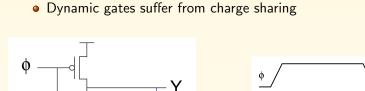ECE Department, University of Texas at Austi



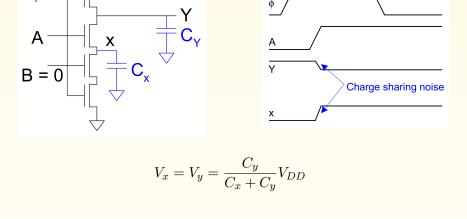


b Abraham, October 8, 2020 14 / 25

Jacob Abraham, October 8, 2020 15 / 25


Secondary Precharge


ECE Department, University of Texas at Austi

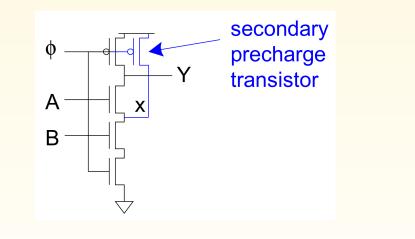
- Solution: add secondary precharge transistors
 Typically need to precharge every other node
- Big load capacitance on Y helps as well




Abraham, October 8, 2020 16 / 25

 

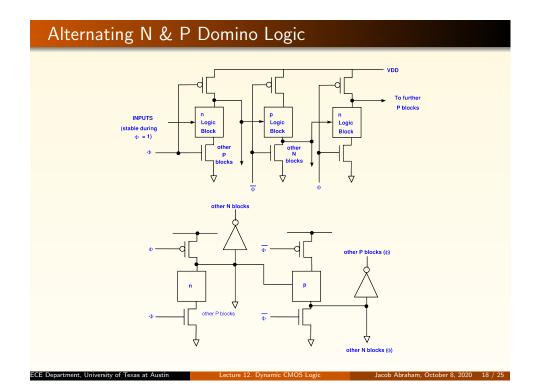


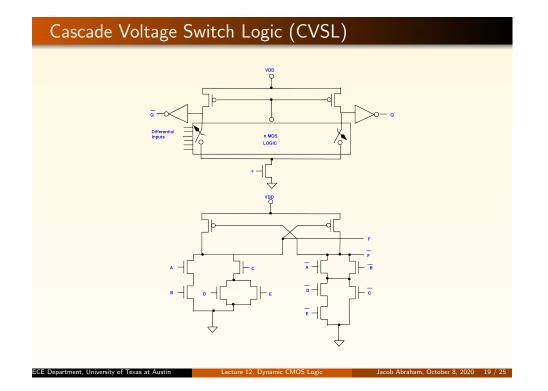


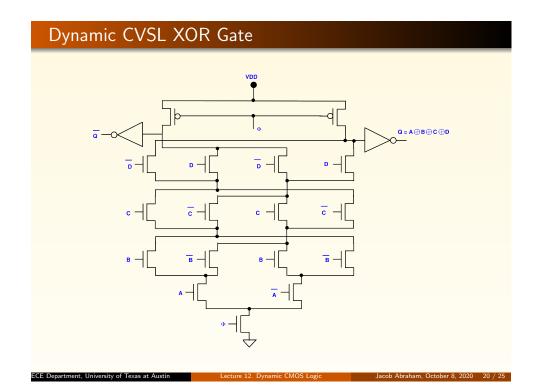

Dual-Rail Domino Full Adder Design

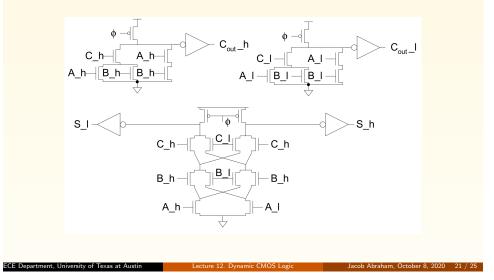
- Very fast, but large and power hungry
- Used in very fast multipliers




 

Domino Logic in Current Designs

- Domino design from Intrinsity used in 1-GHz 0.75W ARM Cortex A8 from Samsung (Intrinsity later acquired by Apple)
- Fast Domino (called "Fast14 NDL") gates are inserted selectively into critical speed paths, with custom SRAMs and optimized synthesized logic elsewhere
- Standard power saving techniques are also used
- Domino gates are clocked by multiphase clocks
- A type of "super-pipeline" where the domino footers form the barrier for the pipeline operation

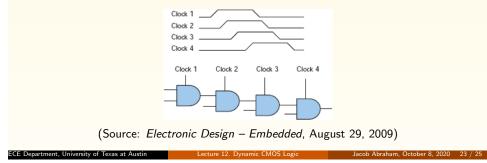

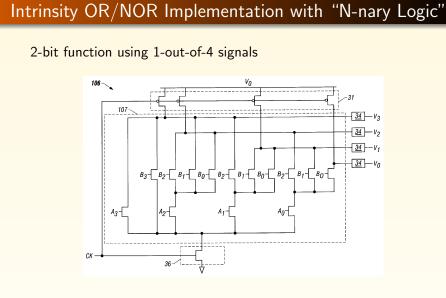

Ref: U. S. Patent 6066965, Method and apparatus for a N-nary Logic Circuit Using 1 of 4 Signals

Jacob Abraham, October 8, 2020 24 / 25

ECE Department, University of Texas at Austi

