

# 18. Design for Low Power

Jacob Abraham

Department of Electrical and Computer Engineering  
The University of Texas at Austin

VLSI Design  
Fall 2020

October 29, 2020

# Power and Energy

Power is drawn from a voltage source attached to the  $V_{DD}$  pin(s) of a chip

## Instantaneous Power:

$$P(t) = i_{DD}(t)V_{DD}$$

## Energy:

$$E = \int_0^T P(t)dt = \int_0^T i_{DD}(t)V_{DD}dt$$

## Average Power:


$$P_{avg} = \frac{E}{T} = \frac{1}{T} \int_0^T i_{DD}(t)V_{DD}dt$$

## Energy stored in capacitor when it is charged from 0 to $V_C$ ,

$$E_C = \int_0^\infty I(t)V(t)dt = \int_0^\infty C \frac{dV}{dt} V(t)dt = C \int_0^{V_c} V(t)dV = 1/2 CV_C^2$$

The capacitor releases this energy when it discharges back to 0
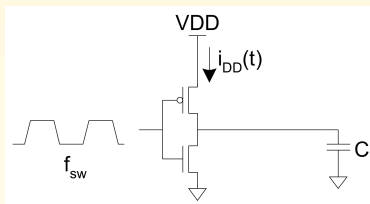
# Example – CMOS Inverter Driving a Load Capacitance



- When input switches from 1 to 0, pMOS transistor turns on and charges the load to  $V_{DD}$
- Energy stored in the capacitor is  $E_c = \frac{1}{2}C_L V_{DD}^2$
- Energy delivered from the power supply is

$$E_c = \int_0^\infty C \frac{dV}{dt} V_{DD} dt = C V_{DD} \int_0^{V_{DD}} dV = C V_{DD}^2$$

**Only half of the energy from the power supply is stored in the capacitor**

**The other half is converted to heat (resistance of the pMOS transistor)**

# Sources of Power Dissipation

## Dynamic Power Dissipation

- Charging and discharging of load capacitances
- “Short-circuit” current while both p- and n-MOS networks are partially on


## Static Dissipation

- Subthreshold leakage (through OFF transistors)
- Gate leakage through gate dielectric
- Junction leakage from source/drain diffusion
- Contention current in ratioed circuits
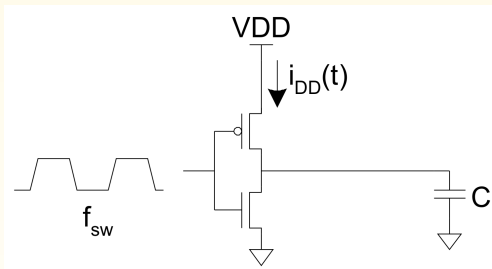
# Dynamic Power

- Dynamic power is required to charge and discharge load capacitances when transistors switch
- One cycle involves a rising and falling output
- On rising output, charge  $Q = CV_{DD}$  is required
- On falling output, charge is dumped to GND
- This repeats  $Tf_{sw}$  times over an interval of  $T$

$$\begin{aligned}P_{dynamic} &= \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt \\&= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt \\&= \frac{V_{DD}}{T} [T f_{sw} C V_{DD}] \\&= \boxed{C V_{DD}^2 f_{sw}}\end{aligned}$$



# Activity Factor

- Suppose the system clock frequency =  $f$
- Let  $f_{sw} = \alpha f$ , where  $\alpha$  = activity factor
  - If the signal is a clock,  $\alpha = 1$
  - If the signal switches once per cycle,  $\alpha = 1/2$
  - Dynamic gates: switch either 0 or 2 times per cycle,  $\alpha = 1/2$
  - Static gates: depends on design, but typically  $\alpha = 0.1$

- Dynamic power: 
$$P_{dynamic} = \alpha C V_{DD}^2 f$$



# Computing Activity Factors

$P_i$ : probability that node  $i$  is 1 ( $1 - P_i$  is probability that it is 0)

Activity factor of node  $i$ ,  $\alpha_i$ , is the probability that the node is 0 in one cycle and 1 in the next

If probability is uncorrelated from cycle to cycle,  $\alpha_i = \bar{P}_i P_i$


Example: 4-input AND gate

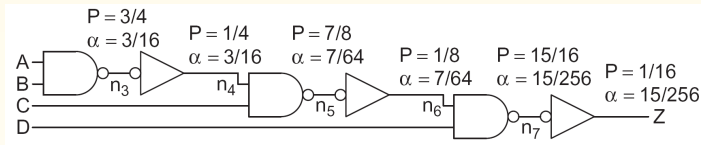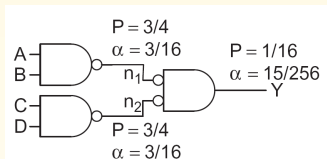

**Tools exist to calculate activity factors, either using probabilities, or by monitoring nodes during simulation**
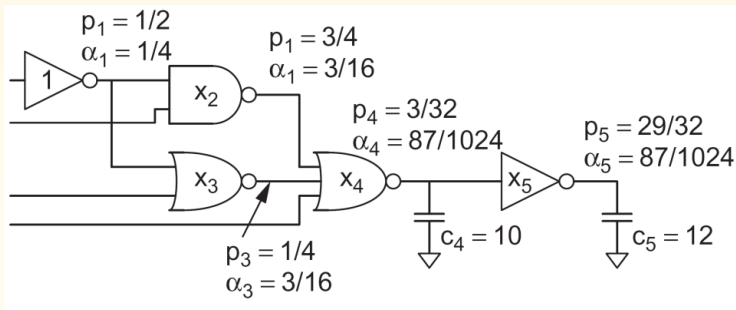
# Activity Factor Example


Where there is **reconvergent fanout**, calculating probabilities becomes more difficult






# Glitches Contribute to Power Consumption

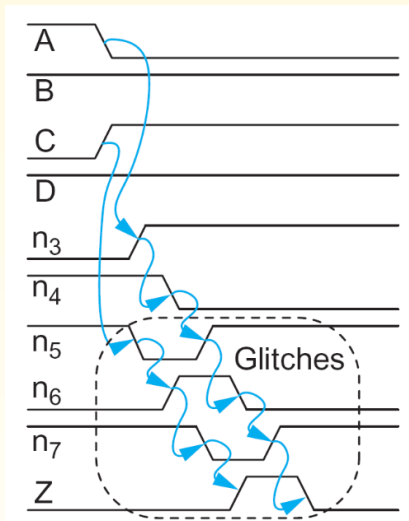Example, glitches in chain of gates and inverters implementing 4-input NAND gate


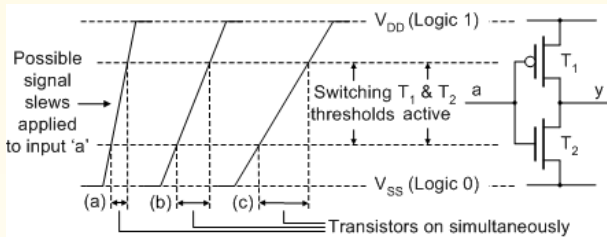
# Short Circuit (“Crowbar”) Current

- When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- Leads to a blip of “short circuit” current.
- $< 10\%$  of dynamic power if rise/fall times are comparable for input and output



Source: EE Times, June 9, 2003

Power reduction depends on the sizes of the driving and driven transistors and the input slew

# Example

- 200 million transistor chip
  - 20M logic transistors, average width:  $12\lambda$
  - 180M memory transistors, average width  $4\lambda$
  - 1.2 V 100 nm process
  - $C_g = 2 \text{ fF}/\mu\text{m}$

## Estimate dynamic power

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks!)
- Estimate dynamic power consumption per MHz (neglect wire capacitance)

$$C_{logic} = (20 \times 10^6)(12\lambda)(0.05\mu\text{m}/\lambda)(2\text{fF}/\mu\text{m}) = 24\text{nF}$$

$$C_{mem} = (180 \times 10^6)(4\lambda)(0.05\mu\text{m}/\lambda)(2\text{fF}/\mu\text{m}) = 72\text{nF}$$

$$P_{dynamic} = [0.1C_{logic} + 0.05C_{mem}](1.2)^2 f = 8.6\text{mW}/\text{MHz}$$

- Static power is consumed even when chip is quiescent.
  - Ratioed circuits burn power in fight between ON transistors
  - Leakage draws power from nominally OFF devices

$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_t}{n v_T}} \left[ 1 - e^{\frac{-V_{ds}}{v_T}} \right]$$

$$V_t = V_{t0} - \eta V_{ds} + \gamma (\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s})$$

$\eta$  describes drain-induced barrier lowering (DIBL),

$\gamma$  describes the body effect

For any appreciable  $V_{ds}$ , the term in brackets approaches unity

# Leakage Example: Estimate Static Power

- Process has two threshold voltages and two oxide thicknesses
- Subthreshold leakage:
  - 20 nA/ $\mu\text{m}$  for low  $V_t$
  - 0.02 nA/ $\mu\text{m}$  for high  $V_t$
- Gate leakage:
  - 3 nA/ $\mu\text{m}$  for thin oxide
  - 0.002 nA/ $\mu\text{m}$  for thick oxide
- Memories use low-leakage transistors everywhere, and gates use low-leakage transistors on 80% of logic

High leakage:  $(20 \times 10^6)(0.2)(12\lambda)(0.05\mu\text{m}/\lambda) = 2.4 \times 10^6 \mu\text{m}$

Low leakage:

$$(20 \times 10^6)(0.8)(12\lambda)(0.05\mu\text{m}/\lambda) + (180 \times 10^6)(4\lambda)(0.05\mu\text{m}/\lambda) = 45.6 \times 10^6 \mu\text{m}$$

$$I_{static} = (2.4 \times 10^6 \mu\text{m})[(20\text{nA}/\mu\text{m})/2 + (3\text{nA}/\mu\text{m})] + (45.6 \times 10^6 \mu\text{m})[(0.02\text{nA}/\mu\text{m})/2 + (0.002\text{nA}/\mu\text{m})] = 32\text{mA}$$

$$P_{static} = I_{static}V_{DD} = 38\text{ mW}$$

If no low-leakage devices used,  $P_{static} = 749\text{ mW}$


## Closer look at the power



15

Source: Shekhar Borkar, Intel

## Power density will increase

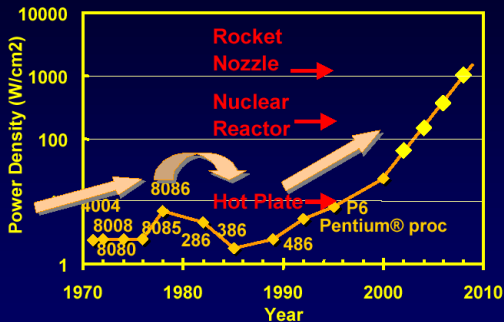


Power density too high to keep junctions at low temp

intel

16

Source: Shekhar Borkar, Intel

# Power Delivery Problem

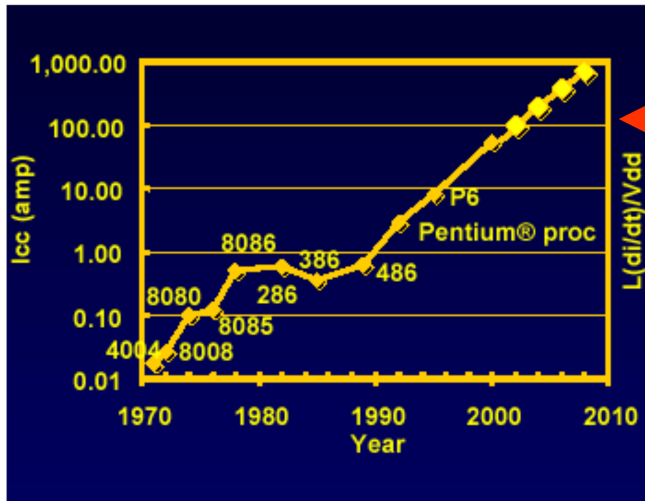



Your car  
starter !

Source: Shekhar Borkar, Intel


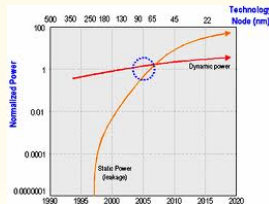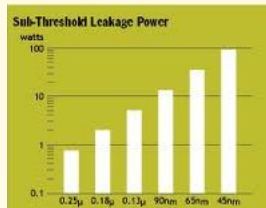
# Leakage Becoming A Major Component of Power

- Leakage component to active power becomes significant % of total power
- $\approx 10\%$  in  $0.18\mu\text{m}$  technology
- Acceptable limit less than  $\approx 10\%$ , implies serious challenge in  $V_t$  scaling!



Sources: S. Borkar, Intel; Chip Design Magazine


# Low Power Design

- Reduce dynamic power
  - $\alpha$ : clock gating, sleep mode
  - $C$ : small transistors (especially on clock), short wires
  - $V_{DD}$ : lowest suitable voltage
  - $f$ : lowest suitable frequency
- Reduce static power
  - Selectively use ratioed circuits
  - Selectively use low  $V_t$  devices
  - Leakage reduction: stacked devices, body bias, low temperature

## Use a combination of techniques at different levels


- Algorithm
- Architecture
- Logic/circuit
- Technology/circuit

# Architecture-Driven Voltage Scaling

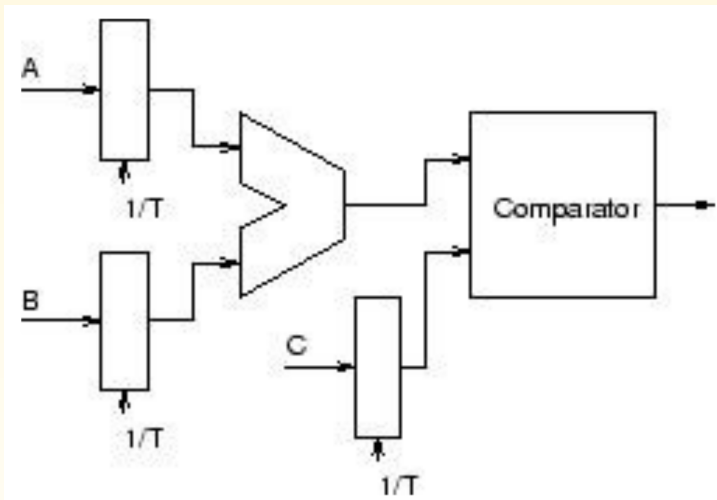

Data-path operator

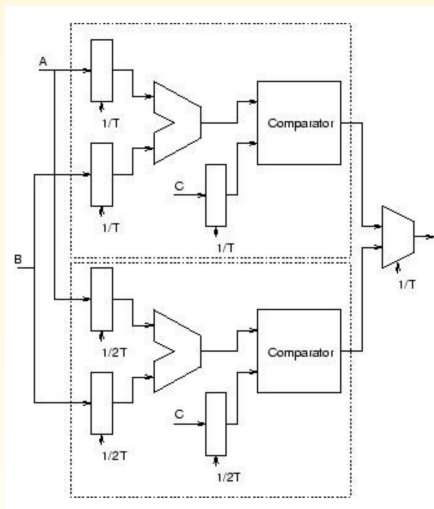
# Architecture-Driven Voltage Scaling, Cont'd



Parallel Implementation

$$P_{par} = (2.15C)(0.58V)^2(0.5f) \approx 0.36P$$

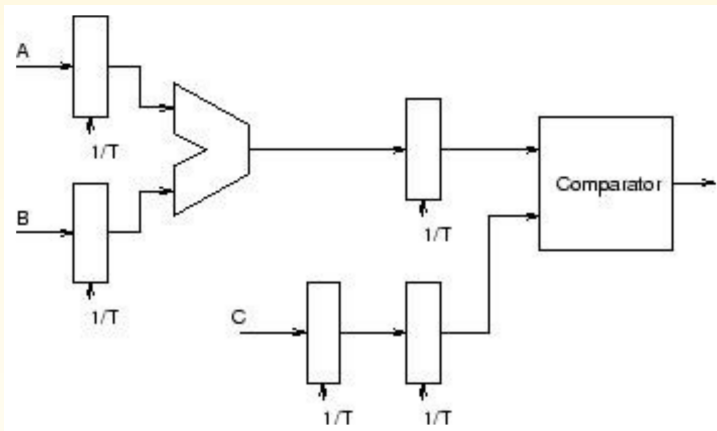
# Architecture-Driven Voltage Scaling, Cont'd



Pipelined Implementation


$$P_{pipe} = (1.15C)(0.58V)^2(f) \approx 0.39P$$
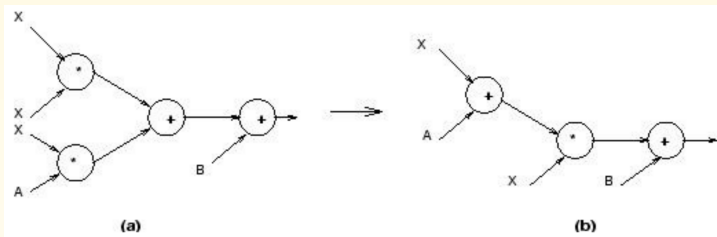
# Power Optimization Using Operation Reduction




Reducing operations, while maintaining throughput
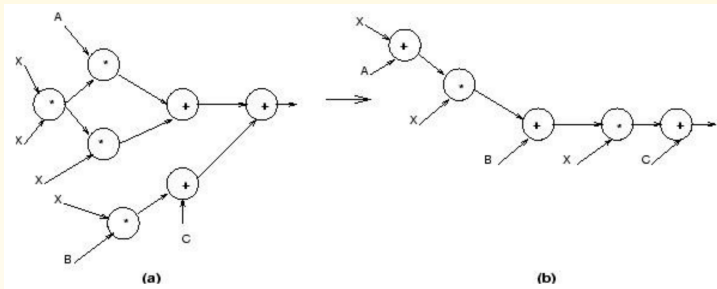
# Power Optimization Using Operation Reduction, Cont'd



Reducing operations, with lower throughput
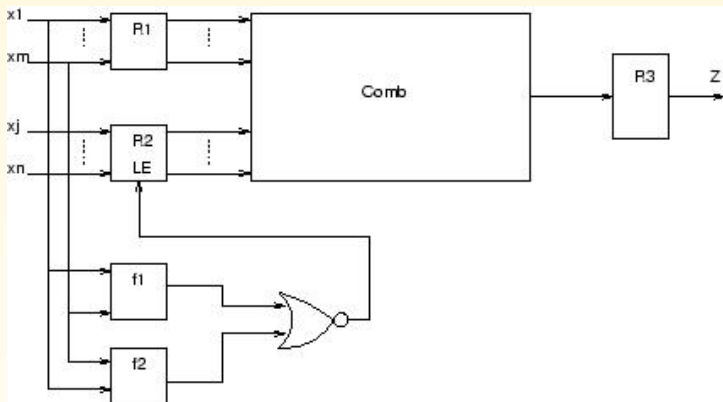
# Precomputation-Based Optimization for Low Power




Precomputation Architecture

$$f_1 = 1 \implies Z = 1; \quad f_2 = 1 \implies Z = 0$$



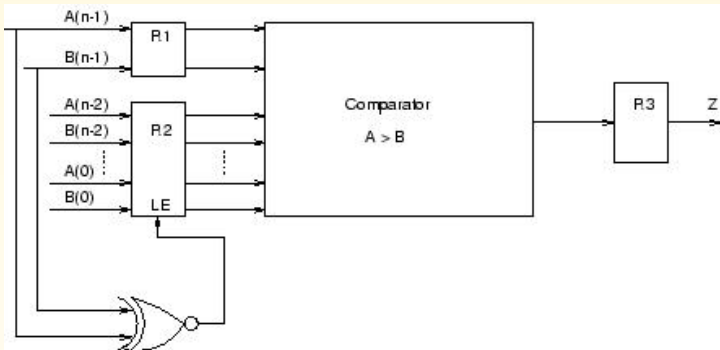
# Precomputation-Based Optimization for Low Power, Cont'd



N-bit Comparator

$$f_1 = A(n-1) \cdot \overline{B(n-1)}; \quad f_2 = \overline{A(n-1)} \cdot B(n-1)$$
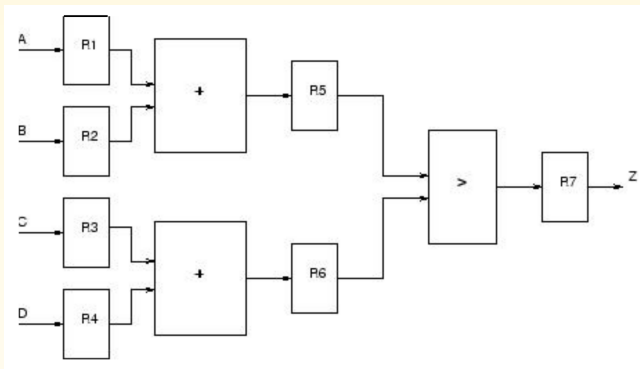
# Precomputation-Based Optimization for Low Power, Cont'd




Adder-comparator circuit

$$f_1 = A(n-1) \cdot B(n-1) \cdot \overline{C(n-1)} \cdot \overline{D(n-1)}$$

$$f_2 = \overline{A(n-1)} \cdot \overline{B(n-1)} \cdot C(n-1) \cdot D(n-1)$$

# Stack Effect – Subthreshold Leakage

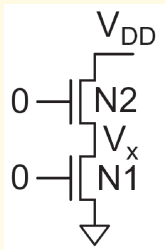



Stack effect reduces subthreshold leakage by a factor of  $\approx 10$

Stacks with three or more OFF transistors have even lower leakage


Silicon-on-Insulator (SOI) circuits are attractive for low-leakage designs

# Gate Leakage

Affected by voltage across the gate

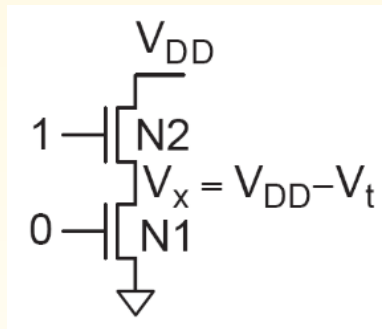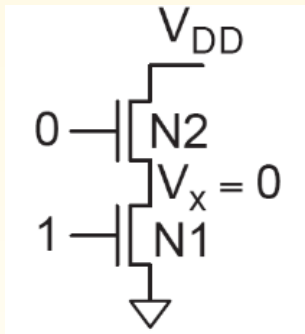

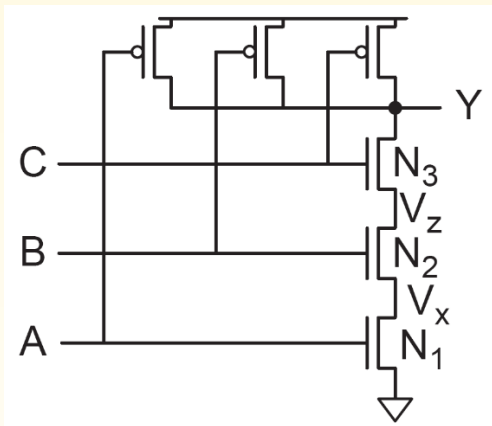
## Example – Pattern Dependence of Gate and Subthreshold Leakage



# Gate and Subthreshold Leakage in NAND3 (nA)

Input State (ABC)	$I_{\text{sub}}$	$I_{\text{gate}}$	$I_{\text{total}}$	$V_x$	$V_z$
000	0.4	0	0.4	stack effect	stack effect
001	0.7	0	0.7	stack effect	$V_{DD} - V_t$
010	0	1.3	1.3	intermediate	intermediate
011	3.8	0	10.1	$V_{DD} - V_t$	$V_{DD} - V_t$
100	0.7	6.3	7.0	0	stack effect
101	3.8	6.3	10.1	0	$V_{DD} - V_t$
110	5.6	12.6	18.2	0	0
111	28	18.9	46.9	0	0

# Power Gating

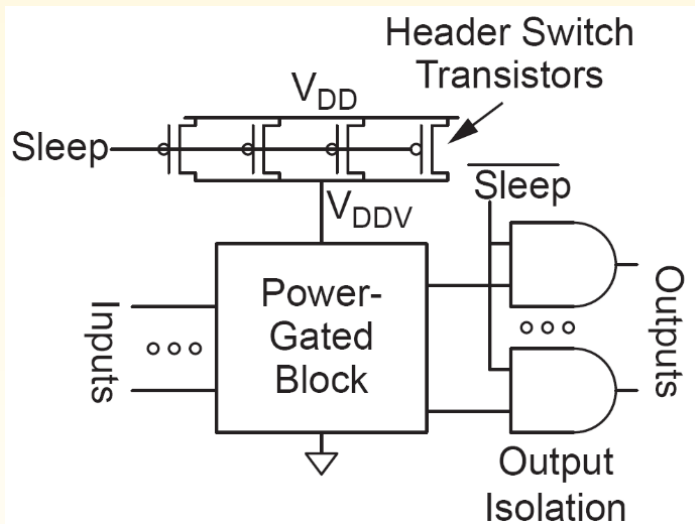


# Controlling Threshold Voltages for Reduced Leakage

## Multiple $V_t$ , Longer channels, Oxide thicknesses


- Low- $V_t$  on critical paths, High- $V_t$  on other paths for reduced leakage
- Longer transistors in the caches
- Thicker oxides for I/O transistors

## Body Bias

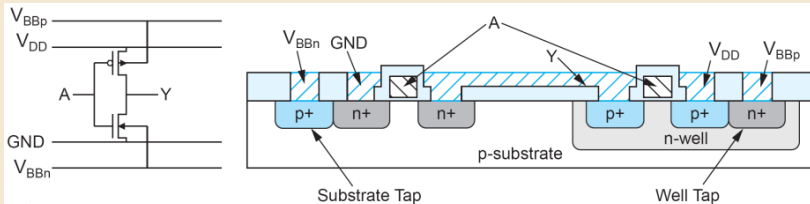




# Voltage Domains for Low Power

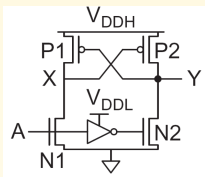


Level Converter

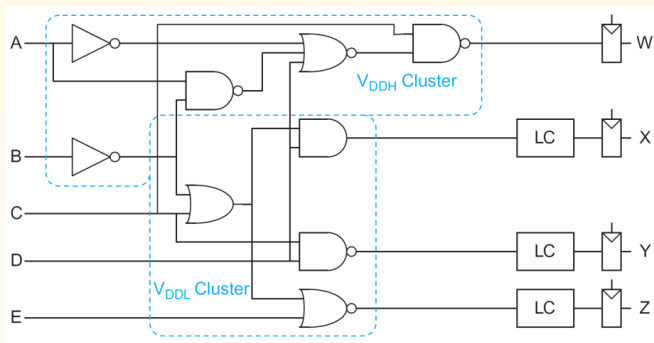


Clustered Voltage Scaling

# Dynamic Voltage Scaling (DVS)

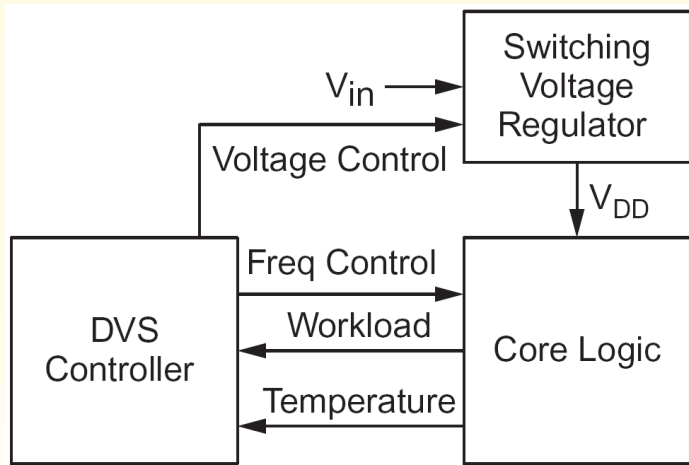


# Energy Reduction from DVS

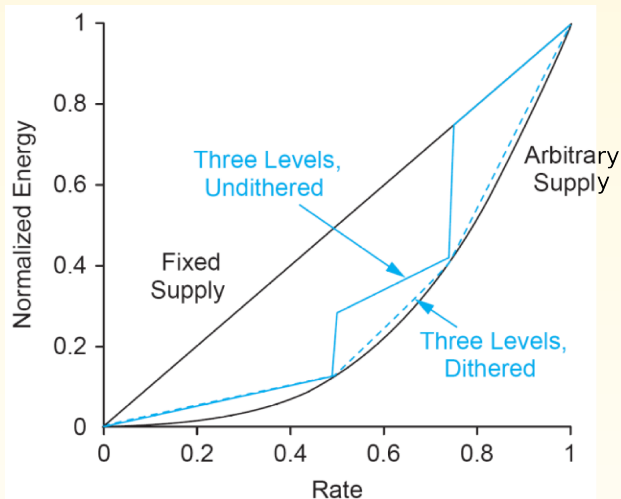
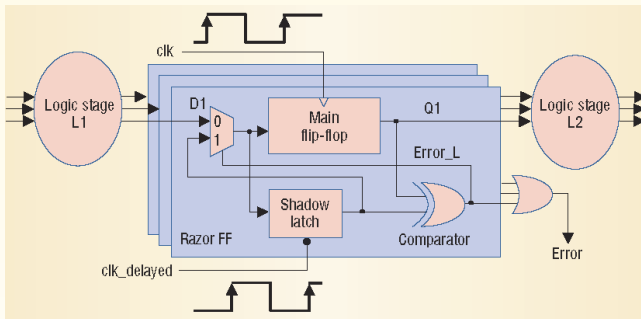
# RAZOR


- Error-tolerant dynamic voltage scaling (DVS) technology which eliminates the need for the voltage margins required for “always correct” circuit operations design
- A different value in the shadow latch shows timing errors
- Pipeline state is recovered after timing-error detection
- Error detection is done at the circuit level
  - The design overhead is large if timing paths are well balanced in the design



Austin et al., 2003

# Direct Monitoring of Critical Path

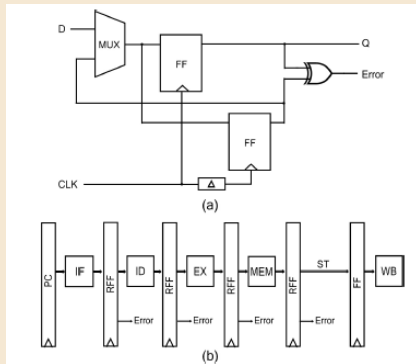
## Razor Flip-Flop (a) and Architecture using it (b)



- Speculative operation requires an additional pipeline stage
- Design may not be suitable for designs that have many critical paths (**increase in area and flip-flop power**)


# Indirect Critical Path Monitor

## TEAtime approach

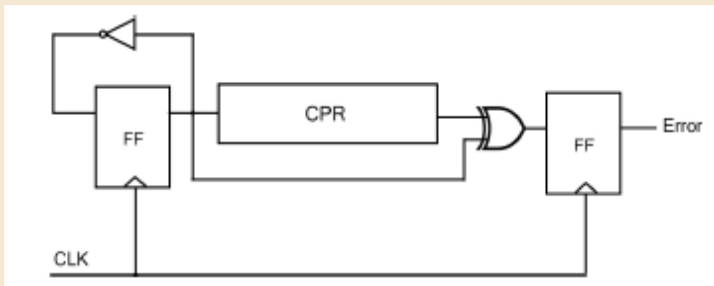


- Use of **Critical Path Replicas (CPRs)** to control voltage or frequency until one of them fail
- CPRs (1-bit version of potential critical paths) are located near potential critical paths to monitor them
- 1-bit detector may result in “oscillations”
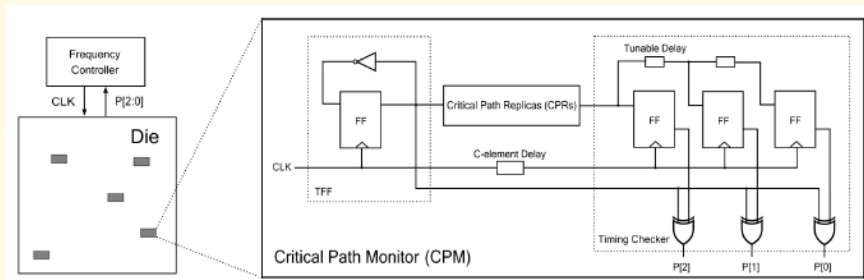
# Adaptive Frequency Control with Critical Path Monitor (Park, 2011)




P[2:0]	Delay of CPRs	Frequency Control
{0,0,0}	Fast	↑
{0,0,1}	Appropriate	—
{0,1,1}	Slow (Safety Margin)	↓
{1,1,1}		

# Use of C-elements to Combine CPRs

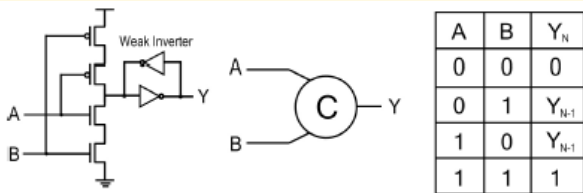

C-element and logic function


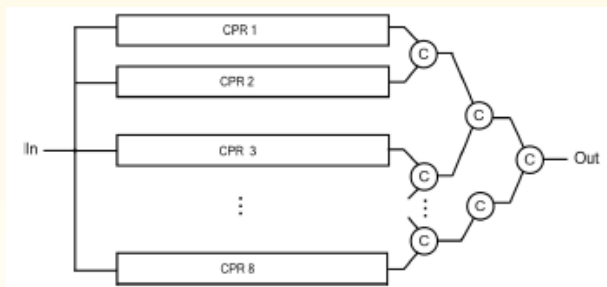


Configuration of 8 CPRs


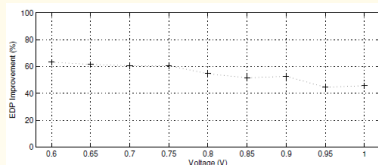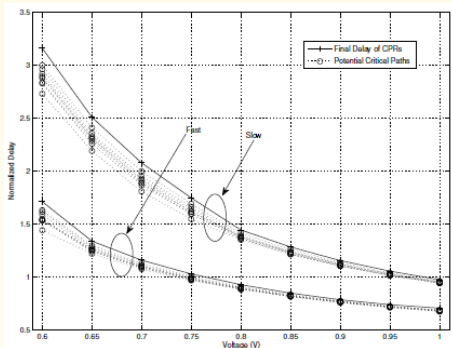
# Simulation Results

- MIPS core implemented in 45nm process
- Optimized to meet target frequency of 1.5GHz
  - Many critical paths
- Power results from HSPICE, PrimeTime and PrimeTimePX




Maximum improvement in  
Energy-Delay product

Delay changes in critical paths and  
CPMs
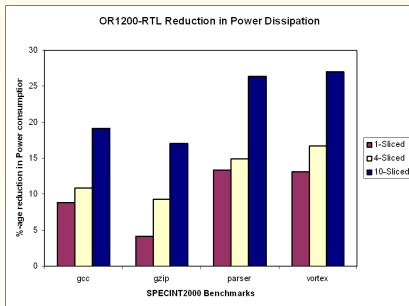
# Low-Power Annotations at the RT-Level (Viswanath, 2006)

- Given a microprocessor design and an instruction
  - Identify the instruction-driven slice
  - Shut off the rest of the circuitry
- This might include
  - Gating out parts of different blocks
  - Gating out floating point units during integer ALU execution
  - Turning off certain FSMs in different control blocks since exact constraints on their inputs are available due to instruction-driven slicing



# Low Power by Design: StrongArm 110

Start with Alpha 21064: 200 MHz @ 3.45V, Power = 26 W

Vdd reduction: Power reduction = 5.3X  $\Rightarrow$  4.9W

Reduce functions: Power reduction = 3X  $\Rightarrow$  1.6W

Scale process: Power reduction = 2X  $\Rightarrow$  0.8W

Clock load: Power reduction = 1.3X  $\Rightarrow$  0.6W

Clock rate: Power reduction = 1.25X  $\Rightarrow$  0.5W

Source: D. Dobberpuhl

## LongRun Technology Demonstration

MHz	Voltage	% Full Power
700	1.65	100%
400	1.4	41%
333	1.2	25%


$$\text{Power} = C \times V^2 \times F = 400\text{MHz}/700\text{MHz} \times 1.4\text{V}^2/1.65\text{V}^2 = 41\%$$

- ◆ Crusoe processor starts off at 700MHz
- ◆ DVD movie requires between 333 and 400MHz
- ◆ Power is reduced to 25 or 41% of full power
- ◆ The result is extended DVD playtime

Source: Doug Laird

## LongRun Technology in Operation

- ◆ Crusoe processor starts off at 700MHz
- ◆ Code Morphing software detects user activity
- ◆ The software dynamically adjusts MHz and voltage to the most efficient power level




Crusoe Processor  
AC/DC Modes

MHz	Voltage
700	1.65
667	1.65
633	1.60
600	1.60
566	1.55
533	1.55
500	1.50
466	1.50
433	1.45
400	1.40
366	1.35
333	1.30
300	1.25
266	1.20
233	1.15
200	1.10


Source: Doug Laird

## Dynamic Software Execution (2nd Pass)

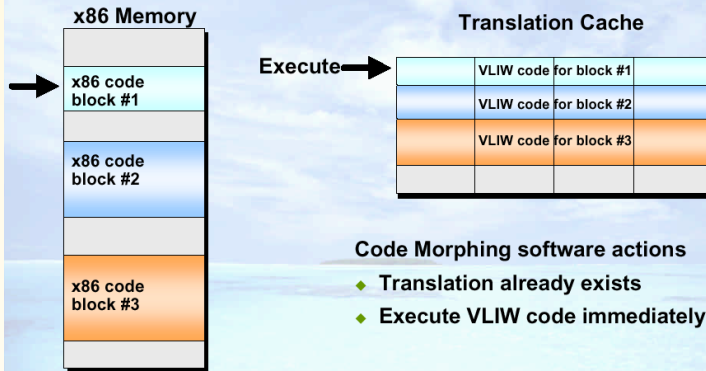


Source: Doug Laird

## Processor Thermal Comparison

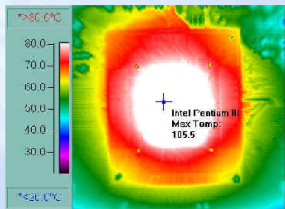

**Pentium III  
Playing DVD**

**105.5° C  
221.9° F**

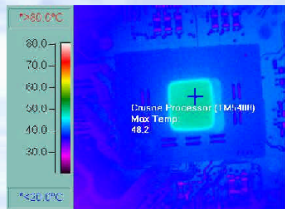
























**Crusoe Processor  
Playing DVD**

**48.2° C  
118.8° F**

Source: Doug Laird

# Intel Atom Power Management Modes

	C0 HFM	C0 LFM	C1/C2	C4	C6
Core Voltage					
Core Clock			OFF	OFF	OFF
PLL				OFF	OFF
L1 Caches			 Flushed	 Flushed	 OFF
L2 Caches				 Partial Flush	 OFF
Wake-Up Time	active	active	 < 1 $\mu$ s	 < 30 $\mu$ s	 < 100 $\mu$ s
Power	