

3. Implementing Logic in CMOS

Jacob Abraham


Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020

September 3, 2020

N- and P-channel Networks

 
- N- and P-channel networks implement logic functions
 - Each network connected between **Output** and V_{DD} or V_{SS}
 - Function defines path between the terminals



Duality in CMOS Networks


Straightforward way of constructing static CMOS circuits is to implement dual N- and P- networks

 - N- and P- networks must implement **complementary** functions
- Duality **sufficient** for correct operation (but not necessary)



$$A + B.C$$

Dual Networks

 


$$A.(B + C)$$

Look at functions of A, B and C, which will produce a connection between P and Q

Constructing Complex Gates


 
Example: $F = \overline{(A \cdot B) + (C \cdot D)}$

- 1 Take uninverted function $F = (A \cdot B) + (C \cdot D)$ and derive N-network
- 2 Identify *AND*, *OR* components: F is *OR* of AB, CD
- 3 Make connections of transistors




Construction of Complex Gates, Cont'd

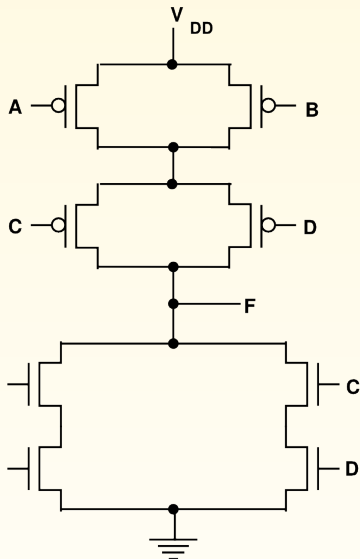 
- 4 Construct P-network by taking complement of N-expression $(AB + CD)$, which gives the expression, $(\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$
- 5 Combine P and N circuits



Layout of Complex Gate

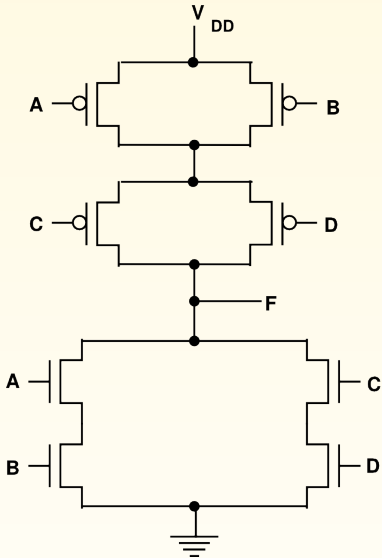

AND-OR-INVERT (AOI) gate

 

Note: Arbitrary shapes are not allowed in some nanoscale design rules

Example of Compound Gate

$$F = \overline{(A + B + C) \cdot D}$$


Note:

N- and P- graphs are duals of each other


In this case, the function is the complement of the switching function between F and GND

Question: Does it make any difference to the function if the transistor with input D is connected between the parallel A, B, C, transistors and GND?

What about the electrical behavior?

 


Example of More Complex Gate

 




$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$

Example of More Complex Gate

 

$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$

Exclusive-NOR Gate in CMOS

 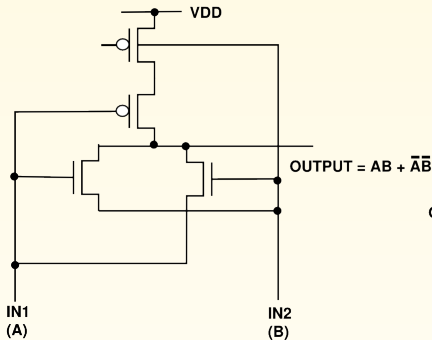 


Note: designs such as these should be checked very carefully for correct behavior using circuit simulation

Pseudo nMOS Logic

Based on the old NMOS technology where a “depletion” transistor was used as a pullup resistor


What happens when there is no path from Z to ground (i.e., $Z = 1$)?

 What happens when there is a path from Z to ground (i.e., $Z = 0$)?



Duality is Not Necessary for a CMOS Structure

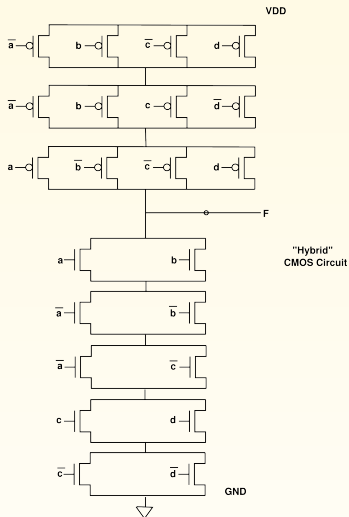Functions realized by N and P networks must be **complementary**, and one of them must conduct for every input combination




$$F = a \cdot b + \bar{a} \cdot \bar{b} + a \cdot c + c \cdot d + \bar{c} \cdot \bar{d}$$

The N and P networks are **NOT** duals, but the **switching functions they implement are complementary**

 Example of Another Complex CMOS Gate

This circuit does not have a pMOS network – just one transistor for each function; it will work only if F and G are complements of each other. Why?




Can evaluate the voltages at F and G ($\{0, V_{DD}\}$) for each value of x, y , and z

$$F = x \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot z + x \cdot y \cdot \bar{z} + x \cdot y \cdot z$$

$$G = \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z}$$

 Example of Another Complex CMOS Gate

This circuit does not have a pMOS network – just one transistor for each function; it will work only if F and G are complements of each other. Why?




Can evaluate the voltages at F and G ($\{0, V_{DD}\}$) for each value of x, y , and z

$$F = x \cdot \bar{y} \cdot z + \bar{x} \cdot y \cdot z + x \cdot y \cdot \bar{z} + x \cdot y \cdot z$$

$$G = \bar{x} \cdot y \cdot \bar{z} + x \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z}$$

 Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of x, y , and z which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$


$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$

$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)

 Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of x, y , and z which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$


$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$

$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)

 Example of Another Complex CMOS Gate, Cont'd



Can also follow **every** path from F and G to GND and identify values of x, y , and z which will enable the path to be enabled.

$$\overline{F} = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot y \cdot \overline{z}$$

$$\begin{aligned} F &= (x + y) \cdot (\overline{x} + y + z) \cdot (x + \overline{y} + z) \\ &= (y + x \cdot z) \cdot (x + \overline{y} + z) \\ &= x \cdot y + y \cdot z + x \cdot z \end{aligned}$$

$$\begin{aligned} G &= \overline{x} \cdot y \cdot \overline{z} + x \cdot \overline{y} \cdot \overline{z} + \overline{x} \cdot \overline{y} \\ &= \overline{x} \cdot \overline{y} + \overline{x} \cdot \overline{z} + \overline{y} \cdot \overline{z} \end{aligned}$$

Can you describe the functions in simple terms?

(Hint: look at the **number** of input variables which are true (or false) when the output is 1.)


Voltages represent digital logic values

- **Strength** of signal:
 - How close it approximates ideal voltage
- V_{DD} and GND rails are strongest 1 and 0
- nMOS transistors pass a strong 0
 - But degraded or weak 1
- pMOS transistors pass a strong 1
 - But degraded or weak 0


Therefore, nMOS transistors are best for the “pull-down” network

Pass Transistors and Transmission Gates


 
Transistors can be used as switches; however, they could produce degraded outputs



 Transmission gates pass both 0 and 1 well




Pass Transistor Logic

  


“Pull-Up” Circuit

 - Used to restore degraded logic 1 from output of nMOS pass transistor




Pass Transistor Logic – Better Layout

 Group similar transistors, so they can be in the same well




Tristate Buffer produces **Z** (high impedance) when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

 


Non-Restoring Tristate

 - Transmission gate acts as a tristate buffer
- Only two transistors, but **nonrestoring**
- Noise on A is passed to Y






Tristate Inverter

 Tristate inverter produces restored output, but complements signal



Multiplexers

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

   


How many transistors are needed?
(The better design uses 3 NAND gates and 1 inverter)

Transmission Gate MUX


Nonrestoring MUX

 - Uses two transmission gates \Rightarrow only 4 transistors



Inverting MUX – adds an inverter

 
- Uses compound gate AOI22
- Alternatively, a pair of tristate inverters (same thing)



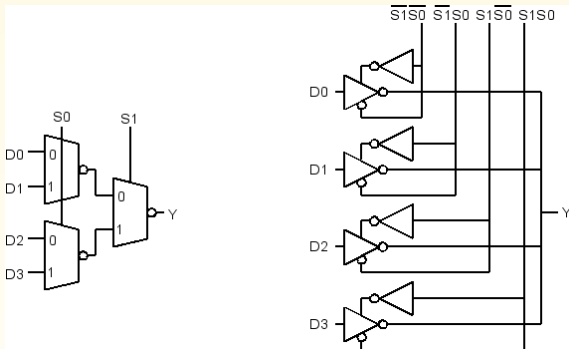4:1 Multiplexer


A 4:1 MUX chooses one of 4 inputs using two selects

- Two levels of 2:1 MUXes
- Alternatively, four tristates





Basic Memory Element

 - When $\text{CLK} = 1$, latch is transparent
 - D flows through to Q like a buffer
- When $\text{CLK} = 0$, the latch is opaque
 - Q holds its old value independent of D
- a.k.a., **transparent latch** or **level-sensitive latch**




D Latch, Cont'd

  D Latch Design:
MUX chooses
between D and
old Q





D Latch
Operation

 


D Flip-Flop (D-Flop)

Another common storage element

  - When CLK rises, D is copied to Q
- At all other times, Q holds its value
- **positive edge-triggered flip-flop** or **master-slave flip-flop**
- Built from “master” and “slave” D latches




D Flip-Flop Operation

 

Race Condition – Hold Time Failure

Back-to-back flops can malfunction from clock skew

 
- Second flip-flop fires late
- Sees first flip-flop change and captures its result
- Called **hold-time failure** or **race condition**



Non-Overlapping Clocks

A simple way to prevent races

 - This works as long as non-overlap exceeds clock skew
- Used in safe (conservative) designs
- Industry does not generally use this approach – managing skew more carefully instead



Building a library of standard cells


- Layout can be time consuming
- One solution is to have layouts of commonly used functions (Inverter, NAND, OR, MUX, etc.), designed to fit together very well

Standard cell design methodology


- V_{DD} and GND should abut (standard height)
- Adjacent gates should satisfy design rules
- nMOS at bottom and pMOS at top
- All gates include well and substrate contacts
- One of the large industry suppliers is ARM, others include TSMC and other foundries

Examples of Standard Cell Layout

Inverter

 

NAND3

 

Horizontal N-diffusion and P-diffusion strips

Vertical Polysilicon gates

Metal1 V_{DD} rail at top, Metal1 GND rail at bottom



32λ by 40λ

Wiring Tracks and Well Spacing

Wiring Track is the space required for a wire

  Example, 4λ width, 4λ spacing from neighbor = 8λ pitch



Transistors also consume one wiring track



Example, **well spacing**: wells must surround transistors by 6λ


Implies 12λ between opposite transistor flavors

Leaves room for one wire track

  


 Example of Area Estimation

Estimate area by counting
wiring tracks
Multiply by 8 to express in λ




 Estimating area of O3AI
Sketch a stick diagram and estimate
area




 Example Circuit 1

Fill in the Karnaugh map to represent the Boolean function implemented by the pass-transistor circuit.



Example Circuit 1

 


$F(a,b,c,d,e):$

a,b,c,d,e):

		e				e			
		c							
		a							
b	d	0	0	1	1	1	1	0	0
		1	1	0	0	0	0	1	1
		0	0	1	1	1	0	1	0
		1	1	0	0	0	1	0	1
		0	1	5	4	20	21	17	16
		2	3	7	6	22	23	19	18
		10	11	15	14	30	31	27	26
		8	9	13	12	28	29	25	24

 Example Circuit 2


Find the function, F , implemented by the following circuit



$$\overline{A} + BC + \overline{B} \overline{C}$$

 Example Circuit 2


Find the function, F , implemented by the following circuit



$$\overline{A} + BC + \overline{B} \overline{C}$$

 
Example Circuit 3

Find the functions X and Y implemented by the following circuit



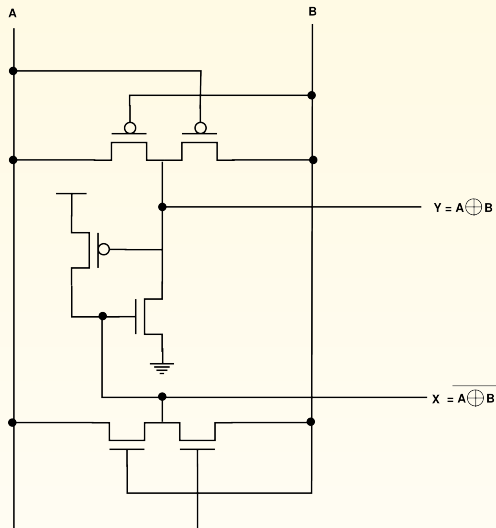Example Circuit 3

Find the functions X and Y implemented by the following circuit



Functions to Circuits

Label the circuit so that it implements the function:

$$F = a \cdot (b \cdot c + \bar{b} \cdot \bar{c})$$

