

## 7. Combinational Circuits

Jacob Abraham

Department of Electrical and Computer Engineering  
The University of Texas at Austin

VLSI Design  
Fall 2020

September 17, 2020

“IEEE UT created a Discord server to help all ECE students with group studying and collaboration. Each ECE course has a channel where you can communicate with other students in the class about coursework. The Discord can be also be used for discussion about other ECE-related topics, including interview preparation and registration advice. Use this link to join the Discord: <https://discord.gg/7kWzKze> (IEEE membership not required to join).”

# Review: Logical Effort, Gates and Paths

Term	Stage	Path
Number of stages	1	N
Logical effort	$g$	$G = \prod g_i$
Electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
Branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
Effort	$f = gh$	$F = GBH$
Effort delay	$f$	$D_F = \sum f_i$
Parasitic delay	$p$	$P = \sum p_i$
Delay	$d = f + p$	$D = \sum d_i = D_F + P$

# Steps in Logical Effort


- |                                   |                                  |
|-----------------------------------|----------------------------------|
| 1. Compute path effort            | $F = GBH$                        |
| 2. Estimate best number of stages | $N = \log_4 F$                   |
| 3. Sketch path with N stages      |                                  |
| 4. Estimate least delay           | $D = NF^{\frac{1}{N}} + P$       |
| 5. Determine best stage effort    | $\hat{f} = F^{\frac{1}{N}}$      |
| 6. Find gate sizes                | $C_{in} = \frac{g_i C_{out}}{f}$ |

## Limits of logical effort

- Chicken and egg problem
  - Need path to compute G
  - But, don't know number of stages without G
- Simplistic delay model, neglects input rise time effects
- Interconnect
  - Iteration required in designs with significant wires
- Maximum speed only
  - Not minimum area/power for constrained delay
 
# Review: Decoder Example, Number of Stages

- 16 word, (32 bit) register file
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs  $A[3:0]$
- Each input may drive 10 unit-sized transistors



## Find: number of stages, sizes of gates, speed

- Decoder effort is mainly electrical and branching
  - Electrical Effort:  $H = (32 \cdot 3) / 10 = 9.6$
  - Branching Effort:  $B = 8$
- If we neglect logical effort (assume  $G = 1$ )
  - Path Effort:  $F = GBH = 76.8$
- Number of Stages:  $N = \log_4 F = 3.1$
- Try a 3-stage design

# Decoder Review: Gate Sizes and Delay

Logical Effort:  $G = 1 * 6/3 * 1 = 2$


Path Effort:  $F = GBH = 154$

Stage Effort:  $\hat{f} = F^{\frac{1}{3}} = 5.36$

Path Delay:  $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

Gate sizes:  $z = 96 * 1 / 5.36 = 18$

Gate sizes:  $y = 18 * 2 / 5.36 = 6.7$

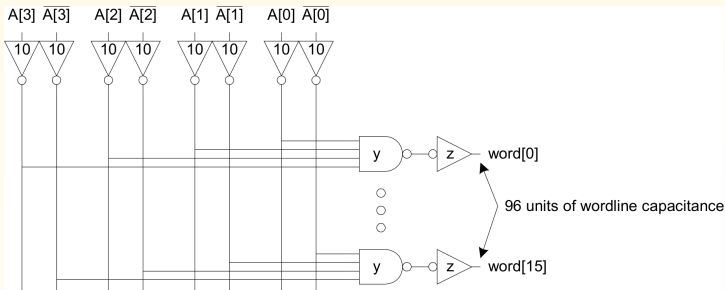


# Decoder Review: Comparison

Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6
 
# Review: Logical Effort Example

Find the logical efforts for the inputs, a, b, and c in the circuit below.




Output		
	Rising	Falling
a		
b		
c		

Suggest a way to reduce the parasitic delay of this circuit by modifying the structure (but keeping the same function).


 
## Example, Cont'd

Find the logical efforts for the inputs, a, b, and c in the circuit below.



Output		
	Rising	Falling
a	55/18	22/15
b	55/18	22/15
c	35/18	7/9

To reduce the parasitic delay of this circuit, swap the parallel combination of pMOS transistors with inputs a, b with the pMOS transistor with input c


## Example: Sizing Paths

Size the path G1-G2-G3-G4 in the circuit below using logical effort  
Find the minimum delay and give the sizes of the P and N transistors to achieve this delay

Assume that the off-path capacitance is the same as the on-path capacitance for each branch

Input capacitance of Inverter G1 = 3 units.

 Load capacitance driven by Gate G4 = 52 units.




# Sizing Paths, Cont'd

Size the path G1-G2-G3-G4 in the circuit

Input capacitance of Inverter G1 = 3 units.

Load capacitance driven by Gate G4 = 52 units.

Delay = 4.8 FO4 units

 

Sizes of transistors:

Gate	P	N
Gate G4	8	8
Gate G3	5	5
Gate G2	3	3
Gate G1	2	1


Delay of the path from A through gates G5 and G4 (assuming the input from G2=1 and D=0): 2.08 FO4 units

# Example of “Bubble Pushing”

Implement the circuit described by the code below

```
module mux(input s, d0, d1,  
           output y);  
  assign y = s ? d1 : d0;  
endmodule
```


 
The specifications are easily met with a design using AND, OR and NOT gates



# Convert to Design using NAND/NOR/NOT Gates

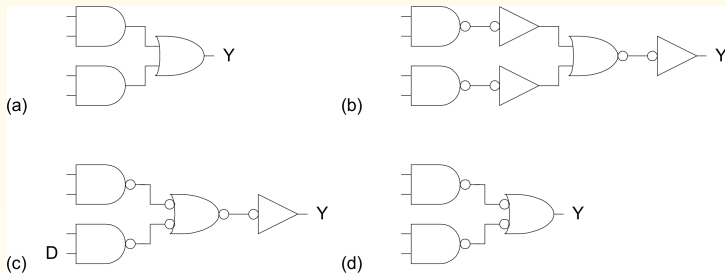
 
## Bubble Pushing

Start with network of AND/OR gates  
Convert to NAND/NOR + inverters  
Push bubbles around to simplify logic  
Use DeMorgan's Law


  
## Example, Continued


Now, design the circuit with one compound gate and one inverter.  
Assume that  $\bar{S}$  is available



# Compound Gates

Unit Inverter

$$Y = \overline{A}$$

 


$$g_A = 3/3$$

$$p = 3/3$$

AOI21

$$Y = A \cdot B + \overline{C}$$

 

$$g_A = 6/3$$



$$g_B = 6/3$$

$$g_C = 5/3$$

$$p = 7/3$$

AOI22

$$Y = A \cdot B + C \cdot \overline{D}$$

  

$$g_A = 6/3$$

$$g_B = 6/3$$



$$g_C = 6/3$$

$$g_D = 6/3$$

$$p = 12/3$$

Complex AOI

$$Y = A \cdot (B + C) + D \cdot E$$

  

$$g_A = 5/3$$

$$g_B = 8/3$$

$$g_C = 8/3$$

$$g_D = 8/3$$

$$g_E = 8/3$$


$$p = 16/3$$

# Another Example


A multiplexer has a maximum input capacitance of 16 units on each input. It must drive a load of 160 units

Estimate the delay of the NAND and compound gate designs

NAND Solution

 

Compound Solution

 

$$H = 160/16 = 10$$

$$B = 1$$

$$N = 2$$

$$P = 2 + 2 = 4$$

$$G = (4/3) \cdot (4/3) = 16/9$$

$$F = GBH = 160/9$$

$$\hat{f} = \sqrt[N]{F} = 4.2$$

$$D = N\hat{f} + P = 12.4\tau$$

$$H = 160/16 = 10$$

$$B = 1$$

$$N = 2$$

$$P = 4 + 1 = 5$$

$$G = (6/3) \cdot (1) = 2$$

$$F = GBH = 20$$



$$\hat{f} = \sqrt[N]{F} = 4.5$$

$$D = N\hat{f} + P = 14\tau$$


  
## Example, Cont'd


Annotate the designs for the multiplexer with transistor sizes which achieve the minimum delay


 
# Order of Inputs to a Transistor Stack

Delay of CMOS gate is affected by input order

- Parasitic delay model used in logical effort calculations is too simple
- Example, calculate parasitic delay for Y falling
  - If A arrives latest:  $2\tau$
  - If B arrives latest:  $2.33\tau$




Choosing inner and outer inputs

- Outer** input is closest to rail (power or ground): **B**
- Inner** input is closest to output: **A**
- If input arrival time is known
  - Connect latest arriving input to inner terminal**

# Asymmetric Gates

## Asymmetric gates favor one input over another

 
- Example, suppose input A of a NAND gate is most critical
  - Use smaller transistor on A (less capacitance)
  - Boost size of noncritical input
  - So total resistance is same



- Calculate logical effort
  - $g_A = 10/9$
  - $g_B = 2$
  - $g_{total} = g_A + g_B = 28/9$
- Symmetric gate approaches  $g = 1$  on critical input
- However, total logical effort goes up

# Symmetric Gates

Inputs can be made perfectly symmetric

 


Make both A and B behave like inner/outer inputs, and keep the P:N ratio 2:1

# Skewed Gates Favor One Edge Over Another










- Example, suppose rising output of inverter is most critical

- Downsize noncritical nMOS transistor

 

- Calculate logical effort by comparing to unskewed inverter with same effective resistance on that edge
  - $g_u = 2.5/3 = 5/6$ ;  $g_d = 2.5/1.5 = 5/3$
- Definition: Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition
- Skewed gates reduce size of noncritical transistors
  - **HI-skew** gates favor **rising output** (small nMOS)
  - **LO-skew** gates favor **falling output** (small pMOS)
- Logical effort is smaller for favored direction, but larger for the other direction


# Catalog of Skewed Gates

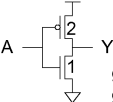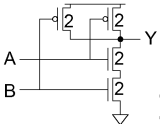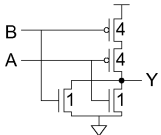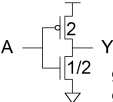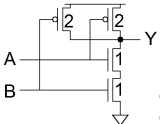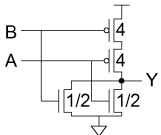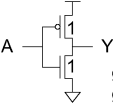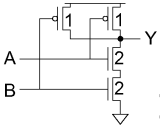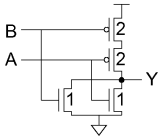	Inverter	NAND2	NOR2
unskewed	 $\begin{aligned} g_u &= 1 \\ g_d &= 1 \\ g_{avg} &= 1 \end{aligned}$	 $\begin{aligned} g_u &= 4/3 \\ g_d &= 4/3 \\ g_{avg} &= 4/3 \end{aligned}$	 $\begin{aligned} g_u &= 5/3 \\ g_d &= 5/3 \\ g_{avg} &= 5/3 \end{aligned}$
HI-skew	 $\begin{aligned} g_u &= 5/6 \\ g_d &= 5/3 \\ g_{avg} &= 5/4 \end{aligned}$	 $\begin{aligned} g_u &= 1 \\ g_d &= 2 \\ g_{avg} &= 3/2 \end{aligned}$	 $\begin{aligned} g_u &= 3/2 \\ g_d &= 3 \\ g_{avg} &= 9/4 \end{aligned}$
LO-skew	 $\begin{aligned} g_u &= 4/3 \\ g_d &= 2/3 \\ g_{avg} &= 1 \end{aligned}$	 $\begin{aligned} g_u &= 2 \\ g_d &= 1 \\ g_{avg} &= 3/2 \end{aligned}$	 $\begin{aligned} g_u &= 2 \\ g_d &= 1 \\ g_{avg} &= 3/2 \end{aligned}$

# Asymmetric Skew

 
## Combine asymmetric and skewed gates

- Downsize noncritical transistor on unimportant input
- Reduces parasitic delay for critical input


 
## Example – I


Find the (worst case) logical efforts of the different inputs in the CMOS circuit below.






## Example - II

 (a) Calculate the delay of the segment from B to S of the adder shown below (the AOI21 is a single stage, shown on the right), given that the output capacitance is 25 units (normalized), and the input capacitance at B is 6 units.




## Example - II, Cont'd



 


(b) Calculate the capacitances of the nodes  $y$ ,  $x$  and  $w$ , and the resulting widths of the transistors.
 
# Best P/N Ratio

- We have selected P/N ratio for unit rise and fall resistance ( $\mu = 2-3$  for an inverter).
- Alternative: choose ratio for least average delay
  - Example: inverter
    - Delay driving identical inverter
    - $t_{pdf} = (P + 1)$
    - $t_{pdr} = (P + 1)(\mu/P)$
    - $t_{pd} = (P + 1)(1 + \mu/P)/2 = (P + 1 + \mu + \mu/P)/2$
    - Differentiating  $t_{pd}$  w.r.t.  $P$ , we get, least delay for  $P = \sqrt{\mu}$
  - In general, best P/N ratio is sqrt of that giving equal delay
    - Only improves average delay slightly for inverters
    - But significantly decreases area and power



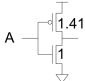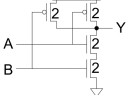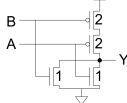	Inverter	NAND2	NOR2
fastest P/N ratio			
	$g_u = 1.15$ $g_d = 0.81$ $g_{avg} = 0.98$	$g_u = 4/3$ $g_d = 4/3$ $g_{avg} = 4/3$	$g_u = 2$ $g_d = 1$ $g_{avg} = 3/2$