

8. Design of Adders

Jacob Abraham

Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020

September 22, 2020

ECE Department, University of Texas at Austin

Lecture 8. Design of Adders


Jacob Abraham, September 22, 2020 1 / 31

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

ECE Department, University of Texas at Austin

Lecture 8. Design of Adders


Jacob Abraham, September 22, 2020 1 / 31

Full Adder Design I

Brute force implementation from equations


$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 


Full Adder Design II

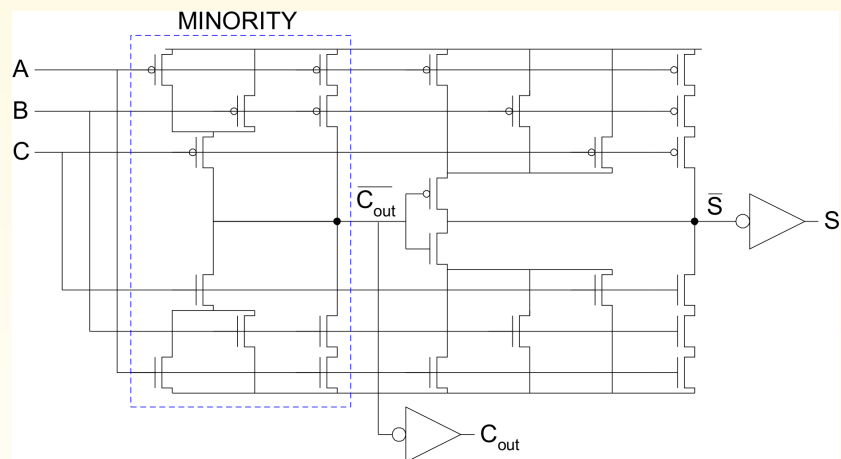- Factor S in terms of C_{out}
 - $S = A \cdot B \cdot C + (A + B + C) \cdot \overline{C_{out}}$
- Critical path is usually C to C_{out} in ripple adder




Layout of Full Adder

 - Clever layout circumvents usual line of diffusion
 - Use wide transistors on critical path
 - Eliminate output inverters




Full Adder Design III

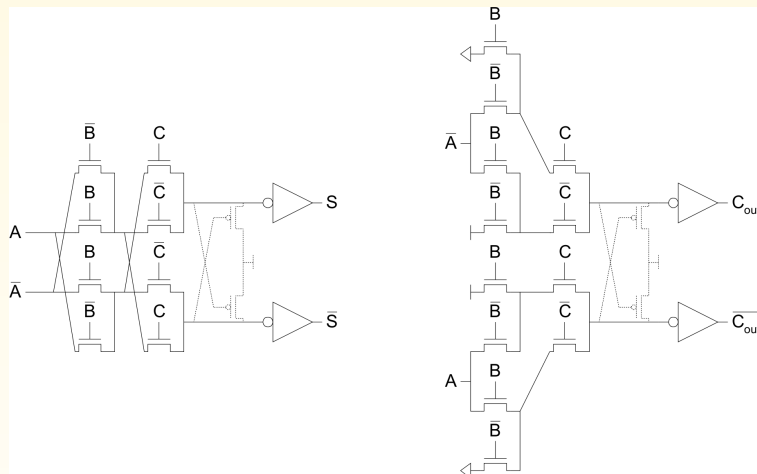- Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area




Ripple Carry Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry (small delay for carry signal)





Deal with Inversions to Speed Up Carry Path

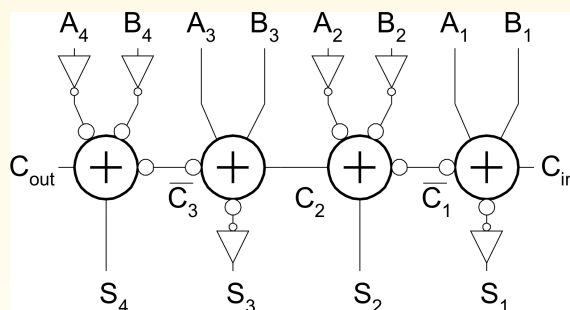- Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Carry Propagate Adders

  - N-bit adder called CPA
 - Each sum bit depends on all previous carries
 - How do we compute all these carries quickly?



Carry Propagate, Generate, Kill (P, G, K)

For a full adder, define what happens to carries

- **Generate:** $C_{out} = 1$, independent of C
 - $G = A \cdot B$
- **Propagate:** $C_{out} = C$
 - $P = A \oplus B$
- **Kill:** $C_{out} = 0$, independent of C
 - $K = \overline{A} \cdot \overline{B}$

Generate and Propagate for groups spanning i:j

- $G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$
- $P_{i:j} = P_{i:k} \cdot P_{k-1:j}$
- Base Case
 - $G_{i:i} \equiv G_i = A_i \cdot B_i$, $G_{0:0} = G_0 = C_{in}$
 - $P_{i:i} \equiv P_i = A_i \oplus B_i$, $P_{0:0} = P_0 = 0$
- Sum: $S_i = P_i \oplus G_{i-1:0}$


Carry Propagate, Generate, Kill (P, G, K)

For a full adder, define what happens to carries


- **Generate:** $C_{out} = 1$, independent of C
 - $G = A \cdot B$
- **Propagate:** $C_{out} = C$
 - $P = A \oplus B$
- **Kill:** $C_{out} = 0$, independent of C
 - $K = \overline{A} \cdot \overline{B}$

Generate and Propagate for groups spanning i:j

 - $G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$
- $P_{i:j} = P_{i:k} \cdot P_{k-1:j}$
- Base Case
 - $G_{i:i} \equiv G_i = A_i \cdot B_i$, $G_{0:0} = G_0 = C_{in}$
 - $P_{i:i} \equiv P_i = A_i \oplus B_i$, $P_{0:0} = P_0 = 0$
- Sum: $S_i = P_i \oplus G_{i-1:0}$




PG Logic

 


Ripple Carry Adder Revisited in the PG Framework

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

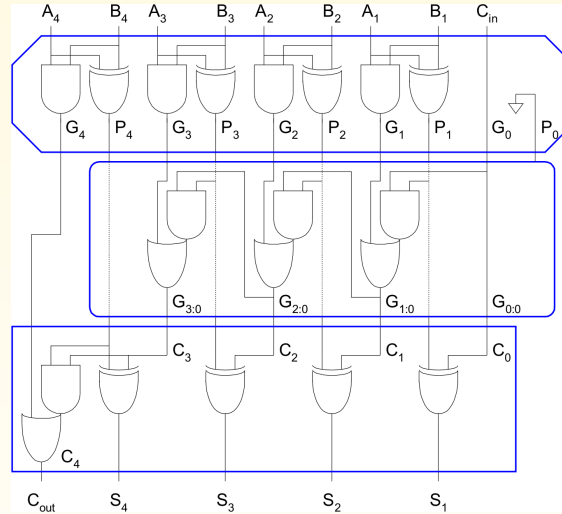


Ripple Carry PG Diagram
 
$$t_{ripple} = t_{pg} + (N - 1)t_{AO} + t_{xor}$$




PG Diagram Notation

 


Carry-Skip Adder

 - Carry-ripple is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal



Carry-Skip PG Diagram

 


For k n -bit groups ($N = nk$)


$$t_{skip} = t_{pg} + [2(n - 1) + (k - 1)] t_{AO} + t_{xor}$$

Carry-Lookahead Adder (CLA)

 
- Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel
- Uses higher-valency cells with more than two inputs



CLA PG Diagram

 


Higher Valency Cells

 


Carry-Select Adder

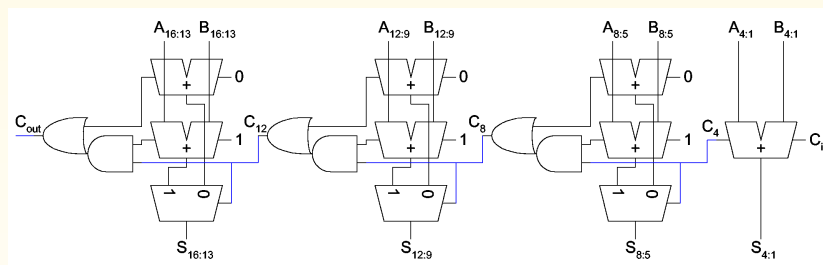- Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- Carry-select adder precomputes n-bit sums for both possible carries into n-bit group




Tree Adders

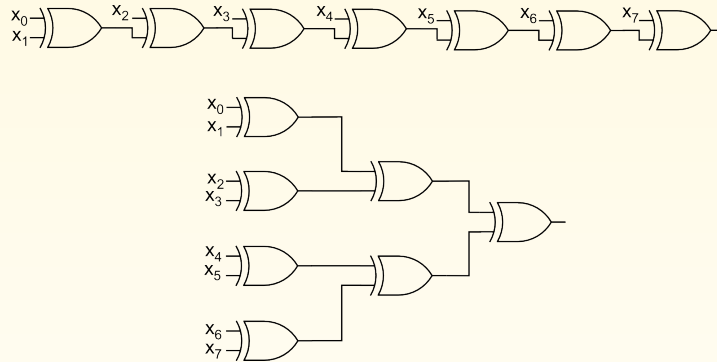- Tree structures can be used to speed up computations
- Look at computing the XOR of 8 bits using 2-input XOR-gates




- If lookahead is good for adders, lookahead across lookahead!
 - Recursive lookahead gives $O(\log N)$ delay
- Many variations on tree adders


Brent-Kung Adder

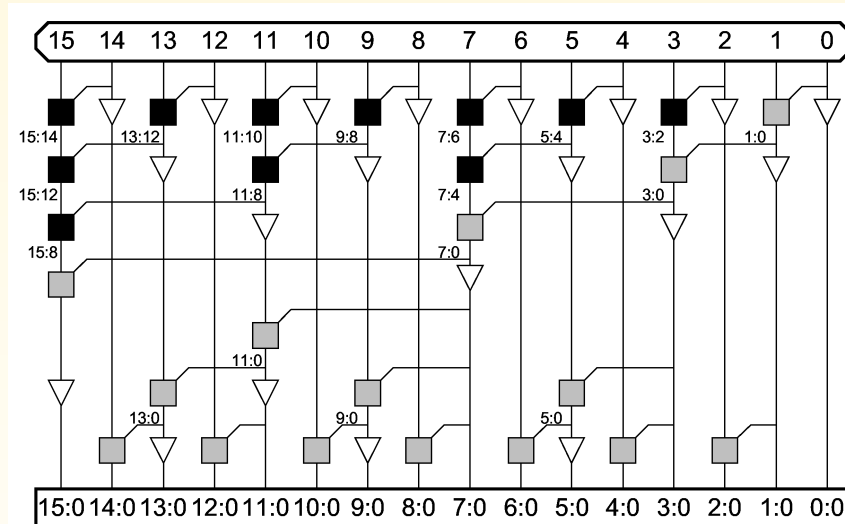

Sklansky Adder

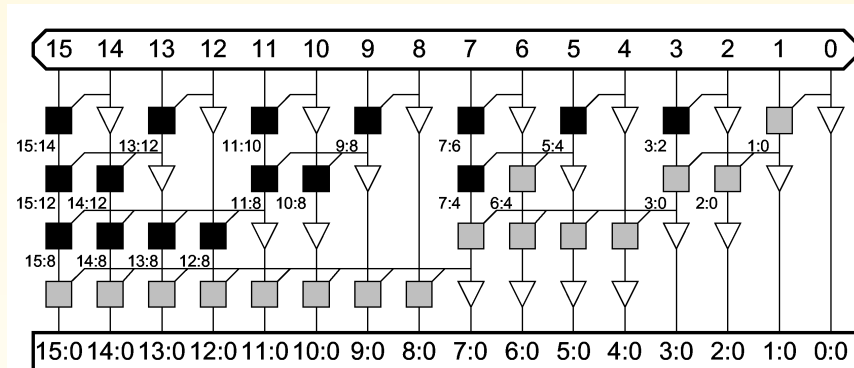


Kogge-Stone Adder

 


Tree Adder Taxonomy

- Ideal N-bit tree adder would have
 - $L = \log N$ logic levels
 - Fanout never exceeding 2
 - No more than one wiring track between levels
- Describe adder with 3-D taxonomy (l, f, t)
 - Logic levels: $L + l$
 - Fanout: $2f + 1$
 - Wiring tracks: 2^t
- Known tree adders sit on plane defined by $l + f + t = L - 1$


Tree Adder Taxonomy, Cont'd

 


Han-Carlson Adder

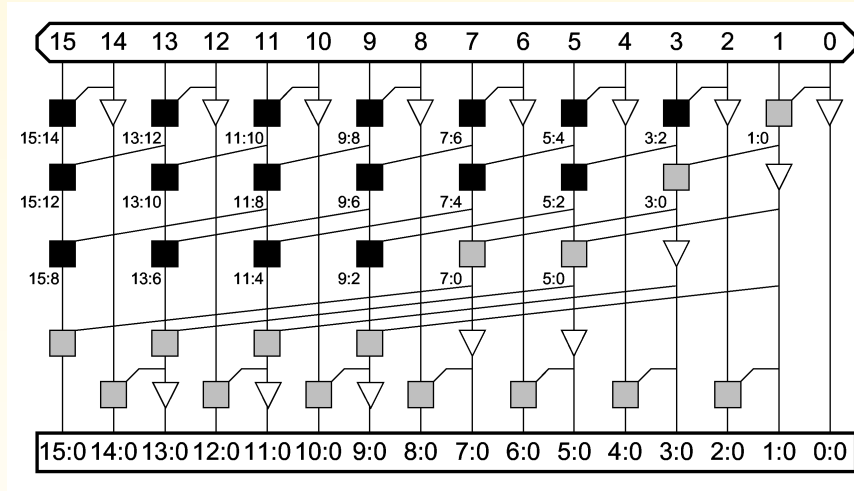


Brent-Kung Adder

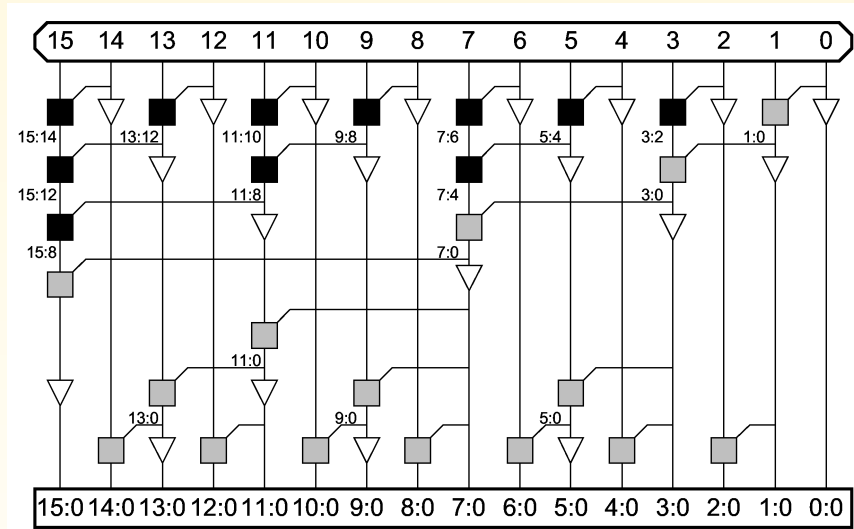


Knowles [2,1,1,1] Adder

 

Ladner-Fischer Adder

 

Tree Adder Taxonomy Revisited

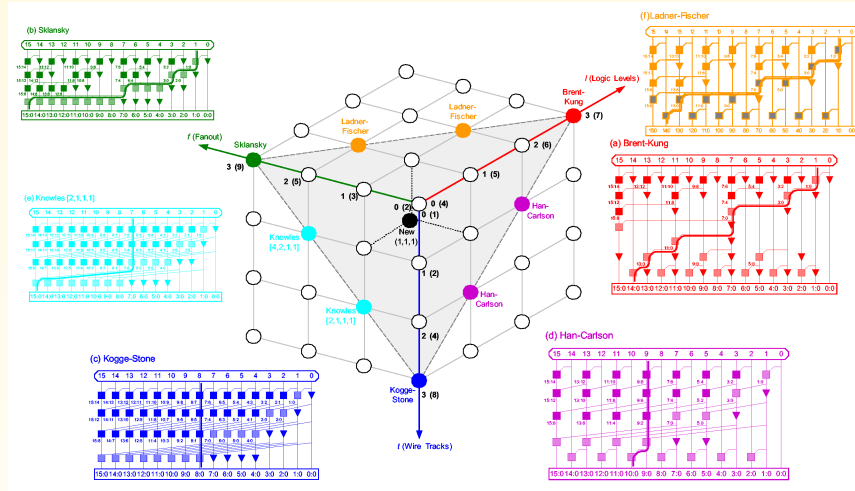

Summary of Adders

Adder architectures offer area/power/delay tradeoffs

Choose the best one for your application

Architecture	Classification	Logic levels	Max. fanout	Tracks	Cells
Ripple Carry		$N - 1$	1	1	N
Carry-skip($n=4$)		$N/4 + 5$	2	1	$1.25N$
Carry-inc. ($n=4$)		$N/4 + 2$	4	1	$2N$
Brent-Kung	(L-1,0,0)	$2\log_2 N - 1$	2	1	$2N$
Sklansky	(0,L-1,0)	$\log_2 N$	$N/2 + 1$	1	$0.5N\log_2 N$
Kogge-Stone	(0,0,L-1)	$\log_2 N$	2	$N/2$	$N\log_2 N$