

9. Datapath Design

Jacob Abraham


Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020

September 24, 2020

1s and 0s Detectors

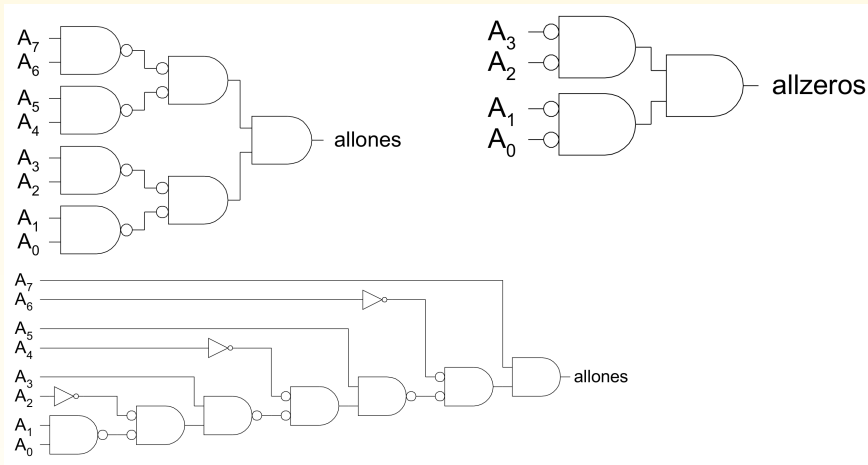
- 1s detector: N-input AND gate
- 0s detector: Inversions + 1s detector (N-input NOR)



Comparators


Equality Comparator

 - Check if each bit is equal (XNOR, or “equality gate”)
- 1s detect on bitwise equality



Magnitude Comparator

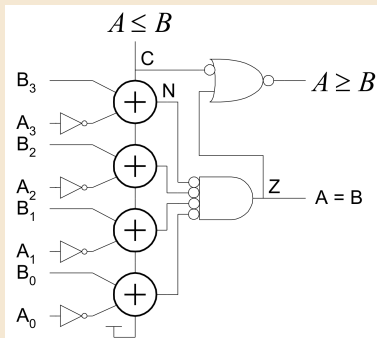- Compute $B - A$ and look at sign
- $B - A = B + \bar{A} + 1$
- For unsigned numbers, carry out is sign bit



Signed Versus Unsigned Numbers

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)


Magnitude Comparison

Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\overline{Z}	\overline{Z}
$A < B$	$\overline{C + Z}$	$\overline{(N \oplus V) + Z}$
$A > B$	\overline{C}	$(N \oplus V)$
$A \leq B$	C	$\overline{(N \oplus V)}$
$A \geq B$	$\overline{C} + Z$	$(N \oplus V) + Z$

- Logical Shift:
 - Shifts number left or right and fills with 0s
 - $1011 \text{ LSR } 1 = 0101$
 - $1011 \text{ LSL } 1 = 0110$
- Arithmetic Shift:
 - Shifts number left or right; right shift – sign extend
 - $1011 \text{ ASR } 1 = 1101$
 - $1011 \text{ ASL } 1 = 0110$
- Rotate:
 - Shifts number left or right and fills with lost bits
 - $1011 \text{ ROR } 1 = 1101$
 - $1011 \text{ ROL } 1 = 0111$

Funnel Shifter

 - A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N - k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N - k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	$N - k$

Computing $N-k$ requires an adder


Simplified Funnel Shifter

Optimize down to $2N-1$ bit input

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0, 0..0$	\bar{k}
Arithmetic Right	$A_{N-1} \dots A_{N-1}, A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0, 0..0$	\bar{k}
Rotate Right	$A_{N-2} \dots A_0, A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0, A_{N-1} \dots A_1$	\bar{k}


Funnel Shifter Design – 1

 - N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (Note: V_t drops)




Funnel Shifter Design – 2

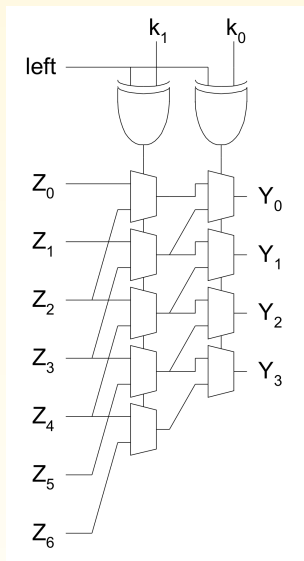- Log N stages of 2-input MUXes
 - No select decoding needed




Multi-Input Adders

 - Suppose we want to add k N -bit words
 - Example: $0001 + 0111 + 1101 + 0010 = 10111$
- Straightforward solution: $k-1$ N -input CPAs
 - Large and slow




Carry Save Addition

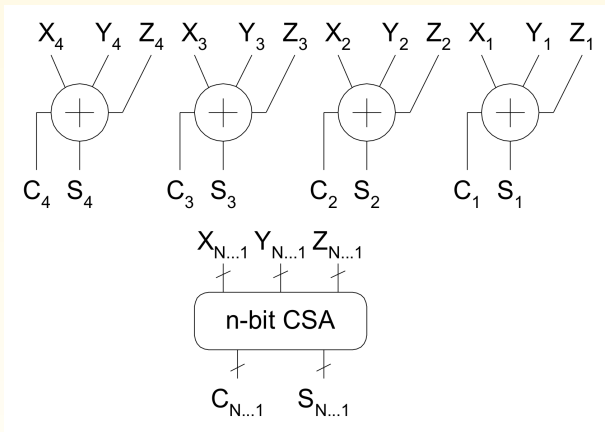- Full adder sums 3 inputs, produces 2 outputs
 - Carry output has twice the **weight** of sum output
- N full adders in parallel: **carry save adder**
 - Produce N sums and N carry outs




CSA Application

 - Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result




Parity Generators


Static XOR Tree

 

Dynamic XOR Circuit

 

Pass Gate Comparator

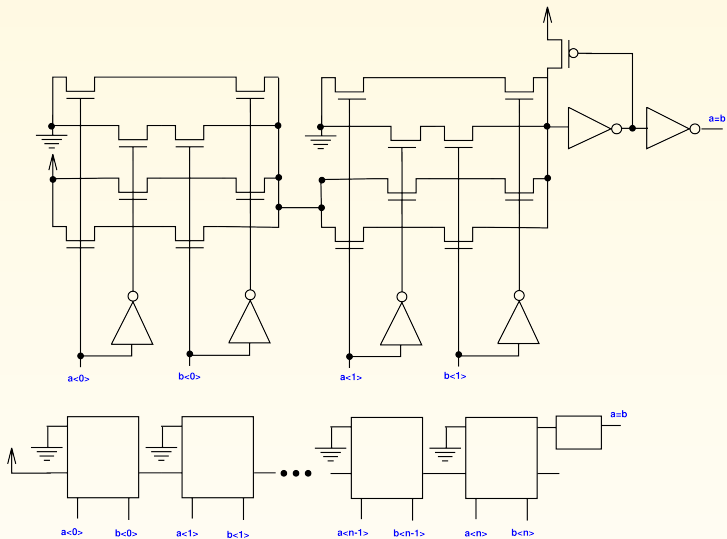

Multiplication

Example:

1100	:	12_{10}	multiplicand
0101	:	5_{10}	multiplier
<u>1100</u>			
0000			
1100			
0000			
<u>00111100</u>	:	60_{10}	product

partial products

- $M \times N$ -bit multiplication
 - Produce N M -bit partial products
 - Sum these to produce $M+N$ -bit product

General Form for Multiplication

Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$

Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$


Product:

$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$


								y_5	y_4	y_3	y_2	y_1	y_0	multiplicand multiplier
								x_5	x_4	x_3	x_2	x_1	x_0	
								x_0y_5	x_0y_4	x_0y_3	x_0y_2	x_0y_1	x_0y_0	partial products
					x_1y_5			x_1y_4	x_1y_3	x_1y_2	x_1y_1	x_1y_0		
				x_2y_5	x_2y_4	x_2y_3	x_2y_2	x_2y_1	x_2y_0					
			x_3y_5	x_3y_4	x_3y_3	x_3y_2	x_3y_1	x_3y_0						
		x_4y_5	x_4y_4	x_4y_3	x_4y_2	x_4y_1	x_4y_0							
	x_5y_5	x_5y_4	x_5y_3	x_5y_2	x_5y_1	x_5y_0								
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	product		

Dot Diagram

Each dot represents a bit

 


Array Multiplier

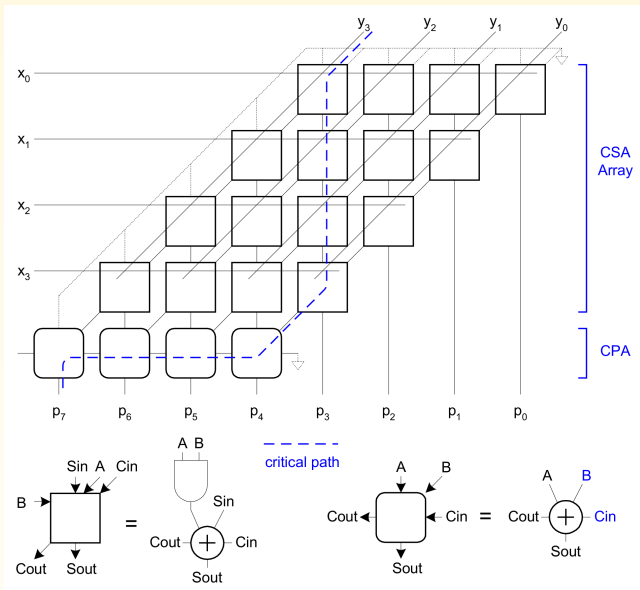

Rectangular Array

 Squash array to fit rectangular floorplan



Fewer Partial Products – Booth Encoding

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products
 - Faster and smaller?
 - Called radix- 2^r encoding
- Example, for $r = 2$, look at pairs of bits
 - Form partial products of 0 , Y , $2Y$, $3Y$
 - First three are easy, but $3Y$ requires adder
- Is there a way to get $3Y$ without an addition step?

Booth Encoding

- Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Radix-4 modified Booth encoding value

Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	X_i	$2X_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	$-0(=0)$	0	0	1


Advanced Multiplication

- Signed vs. unsigned inputs
- Higher radix Booth encoding
- Array vs. tree CSA networks

Serial Multiplication

- Lower area at expense of speed
 - Example, signal processing on bit streams
- Delay for $n \times n$ multiply
 - $2n$ bit product with $2n$ bit delay
 - Additional n -bit delay to shift n bits
 - Total delay of $3n$ bits
- Pipelined multiplier: possible to produce a new $2n$ bit product every $2n$ bit times after initial n bit delay
 - Only interest in high-order bits: n bit *latency* for n bit product
 - Can design for desired *throughput*


Serial Multiplier Architecture

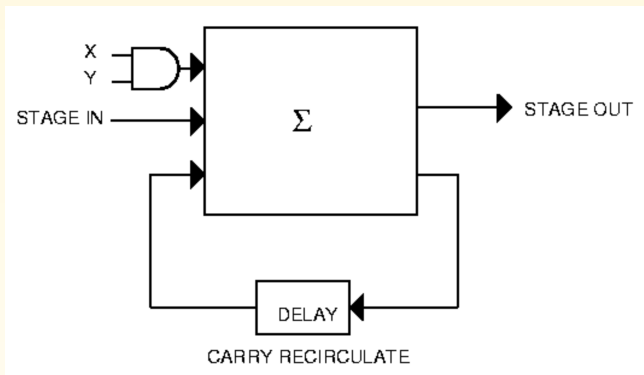

Area for structure increases linearly with number of bits, n

Pipeline multiplier accumulates partial product sums starting with the least significant partial product (result is n -bit number which is truncated to $n-1$ bits before the next partial product)

Division

 


- To divide A by B
 - Shift P and A one bit left
 - Subtract B from P , put the result back
 - If result is negative, additional steps, set low order bits of A to 0, otherwise to 1
 - “restoring” or “non-restoring” division to fix negative result

Divide A by B (n-bits)(view numbers as fractions between $1/2$ and 1)

- ① If B has k leading 0s when expressed using n bits, shift all registers by k bits
- ② For $i = 0$ to $(n-1)$
 - ① If top 3 bits of P equal, set $q_i = 0$, shift (P,A) one bit left
 - ② If top 3 bits of P not all equal, and P negative, set $q_i = -1$, (written as $\bar{1}$, shift (P,A) one bit left and add B
 - ③ Otherwise, set $q_i = 1$, shift (P,A) one bit left, subtract B
- ③ If the final remainder is negative, correct by adding B, correct quotient by subtracting 1; finally, shift remainder k bits right

Radix-4 SRT algorithm used in Pentium chip

Floating Point (IEEE 754-1985)

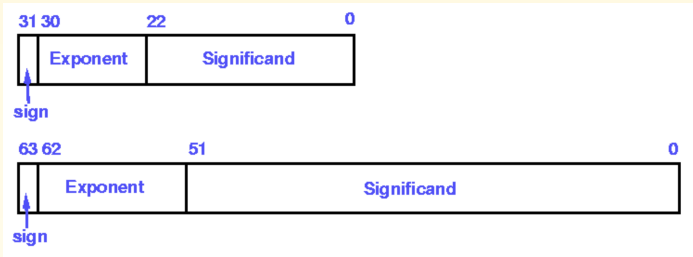

Single precision:

$$N = (-1)^{\text{sign}} \times 1.\text{Significand} \times 2^{\text{Exponent}-127}, 1 \leq \text{Exponent} \leq 254$$

$$N = (-1)^{\text{sign}} \times 0.\text{Significand} \times 2^{\text{Exponent}-126}, \text{Exponent} = 0$$

- “Hidden 1”, Bias, Special values **NaN**, ∞ , $-\infty$
- Rounds to nearest by default, but three other rounding modes
- “Halfway” result rounded to nearest even FP number
- “Denormal” numbers to represent results $< 1.0 \times 2^{E_{\min}}$
- Sophisticated facilities for handling exceptions

Newtons iteration: finding the 0 of a function

- Starting from a guess for the 0, approximate function by its tangent at the guess, form new guess based on where tangent has a 0

Goldschmidt's method

To compute a/b , iteratively, multiply both numerator and denominator by r where $r \times b = 1$

Find r iteratively

- Scale the problem so $b < 1$
- Set $x_0 = a$, $y_0 = b$ and write $b = 1 - \delta$ where $|\delta| < 1$
- If we pick $r_0 = 1 + \delta$, then $y_1 = r_0 y_0 = 1 - \delta^2$
- Next, pick $r_1 = 1 + \delta^2$, etc., and $y_i \rightarrow 1$

Used in the TI 8847 chip and AMD Athlon CPUs