

9. Datapath Design

Jacob Abraham

Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020

September 24, 2020


ECE Department, University of Texas at Austin

Lecture 9. Datapath Design

Jacob Abraham, September 24, 2020 1 / 27

1s and 0s Detectors

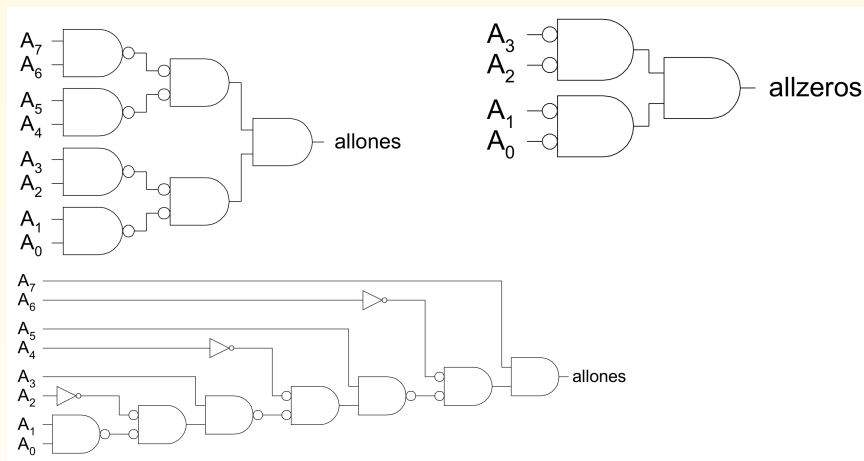- 1s detector: N-input AND gate
- 0s detector: Inversions + 1s detector (N-input NOR)



ECE Department, University of Texas at Austin


Lecture 9. Datapath Design

Jacob Abraham, September 24, 2020 1 / 27

Comparators


Equality Comparator

 - Check if each bit is equal (XNOR, or “equality gate”)
- 1s detect on bitwise equality



Magnitude Comparator

 - Compute $B - A$ and look at sign
- $B - A = B + \bar{A} + 1$
- For unsigned numbers, carry out is sign bit



Signed Versus Unsigned Numbers

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)

Magnitude Comparison


| Relation | Unsigned Comparison | Signed Comparison |
|------------|---------------------|-------------------------------------|
| $A = B$ | Z | Z |
| $A \neq B$ | \bar{Z} | \bar{Z} |
| $A < B$ | $\bar{C} + \bar{Z}$ | $\overline{(N \oplus V) + \bar{Z}}$ |
| $A > B$ | \bar{C} | $(N \oplus V)$ |
| $A \leq B$ | C | $\overline{(N \oplus V)}$ |
| $A \geq B$ | $\bar{C} + Z$ | $(N \oplus V) + Z$ |

Shifters

- Logical Shift:
 - Shifts number left or right and fills with 0s
 - 1011 LSR 1 = 0101
 - 1011 LSL 1 = 0110
- Arithmetic Shift:
 - Shifts number left or right; right shift – sign extend
 - 1011 ASR 1 = 1101
 - 1011 ASL 1 = 0110
- Rotate:
 - Shifts number left or right and fills with lost bits
 - 1011 ROR 1 = 1101
 - 1011 ROL 1 = 0111

Funnel Shifter

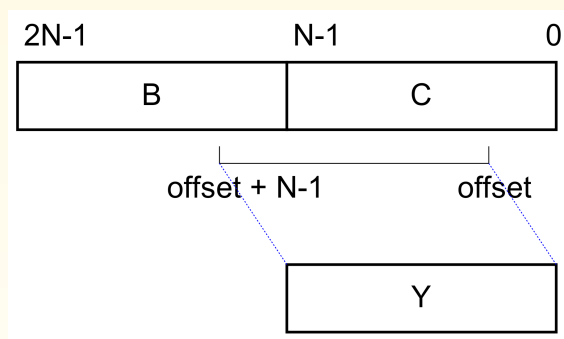- A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Operation

| Shift Type | B | C | Offset |
|------------------|---|---------------------|---------|
| Logical Right | $0 \dots 0$ | $A_{N-1} \dots A_0$ | k |
| Logical Left | $A_{N-1} \dots A_0$ | $0 \dots 0$ | $N - k$ |
| Arithmetic Right | $A_{N-1} \dots A_{N-1}$ (sign extension) | $A_{N-1} \dots A_0$ | k |
| Arithmetic Left | $A_{N-1} \dots A_0$ | 0 | $N - k$ |
| Rotate Right | $A_{N-1} \dots A_0$ | $A_{N-1} \dots A_0$ | k |
| Rotate Left | $A_{N-1} \dots A_0$ | $A_{N-1} \dots A_0$ | $N - k$ |

Computing $N-k$ requires an adder


Simplified Funnel Shifter

Optimize down to $2N-1$ bit input

| Shift Type | Z | Offset |
|------------------|--|----------------|
| Logical Right | $0..0, A_{N-1} \dots A_0$ | k |
| Logical Left | $A_{N-1} \dots A_0, 0..0$ | \overline{k} |
| Arithmetic Right | $A_{N-1} \dots A_{N-1}, A_{N-1} \dots A_0$ | k |
| Arithmetic Left | $A_{N-1} \dots A_0, 0..0$ | \overline{k} |
| Rotate Right | $A_{N-2} \dots A_0, A_{N-1} \dots A_0$ | k |
| Rotate Left | $A_{N-1} \dots A_0, A_{N-1} \dots A_1$ | \overline{k} |


Funnel Shifter Design – 1

 - N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (Note: V_t drops)




Funnel Shifter Design – 2

 - Log N stages of 2-input MUXes
 - No select decoding needed




Multi-Input Adders

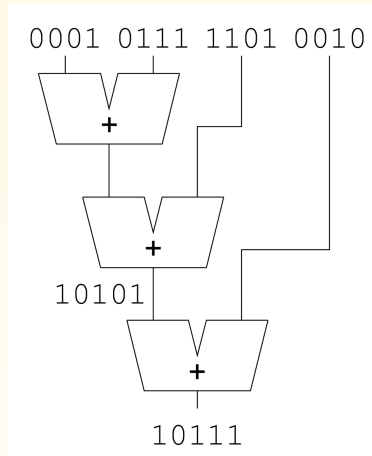- Suppose we want to add k N -bit words
 - Example: $0001 + 0111 + 1101 + 0010 = 10111$
- Straightforward solution: $k-1$ N -input CPAs
 - Large and slow




Carry Save Addition

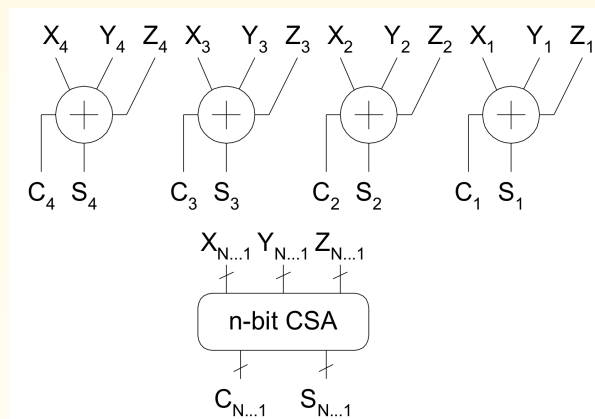- Full adder sums 3 inputs, produces 2 outputs
 - Carry output has twice the **weight** of sum output
- N full adders in parallel: **carry save adder**
 - Produce N sums and N carry outs




CSA Application

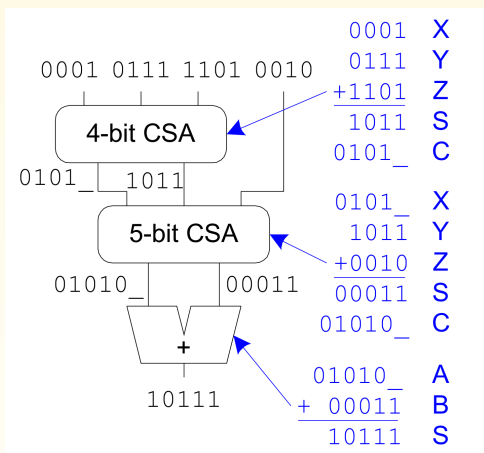- Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result




Parity Generators


Static XOR Tree

 

Dynamic XOR Circuit

 

Pass Gate Comparator

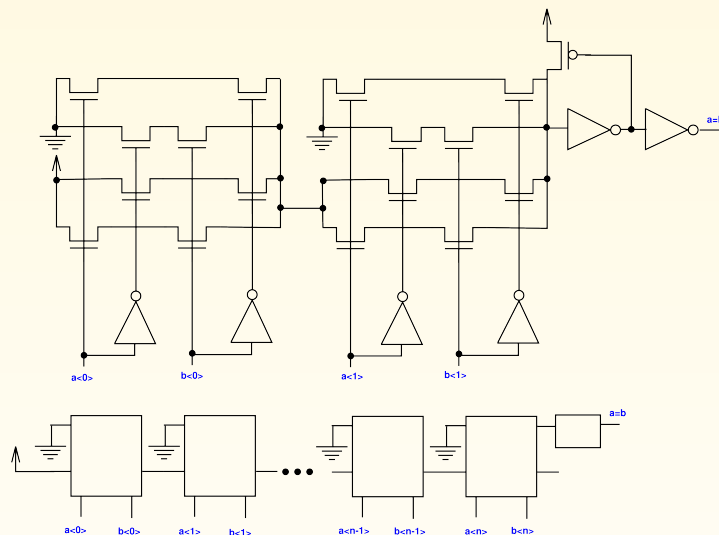

Multiplication

Example:

| | | | |
|----------|---|-----------|------------------|
| 1100 | : | 12_{10} | multiplicand |
| 0101 | : | 5_{10} | |
| 1100 | | | partial products |
| 0000 | | | |
| 1100 | | | |
| 0000 | | | |
| 00111100 | : | 60_{10} | product |

- M × N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product

General Form for Multiplication

Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$

Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$


Product:

$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$


[illegible]

Dot Diagram

Each dot represents a bit

 


Array Multiplier

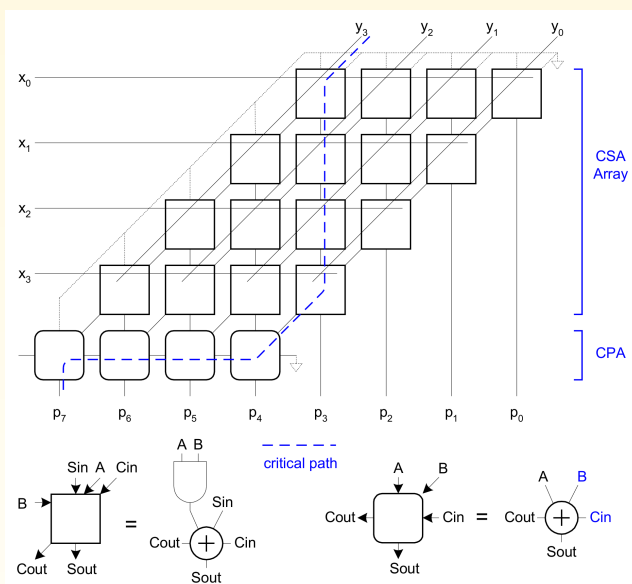

Rectangular Array

 Squash array to fit rectangular floorplan



Fewer Partial Products – Booth Encoding

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products
 - Faster and smaller?
 - Called radix- 2^r encoding
- Example, for $r = 2$, look at pairs of bits
 - Form partial products of 0, Y , $2Y$, $3Y$
 - First three are easy, but $3Y$ requires adder
- Is there a way to get $3Y$ without an addition step?

Booth Encoding

- Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Radix-4 modified Booth encoding value

| Inputs | | | Partial Product | Booth Selects | | |
|------------|----------|------------|-----------------|---------------|--------|-------|
| x_{2i+1} | x_{2i} | x_{2i-1} | PP_i | X_i | $2X_i$ | M_i |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | Y | 1 | 0 | 0 |
| 0 | 1 | 0 | Y | 1 | 0 | 0 |
| 0 | 1 | 1 | $2Y$ | 0 | 1 | 0 |
| 1 | 0 | 0 | $-2Y$ | 0 | 1 | 1 |
| 1 | 0 | 1 | $-Y$ | 1 | 0 | 1 |
| 1 | 1 | 0 | $-Y$ | 1 | 0 | 1 |
| 1 | 1 | 1 | $-0(=0)$ | 0 | 0 | 1 |


Advanced Multiplication

- Signed vs. unsigned inputs
- Higher radix Booth encoding
- Array vs. tree CSA networks

Serial Multiplication

- Lower area at expense of speed
 - Example, signal processing on bit streams
- Delay for $n \times n$ multiply
 - $2n$ bit product with $2n$ bit delay
 - Additional n -bit delay to shift n bits
 - Total delay of $3n$ bits
- Pipelined multiplier: possible to produce a new $2n$ bit product every $2n$ bit times after initial n bit delay
 - Only interest in high-order bits: n bit *latency* for n bit product
 - Can design for desired *throughput*


Serial Multiplier Architecture

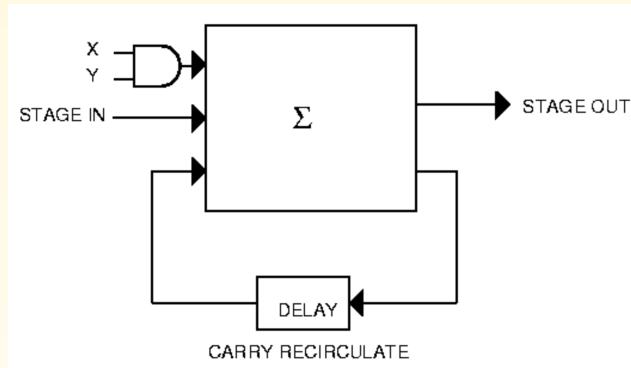

Area for structure increases linearly with number of bits, n

Pipeline multiplier accumulates partial product sums starting with the least significant partial product (result is n -bit number which is truncated to $n-1$ bits before the next partial product)

Division

 

- To divide A by B
 - Shift P and A one bit left
 - Subtract B from P, put the result back
 - If result is negative, additional steps, set low order bits of A to 0, otherwise to 1
 - “restoring” or “non-restoring” division to fix negative result

ECE Department, University of Texas at Austin

Lecture 9. Datapath Design

Jacob Abraham, September 24, 2020 24 / 27

SRT Division

Divide A by B (n-bits)(view numbers as fractions between $1/2$ and 1)

- ① If B has k leading 0s when expressed using n bits, shift all registers by k bits
- ② For $i = 0$ to $(n-1)$
 - ① If top 3 bits of P equal, set $q_i = 0$, shift (P,A) one bit left
 - ② If top 3 bits of P not all equal, and P negative, set $q_i = -1$, (written as $\bar{1}$, shift (P,A) one bit left and add B
 - ③ Otherwise, set $q_i = 1$, shift (P,A) one bit left, subtract B
- ③ If the final remainder is negative, correct by adding B, correct quotient by subtracting 1; finally, shift remainder k bits right


Radix-4 SRT algorithm used in Pentium chip

ECE Department, University of Texas at Austin

Lecture 9. Datapath Design

Jacob Abraham, September 24, 2020 25 / 27

Floating Point (IEEE 754-1985)

 

Single precision:

$$N = (-1)^{\text{sign}} \times 1.\text{Significand} \times 2^{\text{Exponent}-127}, 1 \leq \text{Exponent} \leq 254$$

$$N = (-1)^{\text{sign}} \times 0.\text{Significand} \times 2^{\text{Exponent}-126}, \text{Exponent} = 0$$

- “Hidden 1”, Bias, Special values **NaN**, ∞ , $-\infty$
- Rounds to nearest by default, but three other rounding modes
- “Halfway” result rounded to nearest even FP number
- “Denormal” numbers to represent results $< 1.0 \times 2^{E_{\min}}$
- Sophisticated facilities for handling exceptions

Iterative Division

Newton's iteration: finding the 0 of a function

- Starting from a guess for the 0, approximate function by its tangent at the guess, form new guess based on where tangent has a 0

Goldschmidt's method

To compute a/b , iteratively, multiply both numerator and denominator by r where $r \times b = 1$

Find r iteratively

- Scale the problem so $b < 1$
- Set $x_0 = a$, $y_0 = b$ and write $b = 1 - \delta$ where $|\delta| < 1$
- If we pick $r_0 = 1 + \delta$, then $y_1 = r_0 y_0 = 1 - \delta^2$
- Next, pick $r_1 = 1 + \delta^2$, etc., and $y_i \rightarrow 1$

Used in the TI 8847 chip and AMD Athlon CPUs